

FREE RFID



Elektor

electronics

leading the way

SEPTEMBER 2006

£3.80

www.elektor-electronics.co.uk

MINI SATELLITES

Your circuit in orbit



Scan the RFID code and win a prize!



Projects

- Intelligent RFID Reader
- Mini USB/DMX512 Converter
- Electronic Stamping (on beer, too!)




Pommy Want a Cracker?

A cracker of a catalogue that is!



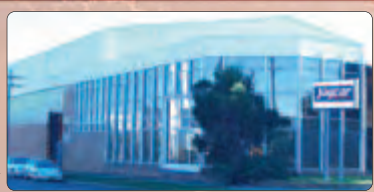For a FREE copy of our 410+ page catalogue from Australia ('It's a cracker') log on to our website www.jaycarelectronics.co.uk/catalogue
All prices £ Stg



POST AND PACKING CHARGES:

Order Value	Cost	Order Value	Cost
£20 - £49.99	£5	£200 - £499.99	£30
£50 - £99.99	£10	£500+	£40
£100 - £199.99	£20		

Max weight 12lb (5kg). Heavier parcels POA. Minimum order £20.

Starship Enterprise Door Sound Simulator

KC-5423 £11.75 + post & packing

This easy to build kit emulates the unique noise made when the cabin doors on the Starship Enterprise open and close. The 'shut' noise is also duplicated. The sound emulator can be triggered by switch contacts (normally open), which means you can use a reed magnet switch, IR beam or PIR detector. Kit includes a machined silkscreened, and pre-drilled case, speaker and all electronics components with clear English instructions.

- Requires 9-12VDC power



NEW FOR '06

For all you Trekkie fans

Two-Way SPDIF/Toslink Digital Audio Converter Kit

KC-5425 £7.25 + post and packing

This kit converts coaxial digital audio signals into optical or vice-versa. Use this bit stream converter in situations where one piece of equipment has an optical audio input and the other a coaxial digital output. Kit includes Toslink optical modules, PCB with overlay, case with screen printed lid, all electronic components and clear English instructions.



NEW FOR '06

Requires 9-12VDC wall adaptor (Maplin #JC91Y £14.99)

Theremin Synthesiser Kit

KC-5295 £14.75 + post and packing

The Theremin is a musical instrument that was invented last century. By moving your hand between the antenna and the metal plate, you create strange sound effects. Kit includes a machined, silkscreened and pre-drilled case, circuit board, all electronics components and clear English instructions.



As used in the Beach Boys classic hit 'Good Vibrations'

Requires 9VDC wall adaptor (Maplin #GSR74R £9.99)

Battery Zapper MkII

KC-5427 £29.00 + post & packing


This kit attacks a common cause of failure in wet lead acid cell batteries: sulphation. The circuit produces short bursts of high level energy to reverse the damaging sulphation effect. This improved unit features a battery health checker with LED indicator, new circuit protection against badly sulphated batteries, test points for a DMM and connection for a battery charger. Kit includes case with screen printed lid, PCB with overlay, all electronic components and clear English instructions.

Suitable for 6, 12 and 24V batteries

- Powered by the battery itself



NEW FOR '06

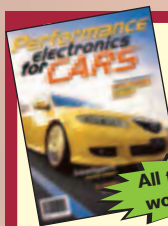

High Performance Electronic Projects for Cars Book

BS-5080 £7.00 + post & packing

Australia's leading electronics magazine Silicon Chip, has developed a range of projects for performance cars. There are 16 projects in total, ranging from devices for remapping fuel curves, to nitrous controllers. The book includes all instructions, components lists, colour pictures, and circuit layouts. There are also chapters on engine management, advanced systems and DIY modifications. Over 150 pages! All the projects are available in kit form, exclusively to Jaycar. Check out our website for all the details.

All these projects work off 12VDC

We stock an extensive range of quality automotive kits

Hand Controller for Digital Adjusters

KC-5386 £25.95 + post & packing

This hand controller is used for mapping/programming the independent electronic boost controller Kit (shown below). It features a two line LCD, and easy to use push buttons. It can be used to program the adjusters then removed, or left permanently connected to display the adjuster's operation. It is designed as an interface and display, and is not required for general adjuster functions after they have been programmed. Kit supplied with silkscreened and machined case, PCB, LCD, and all electronic components.



Independent Electronic Boost Controller

KC-5387 £25.95 + post & packing

Superb control over your turbo boost curve. It can be used in cars fitted with factory electronic boost control using the factory control solenoid, or cars without electronic boost control using a solenoid from a wrecker etc. This is ideal for switching between say, a race/street mode, or a performance/wet weather mode. Boost curve selection is via a dashboard switch, and is all programmed using the handheld digital controller KC-5386 (shown above). Kit supplied with PCB, machined case, and all electronic components.

- Suitable for EFI and engine management systems only



Smart Fuel Mixture Display


KC-5374 £8.95 + post & packing

This kit features auto dimming for night driving, emergency lean-out alarm, better circuit protection, and a 'dancing' display which operates when the ECU is operating in closed loop. Kit supplied with PCB and all electronic components.

- Car must be fitted with air flow and EGO sensors (standard on all EFI systems) for full functionality.

Recommended box UB3 (HB-6014) £1.40ea

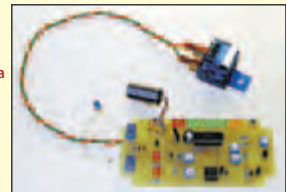Picture shows Spray Controller fitted to the Display Kit.



Add on Intercooler Water Spray Controller for Fuel Mixture Display Kit

KC-5422 £3.00 + post & packing

Simply add these few components to the Smart Fuel Mixture Display Kit (KC-5374) shown above and reduce water consumption by up to two-thirds.

Log on to www.jaycarelectronics.co.uk/catalogue for your FREE catalogue!
0800 032 7241
(Monday - Friday 09.00 to 17.30 GMT + 10 hours only).
For those who want to write: 100 Silverwater Rd Silverwater NSW 2128 Sydney AUSTRALIA

New 410+ page Catalogue
All prices in PDS




Jaycar Electronics

MikroElektronika

MICROCONTROLLER DEVELOPMENT TOOLS

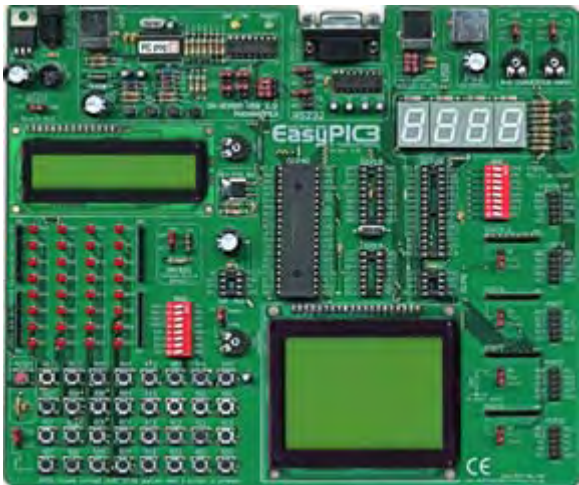Make PIC development easy with the **EasyPIC3 Starter Pack** - **only £99!**



A development system designed to make developing and experimenting with PIC microcontrollers easy and ideally suited to beginners.

- High quality development/experiment board with built-in USB 2.0 programmer and useful I/O devices.
- Can be powered from your PC's USB port or optional mains adapter.
- Compatible with Windows 98/ME/NT4/2000/XP.
- Supports virtually all 8, 14, 18, 28 and 40-pin PICmicro® devices in the 10F, 12F, 16F and 18F families.
- Built-in I/O devices include switches, LEDs, seven-segment displays, potentiometers and RS-232 interface.
- Connectors for character and graphic LCD modules, DS1820 temperature sensor, and USB and PS/2 interfaces.
- All I/O lines available for off-board expansion.
- Useful add-on boards available separately (see below).
- BASIC, C and Pascal compilers available separately (see below).
- Starter Pack includes PIC16F877A microcontroller, DS1820 temperature sensor, 16x2 character LCD, 128x64 pixel graphic LCD, RS-232 data cable, and USB programming cable for just £99.


EasyPIC3 Add-on Boards - from £4.95



A range of add-on boards for use with the EasyPIC3 or in conjunction with your own designs.

- DAC (12-bit D/A with SPI interface) - £9.95
- ADC (4-channel 12-bit A/D with SPI interface) £13.95
- ACCEL (2-axis accelerometer) - £11.95
- 485 (RS-485 interface) - £10.95
- CAN1 (CAN transceiver for CAN-enabled PICs) - £10.95
- CAN2 (CAN transceiver with SPI CAN controller) - £12.95
- KEYPAD (4x4 matrix keypad) - £4.95
- IRDA1 (IrDA transmitter/receiver) - £13.95
- IRDA2 (wireless RS-232 communications) - £13.95
- ETHERNET (SPI serial Ethernet controller) - available soon
- RTC (battery-backed real-time clock) - £10.95
- CF (Compact Flash card reader) - £10.95
- MMC (MMC/SD card reader) - £10.95
- EEPROM (I2C EEPROM) - £4.95

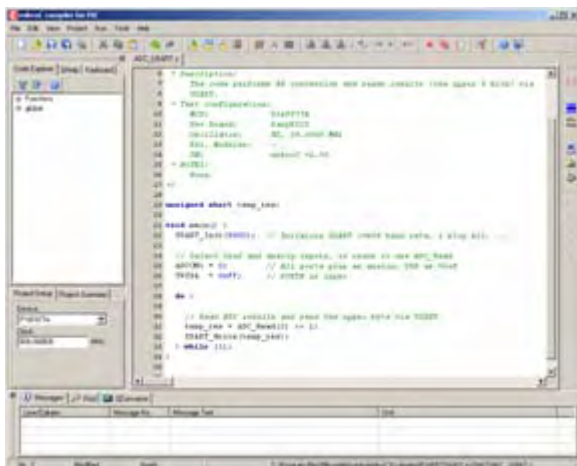mikroBASIC, mikroC and mikroPascal compilers - save 30%



Three easy to use yet powerful compilers for PIC microcontrollers, ideal for beginners and experienced programmers alike.

- Support for PIC12, PIC16 and PIC18 devices.
- User-friendly integrated development environment (IDE), compatible with Windows 98/ME/NT4/2000/XP.
- Highly adaptable code editor with useful features.
- Useful tools include USART terminal, 7-segment display decode and ASCII chart.
- Built-in routines support all EasyPIC3 I/O devices and add-on boards and include ADC, CAN, Compact Flash, EEPROM, Ethernet, Graphic LCD, I²C, LCD, 1-wire, PWM, RS-485, sound, SPI, USART, USB routines and many more.
- 30% discount for customers purchasing EasyPIC3.
- mikroBASIC - £85 (£59.50 with discount)
- mikroC—£145 (£101.50 with discount)
- mikroPascal - £85 (£59.50 with discount)

Call **0845 226 9451** or order online at www.breadboarding.co.uk

All prices exclude UK delivery (£5 normal/£10 next-day) and VAT. Major credit and debit cards accepted. Secure online ordering.

Say, one hundred and twenty-five thousand cards

Here at Elektor we're never stuck for ideas, enthusiasm, inspiration and gusto when it comes to publishing a high quality magazine on electronics. And that's despite the onslaught, in the UK newsstands, on specialist and trade magazines like ours in favour of publications carefully described as 'having a wider appeal to the general public'. Fortunately, over the past few months sales of *Elektor Electronics* magazine have increased to the extent that we're on the verge of re-entering the infamous 'Top-1000' of magazine titles sold through WH Smith — thank you all for your persistence in looking for our magazine!

We get a lot of inspiration from you, our readers, but also from professionals in the industry we speak to from time to time (in various languages). To cut a long story short, the result of talking to just a few people (best described as being in the right place as well as fully aware of Elektor's potential) is attached to this very copy of the magazine: a free RFID card containing a unique hexadecimal number string.


Although RFID gets a lot of attention these days and the associated industry is used to handling really tall orders, our contact persons at Philips and ACG took a deep breath when told them we needed 125,000 cards to go with the full European print run of the magazine. After some more sighing and moaning from the printers, binders and the odd local distributor, everyone agreed that *Elektor's Giant RFID Card Quest* went to prove that there may be some truth after all in the byline 'leading the way' we print with our masthead and logo. As far as I know, no other magazine has ever supplied free RFID cards in such great numbers as we're about to do with this September 2006 issue. It's a milestone and I'm sure the results of giving away a really useful item with the magazine will provide us with yet more inspiration and zest — they're catalysts really in the publication process we run every month for you.

Jan Buiting, Editor

26 Elektor RFID Reader

With this issue we're offering a free RFID card and description of a professional RFID reader for your own applications. The design described here can both read from and write to all types of RFID card that are compatible with the MIFARE and ISO 14443-A international standards.

14 RFID Chips Greet the Future

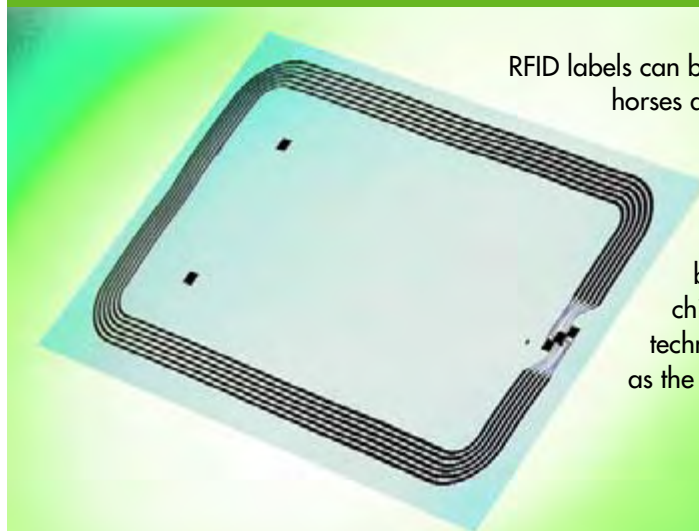

RFID labels can be used to mark racing horses as well as containers, scooters and perfume packages. Passports and sporting-event tickets can also be fitted with RFID chips. The underlying technology is just as varied as the potential applications.

70 USB/DMX512 Converter



Here is a project that will make some on the dance floors very happy... a DMX converter that will set you back just a few pounds.

CONTENTS

Volume 32
September 2006
no. 357



Ready-built PCB available!

know-how

40 Cubesats into Free Orbit

hands-on

- 22** The Elektor Electronics RFID Card
- 26** Elektor RFID Reader
- 34** Experimental RFID Reader
- 46** DiSEqC Monitor
- 60** FPGA Course (4)
- 64** Electronic Stamping
- 70** USB/DMX512 Converter
- 76** Design Tips
Miniature tweezers for SMDs

technology

- 14** RFID Chips Greet the Future
- 52** E-blocks Easy ARM Pack
- 56** Upgrade
for Flash Microcontroller Board

40 Cubesats into Free Orbit



The Delfi-C3 satellite designed by undergraduates offers its transponder and even asks amateurs to actively participate in its space mission. Taking your own pictures from space will soon be possible with the Compass-1, another amateur satellite. But can we shoot our own satellite into space?

info & market

- 6** Colophon
- 8** Mailbox
- 10** News & New Products
- 81** Elektor SHOP
- 84** Sneak Preview

infotainment

- 20** RFID Card Quest
- 75** Retronics:
Pontavi-Thomson Bridge
- 77** Hexadoku



Volume 32, Number 357, September 2006 ISSN 0268/4519

Elektor Electronics aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Publishers: Elektor Electronics (Publishing), Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) (0) 208 261 4509, fax: (+44) (0) 208 261 4447 www.elektor-electronics.co.uk.

The magazine is available from newsagents, bookshops and electronics retail outlets, or on subscription. *Elektor Electronics* is published 11 times a year with a double issue for July & August.

Under the name *Elektor* and *Elektuur*, the magazine is also published in French, German and Dutch. Together with franchised editions the magazine is on circulation in more than 50 countries.

International Editor: Mat Heffels (m.heffels@segment.nl)

Editor: Jan Buiting (editor@elektor-electronics.co.uk)

International editorial staff: Harry Baggen, Thijs Beckers, Ernst Krempelsauer, Jens Nickel, Guy Raedersdorf.

Design staff: Ton Giesberts, Paul Goossens, Luc Lemmens, Karel Walraven

Editorial secretariat: Hedwig Hennekens (secretariaat@segment.nl)

Graphic design / DTP: Ton Gulikers, Giel Dols

Managing Director / Publisher: Paul Snakkers

Marketing: Carlo van Nistelrooy

Customer Services: Margriet Debeij (m.debeij@segment.nl)

Subscriptions: Elektor Electronics (Publishing), Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England. Tel. (+44) (0) 208 261 4509, fax: (+44) (0) 208 261 4447 Internet: www.elektor-electronics.co.uk Email: subscriptions@elektor-electronics.co.uk Rates and terms are given on the Subscription Order Form

Head Office: Segment b.v. P.O. Box 75 NL-6190-AB Beek The Netherlands Telephone: (+31) 46 4389444, Fax: (+31) 46 4370161

Distribution: Seymour, 2 East Poultry Street, London EC1A, England Telephone: +44 (0)207 429 4073

UK Advertising: Huson International Media, Cambridge House, Gogmore Lane, Chertsey, Surrey KT16 9AP, England. Telephone: +44 (0)1932 564999, Fax: +44 (0)1932 564998 Email: relgar@husonmedia.com Internet: www.husonmedia.com Advertising rates and terms available on request.

International Advertising: Frank van de Raadt, address as Head Office Email: advertenties@elektuurnl Advertising rates and terms available on request.

Copyright Notice

The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board layouts, programmed integrated circuits, disks, CD-ROMs, software carriers and article texts published in our books and magazines (other than third-party advertisements) are copyright Segment b.v. and may not be reproduced or transmitted in any form or by any means, including photocopying, scanning or recording, in whole or in part without prior written permission from the Publishers. Such written permission must also be obtained before any part of this publication is stored in a retrieval system of any nature. Patent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does not accept responsibility for failing to identify such patent(s) or other protection. The submission of designs or articles implies permission to the Publishers to alter the text and design, and to use the contents in other Segment publications and activities. The Publishers cannot guarantee to return any material submitted to them.

Disclaimer

Prices and descriptions of publication-related items subject to change. Errors and omissions excluded.

© Segment b.v. 2006

Printed in the Netherlands




All Major Credit Cards Accepted!

ElmScan 5 Scan Tool

- Diagnose any car with EOBD
- Based on the ELM327 IC
- Supports all EOBD and OBD-II protocols
 - ✓ ISO15765-4 (CAN)
 - ✓ ISO14230-4 (Keyword 2000)
 - ✓ ISO9141-2
 - ✓ J1850 VPW
 - ✓ J1850 PWM
- 9600 or 38400 baud
- Supported by more software than any other OBD interface, including free and open source software
- Inexpensive
- Automatic protocol detection
- Package includes cables, software CD, and Quick Start Guide
- Buy from your local UK distributors!

www.ElmScan5.com/epe

Your price conscious PCB supplier



Online price calculation
Online ordering
Online order tracking
Online 24/24H and 7/7D

Interested? Contact us: +32 15 28 16 30
E-mail: euro@eurocircuits.com
www.eurocircuits.com

Verified

- pooling for standard boards
- up to 6 layers
- from 1 to 1000 pieces
- from 4 working days onwards

à la carte

- technology at the right price
- up to 8 layers
- from 1 to 1000 pieces
- from 3 working days onwards

On demand

- your board, our challenge
- up to 20 layers
- from 1 piece onwards
- from 2 working days onwards

BitScope

Pocket Analyzer

USB Oscilloscope & Logic Analyzer

The new generation Scope for the age of microelectronics.



- ✓ **8 Channel 40MS/s Logic Analyzer**
Capture digital signals down to 25nS with arbitrary trigger patterns.
- ✓ **3 Input 100MHz Analog DSO**
Classic Analog Scope using a standard x1/x10 BNC probe. Additional inputs on the POD for dual channel operation.
- ✓ **8 + 1 Mixed Signal Scope**
True MSO to capture an analog waveform time-synchronized with an 8 channel logic pattern triggered from any source.
- ✓ **Real-Time Spectrum Analyzer**
See the spectrum and waveform of analog signals simultaneously and in real-time
- ✓ **Waveform Generator**
Load up to 32K arbitrary waveform and replay via the onboard DAC (10MS/s) or a digital pattern from the POD (40MS/s)

Turn your PC or NoteBook into a powerful Scope and Logic Analyzer!

See inside your circuit in the analog and digital domains at the same time to make tracking down those elusive real-time bugs much easier.

Pocket Analyzer combines a high speed sample-synchronized storage scope and logic analyzer with a programmable waveform and logic pattern generator. Also included is an integrated real-time spectrum analyzer and powered "Smart POD" expansion interface so you've got all bases covered!

About the same size and weight as a Pocket PC, this USB powered BitScope needs no bulky accessories. It's the perfect low cost "go anywhere" test and debug solution.



Standard 1M/20pF BNC Input

200uV-20V/div with x10 probe
S/W select AC/DC coupling
S/W select 50ohm termination
Arbitrary Waveform Generator

BitScope "Smart POD" Connector

8 logic channels, 2 analog channels
Dual channel capture from POD A/B
Async serial I/O for external control
Logic Pattern generator 32K 40MS/s


BUS Powered USB 2.0 Device

Single USB cable to your PC
Compressed data transmission
Simple ASCII control protocol
BitScope Scripting Language

External/Passthru Power Supply

Auto senses an external supply -
removes power load from USB
for use with unpowered hubs.
Supplies up to 500mA via POD

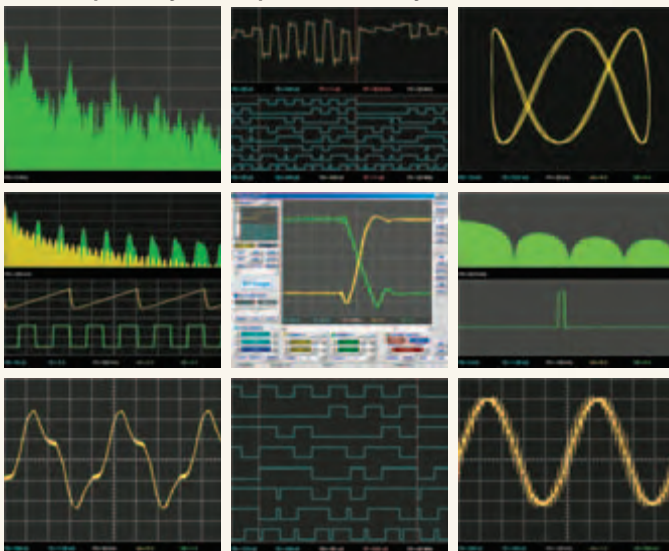BitScope and your PC provide an array of Virtual Instruments




BitScope DSO 1.2 software for Windows and Linux

- R&D
- Education
- Robotics
- Lab Scope
- Fast DAQ
- Service
- Debug

BitScope Pocket Analyzer uses highly integrated Surface Mount technology to provide functionality you would expect from scopes many times the size and price. Its programmable Virtual Machine architecture means new functionality can be added via software. For custom Data Acquisition, export directly to your spreadsheet.

www.bitscope.com

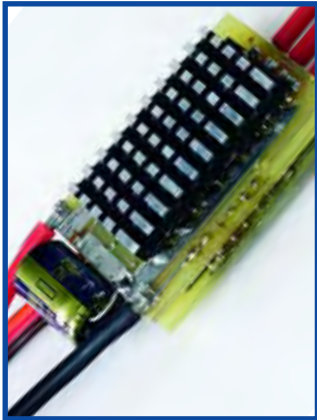

Brushless Motor Controller

Dear Elektor people — I'm definitely interested in your brushless motor controller (February 2006) but have run into a few problems while studying the design in some detail.

1. In Figure 5 (control module schematic), the connection to +5 V on K3 (channel from/to transmitter) is missing. On the PCB this connection is present.

2. The pdf file supplied free of charge by the author mentions a 'buzzer mode'. Also, it says that the configuration may be followed by means of 'beeps' from a 'buzzer' which I can no find anywhere in the design. How do I proceed?

I would like to use this controller with a modified power stage in a model car that definitely requires active braking. The default settings mentioned in the pdf do not agree with those in the magazine... I guess the pdf and the controller are not too well matched.

214820 (by email)

We confirm that the circuit diagram in Figure 5 fails to show that the centre pin of K3 is at +5 V, and that all +5 V points in the diagram are connected to this pin. The PCB however has all the right connections. This may be the cause of some confusion for which we apologise.

The 'buzzer' in the pdf document is the motor itself, which will produce a buzzing sound when repeatedly reversed at a high

rate. Useful if your model car careers into the undergrowth! The default settings are best taken from the pdf document. We hope you will get your model car on the asphalt soon!

Old PCB numbers

Dear Jan — while rummaging around on my loft I found an old Elektor printed circuit board numbered 'EPS 9860' I cannot remember anything about. The centre of the board has an LM324, two presets, diodes and a couple of electrolytics. Is this some kind of tone control or amplifier?

Tanglung (Singapore)

The EPS number 9860 is for a Peak Programme Meter from the January 1978 issue. The number may be confusing in this day and age because of the first two digits '98'. In the old days (we're talking about almost 30 years ago) a different PCB numbering system was used. Starting with the July/August 1978 double edition, a 5-digit PCB production number was adopted, for example, 78003, but only for Summer Circuits projects. The first two digits then indicate the year in which the project was first filed for publication. By November 1978 all articles got the 5-digit code, the first number issued being 79001. In January 1988 the system numbering was expanded to six digits, with the third digit (e.g., '4') indicating a Summer Circuits article (e.g., 884056). From March 2000 on, any software and other article-related items followed this number system by means of an extension. Before this change, software items were consecutively numbered, independently of the article number. Elektor production number extensions -1 through -9 are reserved for PCBs; -11 through -19 for floppy disks and downloads; -41 through -49 for controllers and -91 through -99 for modules, kits and the like. A special Forum topic is available on our website to help readers find articles from Elektor issues published before 1995. Provided an EPS number and/or an exact

article title can be supplied, any article since 1975 can be supplied as a photocopy and sent by post. We are however unable to find old articles based on vague or incorrect information.

FPGA, Colossus New & Old

Dear Jan — I am reading your FPGA Course articles with interest.


This is (coincidentally) in parallel with finding out more about the secret UK code breaking electronic computer of 1943 — 'Colossus' — which has been rebuilt and

tectures. Do you or Mike Simpson know if anyone has been inclined to try?

The 800-MHz Pentium emulator of Colossus runs slower than the valve and paper tape original, but it is of course a series emulation using software modulo-2 addition rather than using hard wired five bit parallel 0.5-MHz XOR adders like the original.

It would be interesting to see how fast a 50-MHz FPGA emulator could run, though the subject is probably far too specialised to interest the general reader!

Robert Cochrane (UK)

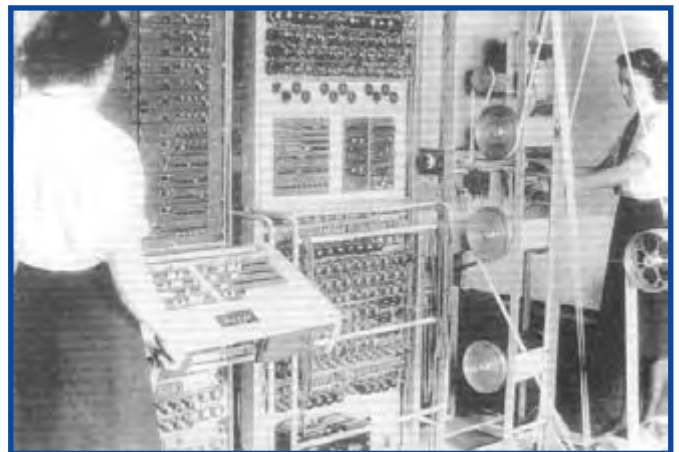

Bill Tutte's amazing statistical analysis of the German High Command Lorenz machine messages on which it was based. I have sent you a card showing the original (card reproduced here courtesy of Bletchly Park Trust Ltd, Ed.).

I was intrigued by the links between the two (Colossus was a switch programmed gate array computer with an architecture based on the derived structure of the Lorenz machine wheels) and saw that Mike Simpson ('Colossus Jr', Elektor Electronics October 2005) is obviously very familiar with this work.

I think it should be possible to build fast versions of Tunny (the electronic valve emulator of Lorenz) and Colossus with an FPGA, using a gate layout a bit like the original archi-

Thank for the interesting email and the nice postcard Robert! I have copied your message to Paul Goossens, our in-house FPGA pundit and await his response to the challenge.

£20 Sweex Router turned webserver

Dear Jan — referring to the February 2006 Modding & Tweaking pages, I can now send strings from a web page to the second serial port and there is no "terminal chatter" to mess things up. See

www.sunspot.co.uk/Projects/SWEEX/second_rs232.html

and

www.sunspot.co.uk/Projects/Sweex.htm

Corrections & Updates



2006 issue for a better appraisal of Jeroen's "general approach" to electronics.

ARMed for IDE, and more

Dear Jan — In the April 2005 issue you asked for details of practical applications for the *Elektor Electronics* ARMee Development System. I use my board as a test bed for embedded code development and to test other hardware. I do a lot of long term tests logging the results over sever-

I am trying to persuade the 'Linux Gods' to let hardware enthusiasts use their product as an 'Embedded Linux Distro' — one is working well enough to be of use and can be downloaded. They seem to modify Linux for its own sake — I want a tool to control hardware — hence my website.

Please keep the Jeroen Domburg projects coming — but support a proper 'distro' tool for use of those of us who solder.

The files on the USB stick can be modified without needing to change the router firmware from that published by Elektor.

Your author Jeroen Domburg led me into a new world of embedded Linux — trouble is they are all experts out there and there is almost no basic tutorial for an absolute beginner like me. You should have printed a health warning! But then I may not have jumped and I am glad I did. I only think a few of us did though.

I would love to see such a tutorial in *Elektor*. At below £20 all in the Sweex etc. are fantastic platforms compared to the average micro board.

Pay Jeroen to build an Embedded Linux "distro" that addresses all the ports and is easy to customise — available from your site(?)

Graham
(by email and on EE Forum)

Glad to see that the article spurred you into learning a bit about embedded Linux, Graham. The monthly Modding & Tweaking pages supplied by Jeroen are currently among the most popular in our magazine. See also 'Electroshack' in the July August

al hours or days. To this end, I designed an IDE interface board inspired by a couple of similar designs in *Elektor* (see photo). I can connect one or more hard disks, a CDROM drive and a CF card. I wrote FAT and ISO filing system drivers — all in all a very useful little system. I designed it in a way that allows more than one card to be plugged into the expansion connector at the same time (using a simple parallel bus) so my setup actually consists of an ARMee board connected to a 4-slot backplane. Then each card plugs into the backplane. However, I haven't yet got round to making any other types of boards, though I do have a paper design for an I/O card with A/D, D/A, relays, more digital I/O etc.

I also thought of designing a completely new system with an ARM9 core on a board that plugs into the backplane. This would be a much more flexible, modular system which could be expanded



FPGA Prototyping Board

March 2006, ref. 050370-1

A small number of FPGA Prototyping Boards from the first production batch have six SMD electrolytic capacitors fitted the wrong way around: C5, C6, C7, C13, C14 and C15. The dash on these capacitors has to be at the side of the connectors. If they are at the side of the LCD, there are two options:

1. you remove the capacitors and refit them with the correct orientation;
2. you return the FPGA board to us and we will do the above free of charge.

In any case, do not apply the supply voltage before it has been ascertained that the six electrolytics are fitted the right way around.

from my cells but one colleague was only getting 70% or so and blamed his cells. A quick swap of cells and charging on my charger produced in excess of 95%.

The result is that this tester is a good way of checking that your charger is doing what it is required to do. It is pointless getting higher and higher capacity cells if your charger is not fully charging them.

Geoff Moore (UK)

The article produced a good response and other readers have informed that it has enabled them to once and for all sort out ongoing problems in the 'battery department'.

easily. Just a thought. Please can you pass this info on to the designer.

Dave (UK)

Good to see Dave that our articles, boards and software have enabled you to actually build such an impressive system. This sort of information is very rewarding not only for the respective authors but also for us editors and designers working in a publishing company.

AA cells fully charged?

Dear Editor — several of my colleagues and myself have built this useful piece of equipment (Simple Rechargeable AA Cell Characteriser, April 2006, Ed.) and have found that not only does it check the quality of an AA cell but it also checks the amount of charge that different chargers put into the cells.

I get between 98% and 103% of the rated capacity

MailBox Terms

– Publication of reader's correspondence is at the discretion of the Editor.

– Viewpoints expressed by correspondents are not necessarily those of the Editor or Publisher.

– Correspondence may be translated or edited for length, clarity and style.

– When replying to Mailbox correspondence, please quote Issue number.

– Please send your Mailbox correspondence to:

editor@elektor-electronics.co.uk or
Elektor Electronics, The Editor,
1000 Great West Road,
Brentford TW8 9HH, England.

Compact varifocal camera

deView has launched its new Varifocal Day/Night IR Bullet camera to meet the demand for high performance compact cameras. Claimed an excellent choice for active monitoring and surveillance programs, the varifocal Sony 1/3-inch CCD compact camera features built in infra-red LED with automatic backlight

compensation. The 480 TV line colour camera is equipped to operate in various light conditions, automatically switching from colour images to high sensitivity monochrome-mode in low light environments.

Designed for discreet surveillance and easy installation, the

bullet camera has an attractive aluminium weatherproof housing together with slide-on sun shield and optional adjustable mounting bracket. This aesthetically pleasing product can be installed internally and externally. Ideal for industrial and

domestic property, commercial buildings and public buildings such as hospitals, schools, airports, ports etc.

www.deview.com.

(067111-10)



New generation Dataman universal USB programmers

Dataman has launched a new range of truly universal programmers built to meet the demands to support all device technologies. The new programmers all have a USB2 interface, which will particularly suit the needs of those engineers who prefer to use a laptop for program development.

The **Dataman-40Pro** is a small, fast and portable programmer with a 40 pin socket designed to support a wide range of memory and logic devices, including the latest low voltage chips. It is ideal for the engineer on-the-move who needs to set up his working environment quickly in a small space.

The **Dataman-48Pro** is for engineers who want the best



programming speeds and need to cover the widest possible range of memory and logic parts. It supports over 25,000 devices, from 5 volts down to 1.5 volts.

Large quantities of chips can be programmed more quickly by connecting multiple 48Pro programmers to the same PC. This setup will work either as a gang programmer or to program chips with different data simultaneously.

The **Dataman-40Pro** and **Dataman-48Pro** both have an In System Programming (ISP) connector with a JTAG interface, which programs chips whilst still inside the end target system.

The **Dataman-448Pro** is built to meet the demands of high volume production programming with minimal operator effort. The **Dataman-448Pro** features four independent universal programming modules with support for over 22,000 devices.

The new programmers are operated from an easy to use Windows interface. Software to cover new chips is released every 2-3 weeks and may be freely downloaded from Dataman's website.

To show their confidence in these new products Dataman is covering them for a 3 year warranty period.

(067192-1)

www.dataman.com

New searchable listing of European technology events

Tech Event Guide Ltd announces a new searchable online database which aims to become the definitive free listing of technology events throughout Europe. Unlike other listings, the online Tech Event Guide (www.techeventguide.com) includes information on key industry shows and conferences as well as company-specific seminars and training days provided by manufacturers and distributors. Registration to the site is free and



electronics engineers can browse a continually updated list of events by date, name or location, or make a selective search for events by location and key products areas such as Analogue, RF and Microwave, FPGAs, ASICs, & Logic, Power and Power Supplies, Processors, Microcontrollers and DSC or industry sectors such as Automotive & Transport, Aerospace and Defence, Communications & Networking, Control & Automation or EDA/Design Tools.

Users can download registration forms and event literature directly from the Tech Event Guide website or to click a link through to the event's own website for additional information. Once registered, users can create their own 'My Tech Event Guide' profile so that they can monitor every opportunity to

improve their skills and industry knowledge within their chosen locations, product groups and industry sectors. Companies can add details of their own seminars and training days to the site by completing the free registration and uploading their event information either as a free listing or as an

enhanced listing. Mike Maynard, Director of Tech Event Guide explained, "Although Event Diaries are already available, they typically focus primarily on major events and rarely include company-specific events. By giving registered companies the ability to upload details of their own seminars and training

days, the database aims to build into a definitive listing of technology events, and a valuable resource for electronics engineers, in every country throughout Europe."

(067192-3)

www.techeventguide.com

Network cable analyser gets an intelligence boost

Peak Electronic Design Limited have launched an enhanced version of their Network Cable Analyser the *Atlas IT* (model UTPO5), designed and made in the UK.

The *Atlas IT* has always had the unique ability to analyse many types of RJ45 based network cabling, including Ethernet, Token Ring, Patch cables and Crossover Cables. The connection pattern of the cables is automatically recognised and displayed on the unit's display as well as confirmation of the full connection pattern.

Now the *Atlas IT* has been enhanced with cable definitions of 8 more cable types, including Cisco terminal cables, Linn Audio network cables, Ethernet Economisers, 4 line crossovers, voice/data cables and many more. Additionally, for the first time ever, the *Atlas IT* can now recognise the cable type even if there are connection faults (such

as missing connections, swapped lines or other errors). It will display the cable type and highlight any lines that have errors.

The *Atlas IT* hardware has had a boost too, now it can cope with connection to live comms systems and even withstand the high telephone ring voltages (upto 80 V) associated with mixed voice and data cabling. Using the *Atlas IT* could not be easier, connect the main unit at one end of your cable run and the miniature (18mm cube) terminator at the other end. For socket testing you can use the supplied mini patch leads too. Press the test button and after a few seconds the results of the analysis are displayed on the clear alphanumeric display. If you use the unique Identified Terminators, the *Atlas IT* will identify the cable run for you too, allowing the easy testing and identification of many cable runs (upto 24) without having to

make lots of trips to swap terminators. The *Atlas IT* will automatically power down after a period of inactivity, so you'll never forget to switch it off.

Measuring just 103mm x 70mm x 20mm, the *Atlas IT* fits in the palm of your hand or could even happily dangle from a network socket! When it's not in use, it can be stored safe and sound in the supplied custom machined carry case along with your accessories, terminators, cables and a spare battery. The *Atlas IT* is available from many distributors including Farnell and Maplin as well as directly from the manufacturer



for £89.00
fully inclusive of UK delivery
and VAT.

(067192-2)

Peak Electronic Design Limited,
Atlas House,
Harpur Hill Business Park,
Buxton, Derbyshire SK17 9JL.
Tel. 01298 70012,
Fax. 01298 70046.
email: sales@peakelec.co.uk
web: www.peakelec.co.uk

Single-chip GPS receiver with highest sensitivity and low power consumption

Atmel® Corporation and u-blox AG, recently announced the availability of their latest weak-signal tracking GPS technology in an ultra-small form factor. The new single-chip ATR0635 measures just 7 x 10 mm, and integrates a complete ANTARIS® 4 GPS receiver including ROM-based SuperSense® software in a 96-pin BGA package. The small size plus the extremely low power consumption (62 mW in continuous power mode) make

the ROM-based ATR0635 an excellent fit for handheld and mobile applications such as mobile phones, PDAs, smartphones, after-market navigational products, and recreational consumer products.

Other products such as GPS 'plug-in' accessories for PCs, small GPS mice, Bluetooth® GPS devices, and other accessories equipped with GPS functionality will also enjoy the single chip's advantages in terms of small size,

reduced power needs, and built-in features such as the ANTARIS 4 USB port. Its high tracking sensitivity of -158 dBm allows for weak-signal tracking in urban canyons and even indoors.

The 96-pin, ball-grid-array single chip has an excellent cost-performance ratio due to needing only a few external components. The ATR0635 also brings benefits such as simplified chipset integration which accelerates design projects for ANTARIS 4-

based products.


ATR0635 samples in 7 x 10-mm 96-pin BGA packages are available now.

Atmel and u-blox offer a complete evaluation kit including ultra-small footprint example design which helps to dramatically shorten development cycle times.

Further information may be found at www.u-blox.com/products/atr0635.html.

(067192-5)

ByVac Electronics

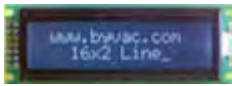

Cool Blue 16x2 LCD illuminated white lettering can be seen in full daylight. Makes projects stand out from the rest £9.95



Cool Blue 16x2 LCD fitted with the serial interface, simple text commands can scroll display, turn back light on off etc. Very powerful. £22.90

Serial LCD controller, will control any HD44780 compatible displays, 1,2 or 4 lines up to 180 total characters, fully software configurable automatic Baud rate etc. Works from RS232 port, USB to serial converter or directly from a microcontroller. Simple two character text commands for full control. Very small will fit behind the display. Scrolling text, macro facility, and much more. £11.00



Only 40mm x 19mm !



Serial Analogue board, 10 bit, 3 analogue inputs, 2 digital I/O, all serially controlled using simple 2 letter text commands. Analogue as percentage or absolute 10 bit value. £12.50

General purpose Digital-Analogue input/output. Converts serial text commands into digital I/O, 4 digital I/O and 4 analogue input channels. £11.00



Control hardware using simple text commands see www.byvac.co.uk

RS232 Serial Lead £4.50 Power Regulator £4.95

MONEY BACK GUARANTEE

If you are not completely satisfied, return the goods within 30 days for a full refund.

Purchase Options: On-Line at www.byvac.co.uk • Telephone 07905 734 348 • email sales@byvac.com • Cheque or Postal Order to: ByVac, PO BOX 4049, Penistone, SHEFFIELD, S36 6WP

Post and packing UK £2.50 World Wide £3.50
10% discount code for online orders use ELK6



PEAK www.peakelec.co.uk Peak Electronic Design Ltd
Atlas House
Harpur Hill Business Park
Buxton, SK17 9JL, UK
Tel. 01298 70012


"They are worthy additions to any amateur constructor's bench at an affordable price."
Rev. Dobbs, PW Magazine



LCR Analyser - Atlas LCR40

- Automatically identify and measure Inductors, Capacitors and Resistors.
- Automatic test frequency selection.
- Inductors from 1µH to 10H.
- Capacitors from 1pF to 10,000µF
- Resistors from 1Ω to 2MΩ.
- 1% Basic accuracy.

Example screenshots

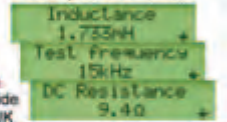

Made with pride here in the UK

Star Pack Offer - Buy both analysers for £130 and get a free carry case and free probe accessories!


Semiconductor Analyser - Atlas DCA55

- Automatically analyse most 2 and 3 leaded semi's: transistors, MOSFETs, JFETs, diodes, LEDs etc...
- Automatically identify all leads. Connect any way!
- Measures lots of parameters too, such as gain, PN characteristics, MOSFET gate thresholds, leakage current and much more.



£55

Example screenshots:

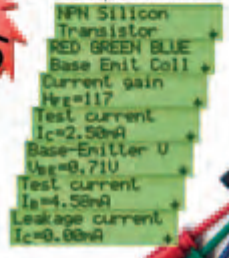


all prices include UK Delivery and VAT

№1 Number One Systems

Easy-PC for Windows


The World Beating PCB design software

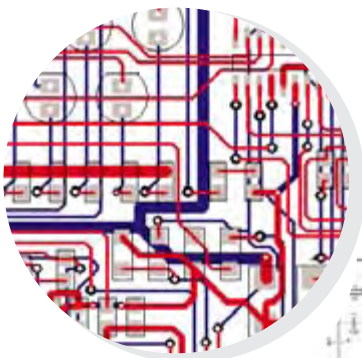

Easy-PC version 10 sets another milestone

Winning accolades the world over, Easy-PC for Windows V10 is another major milestone in the evolution of this extremely popular software tool. Try a demonstration copy of Easy-PC and prepare to be amazed at the power, versatility and remarkable value for money.

STILL FROM ONLY
£247
PLUS VAT

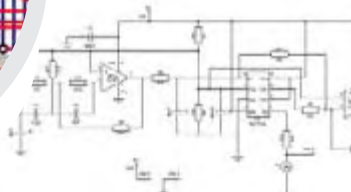

Fully integrated Schematics & PCB layout in a single application complete with forward and back annotation. Design and rules checks at all stages ensure integrity at all times. Professional manufacturing outputs allow you to finish the design process with ease.

Version 10 features

- Intelligent Gerber Import option
 - Track/Shape 'Hug' Mode Routing
 - Text Callouts
 - Layer & Via Stack Previews
 - Blind & Buried Via Support
 - Teardrop Pads
 - Draw Spacing Clearances
 - Spiral Tracks & Shapes
- Plus many more exciting features.....

Stop press... Stop press... Stop press... Stop press...
Easy-PC imports Eagle files as well as Tsien Boardmaker 2 files

call for a brochure, prices & CD on +44 (0)1684 773662
or e-mail sales@numberone.com
you can also download a demo from

www.numberone.com

Oak Lane, Bredon, Tewkesbury, Glos. GL20 7LR. United Kingdom



At FTDI, you'll find *more* than just our acclaimed range of USB Interface Chips...

We also have a wide range of competitively priced USB interface modules and cables ideal for implementing one-off designs through to full mass production runs.
Our on-line shop accepts payment by credit card - no minimum order restrictions apply

TTL-232R USB to TTL Serial I/F Cable

£11.10



- Easy solution for attaching 5v / 3.3v MCU to USB
- Fully 5v compatible I/O signal levels
- 3.3v I/O version also available
- TTL UART interface
- FTDI VCP or D2XX Drivers available
- 1.8m long 6 way cable
- 6 pin SIL pin socket (0.1in pitch)
- FT232RQ embedded into USB type "A" plug
- Data transfer rates from 300 baud to 3M baud
- Optional RTS/CTS or X-ON/X-OFF handshaking

MM232R Miniature USB Module

£10.00



- Micro Miniature USB Module
- FT232RQ USB UART
- 0.1in Pitch Pinout
- TXD, RXD, RTS#, CTS# UART Interface Pins
- Communication from 300 baud to 3M baud
- Four configurable GPIO Pins
- USB Self / Bus powered options
- 3.3v / 5v I/O signal level options

UM232R / UM245R DIL Modules

£11.10



- 24 Pin DIL format USB Modules
- FT232RL USB UART (UM232R)
- FT245RL USB FIFO (UM245R)
- Turned pins fit standard 24 pin i.c. socket
- USB Self / Bus powered options
- 3.3v / 5v I/O signal level options
- Full set of UART Interface Pins (UM232R)
- All multi-function CBUS GPIO Pins available (UM232R)
- Power Enable control available (UM245R)

DLP-RFID1 USB - RFID Reader / Writer

£79.50



A low-cost, USB-powered module for reading and writing ISO 15693, ISO 18000-3, and Tag-it™ passive RFID transponder tags.

- read and write up to 256 bytes of data
- read the unique identifier (UID).
- Internal antenna inside the unit
- Unit size 3.25" x 2.3" x .83"
- Operating range from 2-6 inches depending upon the size of the transponder tag.

DLP-D USB Security Dongle

£6.99



- Protect your application software with this low cost USB software security dongle
- ChipID Feature returns unique number for every dongle
- User EEPROM area allows storage of customer information and validation data
- Devise your own encryption scheme
- Basic demo software in VB and VC++ included
- Optional Software Guardian application software bundle available

US232R-10 Premium USB - RS232 Cable

£12.50

10cm version



Looks great and works great with MAC platforms as well as PC.

- High tech white gloss enclosure
- Blue side-lit LED TX and RX traffic indicators
- Gold Plated USB and DB9 connectors
- Supplied in retail packaging with driver CD
- Communication rates from 300 baud to 1M baud
- 10cm cable length (1m version available at £14,50)

DLP-Tilt USB Accelerometer Module

£27.80



The DLP-TILT USB-to-accelerometer module has four primary application areas:

- vibration analysis
- tilt sensing
- AC signal analysis
- two-button mouse pointing device alternative
- demonstration software provided using FTDI's Virtual COM Port (VCP) drivers

UC232R-10 Economy USB RS232 Cable

£10.50

10cm version



- Matt finish, nicely sculpted white plastic enclosure
- Supplied loose packed in an anti-static bag
- Wide range of drivers downloadable from FTDI web site
- Communication rates from 300 baud to 230k baud
- 10cm cable length (1m available to special request only)

Future Technology Devices Intl. Ltd
373 Scotland Street
Glasgow G5 8QB
Tel : 0141 429 2777
E-Mail : chipshop@ftdichip.com
Web : www.ftdichip.com

Volume Discounts Available



** Prices shown exclude shipping & VAT

Over 50 different USB Interface products in stock at www.ftdichip.com/shop.htm

RFID Chips Greet t



An employee of the Metro trading firm pulls a pallet of diapers through an RFID reader gate, which rapidly reads the data from the chips. The antennas of the RFID reader are located to the left and right (visible on the right side). (photos: Philips)

Renke Bienert

RFID labels can be used to mark racing horses as well as containers, scooters and perfume packages. Passports and sporting-event tickets can also be fitted with RFID chips. The underlying technology is just as varied as the potential applications.

Inanimate objects, as well as animals and in principle people, can be identified automatically without direct contact if they are fitted with small radio-frequency identification (RFID) responders. This technology is poised for a breakthrough this year in many sectors. In the near future, RFID labels will be so cheap that they can be used to mark even relatively low-priced goods.

The route taken by every milk jug, aspirin package or newspaper from production to selling (and possibly even further) could then be tracked electronically. Logistics specialists welcome the new technology because it promises to yield considerable cost and time savings in transport and storage, but many consumer associations and more than a few champions of privacy are worried about the potential for 'transparent customers'.

Curse or blessing?

The mood among the general public is equally contradictory, as was already shown by our brief international RFID survey on the *Elektor Electronics* website. For instance, 80% of the participating readers assumed that RFID tags will make their everyday lives easier, but an equally large percentage thought that personal privacy and data protection are 'threatened'. Perhaps the high level of insecurity arises from the fact that radio-based identification cannot be seen or heard, just like 'electromog'. The possibility that an RFID responder that you

may be carrying, whether or not you are aware of it, could be read out by a government authority, a company or an avid hacker is thus a fear that must be confronted by the manufacturers of this technology. This fear is also fed by horror stories, such as the story that a security company ordered its employees to have RFID chips implanted under their skin.

However, as with nearly all innovations the entire technology should not be condemned based on a few particular applications. Besides that, there is certainly more than one form of RFID. Consequently, the simultaneous appearance of media reports on RFID viruses and 2006 World Cup tickets or passports fitted with RFID chips does not necessarily mean malicious programs will spread via your passport or admission ticket that in the future (see also the web links at the end of this article).

RFID in a nutshell

First, a brief explanation of the terminology: the 'RF' in 'RFID' stands for using radio frequencies to transmit data and possibly also energy. The term 'ID' can refer to a variety of applications, ranging from simply reading numbers to encrypted data exchange or complicated computations for verifying the authenticity of an identification document. A RFID system normally consists of a transceiver (or 'reader') and a number of RFID responders, which are sometimes called 'tags', 'transponders' (a

The Future

A brief overview of RFID devices

wrong use of the term) or simply 'cards'. It's also necessary to make a distinction between active and passive responders. Active responders are powered by batteries, while passive responders take their operating power from the field emitted by the transceiver. Here we limit our attention to passive responders, because they are smaller and cheaper than active responders and thus far more significant for everyday applications.

Coupling methods

Three different types of coupling can be used for data transmission between the responder and the reader: capacitive, inductive, and electromagnetic, with the latter being important at relatively high frequencies.

Capacitive coupling employs the electrical field and is limited to a small transfer range. It is thus rather insignificant in practice. Inductive coupling uses a magnetic field to transfer energy and data, with a coil being used as an antenna (Figure 1). Systems operating at 125 or 135 kHz, as well as at 13.56 MHz, are in widespread use. The choice of these specific frequencies has nothing to do with the technology, but is instead based on legislation that makes these frequencies available for RFID applications. Applications using inductive coupling are already quite common.

At high frequencies such as 434 MHz, 862–956 MHz and 2.45 GHz, the coupling is no longer purely inductive or capacitive because the wavelength is small relative to the size of the components. In this case, propagation of electromagnetic fields through space is used to transmit energy and data.

Tagging

A basic distinction is made between 'object-related' and 'personal' applications. In the former case, the responder takes the form of a label attached to an object (see **Figures 2 and 3**). Such responders attached to goods are often called RFID tags or RFID labels.

Logistics specialists may want to know when an object is at a certain location. Using RFID tags, data for all delivered pallets and cartons can be acquired automatically when the goods are delivered. That makes it easier to keep track of inventory, helps reduce shrinkage due to theft, and facilitates distinguishing genuine goods from counterfeits.

The largest possible reading range and easy operation are important factors in such applications. They do not require complex computational operations in the RFID tags or large data volumes, but they do require large numbers of tags to be read quasi-concurrently. Reading several hundred or even a thousand tags per second at a range of tens of centimetres to a few metres (extending to more than 5 m) is readily possible. That is offset by small data volumes (several bytes) and a

data rate of a few kilobits per second. The tag usually holds only a number that can be linked to product characteristics in a database. In many cases, the database can be accessed via the Internet, which means it can be consulted from Beijing just as easily as from San Francisco. The new Electronic Product Code (EPC) standard

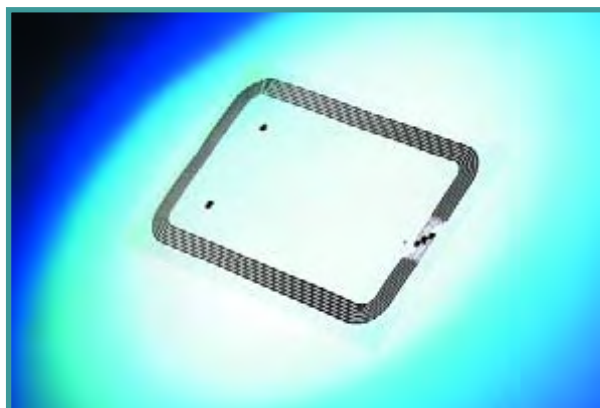


Figure 1. RFID label with antenna and chip.



Figure 2. Label inlays on a roll. An inlay consists of a chip, an antenna coil and a substrate (paper or film).

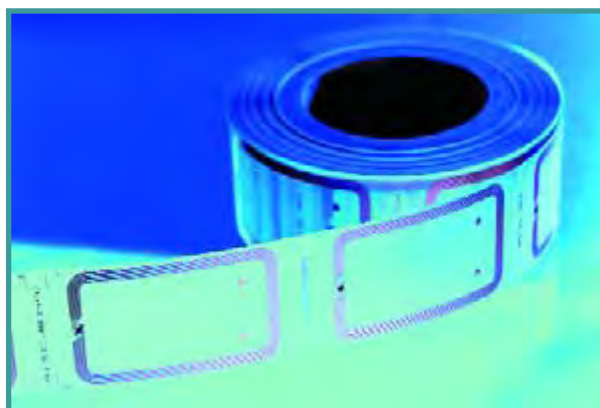


Figure 3. Manufacturing RFID labels. If you look closely at the bottom surface behind the roll, you can see the antenna coils shining through the base layer.

Frequencies for RFID tags

	100 – 150 kHz	13.56 MHz	UHF	2.45 GHz
Influence of water and humidity	Low	Low	High	Very high
Influence of metals	Low	High	High*	High*
Responder design	Simple	Simple	Complex	Very complex
Range	Short	Medium	Large	Large
Number of readable responders	Small	Large	Large	Large

* This can be minimised with a suitable tag design.

Contactless interface as specified by ISO/IEC 14443

Analogue portion

Mifare technology uses a contactless interface that complies with the ISO/IEC 14443 standard. A carrier frequency of 13.56 MHz is used for energy transfer and data transfer between the reader and the card. The read/write range is limited to a distance of less than 10 cm.

As shown in the illustration, the contactless interface can be explained in simplified terms using the operating principle of a transformer. The antenna coil of the reader generates an alternating magnetic field at 13.56 MHz. In simplified terms, the reader antenna can be regarded as the primary winding of a loosely coupled transformer. The card antenna acts as a secondary winding that picks up part of the generated magnetic field. This provides the card chip with the necessary energy. (The terms 'PCD' and 'PICC' used in the figure come from the ISO standard and are explained in the glossary.)

The magnetic field is amplitude modulated by the reader to transfer data from the reader to the card, in this case using a Miller-coded data stream and binary 100% modulation in accordance with ISO/IEC 14443A.

Load modulation is used to transfer data in the opposite direction (from the card back to the reader). This means the card uses the modulating data signal to switch a load in or out. The variations in the load on the 'secondary' side of the transformer are detected by the reader on the 'primary' side.

The data rate is 106 kbit/s in both directions (optionally as high as 847.5 kbit/s). The

energy provided by the reader is sufficient to operate a microcontroller.

As it is basically impossible to say in advance whether more than one card is within the operating range of the reader, card selection must occur before the actual communication session in order to ensure that only one card is addressed (collision protection).

Digital portion


Data (including user data) can be transferred after the card has been selected. The following rules apply:

- 'Reader talks first': the transceiver always transmits first and the card replies.
- The card always replies within an agreed time, while the transceiver can take its time.

In the simplest case (as with the Mifare Ultralight card used in our RFID reader project), this is accomplished by direct use of suitable card commands ('Read' and 'Write' in the case of the Mifare Ultralight card). This means there is only a simple, rigid protocol, and errors cause termination of the communication session.

This is naturally impractical for relatively complex applications, so there is also a flexible transmission protocol for microcontroller smart cards. It is specified in Part 4 of the ISO/IEC 14443 standard. This protocol:

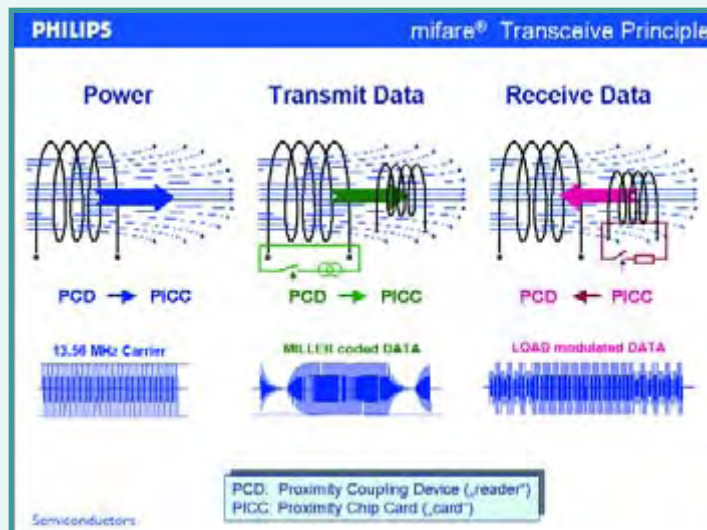- allows different sizes of data blocks (depending on the buffer size of the card or reader)
- defines an error handling procedure (error detection and correction)
- permits chaining of data blocks to transfer relatively large data volumes
- supports flexible timing (which means the card can request extra time for execution of a command)



guarantees internationally unique product numbers, which represent a sort of electronic barcode.

Smart cards

'Personal' responders impose different technical requirements. In this case the responders are generally referred to as 'smart cards' instead of 'tags'. With a smart card, the user must always actively initiate a read/write process by bringing the card close to a transceiver. A large operating range is not only unnecessary in this case, it is also undesirable. Unauthorised reading of the data can be prevented by design by keeping the operating range as small as possible. The standardized interface for contactless smart cards (ISO/IEC 14443) thus defines the technical parameters such that the maximum possible range is limited to 10 cm (see inset). However, it may be necessary to exchange relatively large amounts of data in this case (up to several kilobytes), and suitable data security is naturally required as well. The contactless interface is designed to supply energy to suitable microcontrollers embedded in smart cards and transfer relative large data volumes at rates up to several hundred kilobits per second. Sample applications include the new electronic passport (see the web links) and electronic tickets for local public transport systems, like Oyster on the London Underground.

Which frequency for what?

Contactless smart cards generally operate at 13.56 MHz and typically employ the ISO/IEC 14443 standard (see inset). The Mifare technology described in the RFID reader project in this issue is the most widely used technology worldwide for smart card RFID applications. Selecting the right frequency is more complicated for tagging applications. As indicated in the table, various factors come into play at different frequencies. The influence of water is negligible at very low frequencies, but it increases at high frequencies. As water absorbs a lot of energy at 2.45 GHz, for example, it is better to choose 135 kHz for systems that must work under conditions of high relative humidity. In a metallic environment, such as with an RFID tag on a beer keg, it is better to select a low frequency or design a UHF tag with a suitable antenna. Antenna design for tags that use inductive coupling is easier than for high-frequency tags. On the other hand, UHF tags have a larger theoretical range, which is essentially limited only by statutory provisions. Naturally, the number of tags that can be read per second is higher at relatively high frequencies due to the greater available bandwidth.

Security

System security and data security must be given adequate attention before the system is put into service. Of course, the requirements depend on the specific application. In a system with object-related RFID tags, which in the simplest case only replace barcode labels, it is basically not necessary to have any more security than when barcodes are used (but also no less!). The data is stored in compliance with a standard and can be write-protected. However, everyone who has access to the tag can read and copy the stored data, just as with a barcode. In contrast to barcode systems, it is relatively easy to increase the functionality and security of RFID tags. The first step is to protect the data against copying. One way

Preventing replay

A typical application for contactless smart cards is an access control system, such as for a company. Every employee with access authorisation carries a badge containing a smart card. The employee holds the card in front of a reader before entering a secure area. That causes access to be granted or the door to open automatically.

Of course, the authorisation data is transmitted between the card and the reader in encrypted form. However, a 'session key' is needed to prevent an attacker from recording the transmitted data and then simply using it again (a 'replay attack').

In the '3-pass mutual authorisation' method, the correctness of the secret key is verified and a session key is generated. This works as follows:

- 1) The card generates a random number RndB, which is encrypted using a secret key and then sent to the reader.
- 2) Decryption in the reader then yields the same random number RndB if the reader uses the same secret key. The decrypted number is permuted to form the number RndB*. The two numbers RndB* and RndA are then encrypted and sent back to the card.
- 3) The card recovers the two received random numbers by decryption and reverses the permutation of RndB*. If the result is the same as the number RndB previously generated by the card, the keys used by the card and the reader must be the same. In this way, the card recognises that the reader is authentic. The card then permutes RndA to generate RndA*, encrypts RndA*, and sends this number back to the reader.
- 4) Now the reader can decrypt RndA* and convert it back to RndA to test the correctness of the key that was used. If the test is successful, the reader has recognised that the card is genuine.

After this authentication both sides know that they are using the same key, even though the key never left the card or the reader. A temporary session key can now be generated from the random numbers, which are known only to the reader and the card because they were transmitted in encrypted form. The session key is then used for data encryption during the rest of the communication session. The advantage of such a session key is that it is based on random numbers, which means a new key is used in each session. That effectively defends against replay attacks.

to do this is to assign each RFID tag a unique identification number (UID). The UID is stored in unalterable form in the memory of the RFID by the chip manufacturer and thus provides a basic form of protection against copying.

Secret keys

The next step is to use this method to protect writeable (or rewriteable) memory areas against misuse. Here the UID

Web links

RFID card applications everywhere in the world:

www.mifare.net/news/#press

World Cup ticket with RFID chips:

www.ektor-electronics.co.uk/Default.aspx?tabid=27&art=53048&PN=On

Technical details of electronic passports:

www.ektor-electronics.co.uk/Default.aspx?tabid=27&art=53049&PN=On

RFID viruses:

www.ektor-electronics.co.uk/Default.aspx?tabid=27&art=53050&PN=On

Explanation of DES and Triple DES:

en.wikipedia.org/wiki/Triple_DES



Figure 4.
The advantages of RFID technology come to the fore with perishable goods, since it saves time in transport.

is used to generate a chip-specific secret key that is used to encrypt the data. The user requires the following to evaluate the data stored in such a tag:

- the UID
 - a secret key
 - knowledge of the encryption method that is used
- Other ways to protect data include password functions and true encryption processes in the tag to encrypt the transmitted data as well. Although many things are tech-

nically possible, complex methods are usually not used in simple systems for cost reasons.

Data safe

Smart cards typically require a relatively high level of security because personal data (such as with a passport) or relatively large monetary values (such as with an electronic ticket) are often stored in them. The same security requirements can fundamentally be fulfilled with contactless smart cards as with contact cards.

Naturally, the first step is to encrypt the transmitted data. There are various standards for this purpose, with the degree of security typically being stated in the form of the length of the key. In simplified terms, the length of the key corresponds to the statistical number of incorrect attempts to guess an unknown key. In the case of a DES algorithm with an 8-byte key, of which only 56 bits are actually used for the key, the single correct key must be found from among 72,000,000 billion possible keys.

This sounds like a very large number, but in an era of networked computers there are many applications for which it does not provide adequate security. One option is to use a longer key, such as 112 bits with Triple DES, or a different encryption method.

Here again, effort and cost must be weighed against the required security, and for that reason many different concepts are available. However, the security of a system consisting of several components is only as good as the security of the weakest link in the system. There is thus little point in encrypting the data in the card if it is possible to eavesdrop on a communication session and then simulate a new session. However, effective methods for protecting against this form of attack and several other forms of attack are available (see the 'Replay' inset).

(060204-1)

RFID glossary

Tagging	Capturing tags (including RFID tags)	UHF	Ultra High Frequency; in this case frequencies in the 862–956 kHz band
ISO	International Organization for Standardization	Eavesdropping	Undesirable listening in on RFID communications
IEC	International Electrotechnical Commission	Skimming	Undesirable use of an RFID label or contactless smart card
ISO/IEC 14443	International standard for a contactless smart card interface with a maximum range of 10 cm and an operating frequency of 13.56 MHz	Replay attack	An unauthorised transaction generated by repeating a previous transmission obtained by eavesdropping
PCD	Proximity Coupling Device: a transceiver for contactless smart cards (complaint with ISO/IEC 14443)	Modified Miller coding	Pulse position coding scheme in which specific pulses are omitted to save energy
PICC	Proximity Chip Card: a contactless smart card (complaint with ISO/IEC 14443)	DES	Data Encryption Standard: a symmetric encryption method for 8-byte data blocks with a key length of 56 bits (8 bytes without parity bits). See the web links.
ISO/IEC 15693	International standard for a contactless label interface with a maximum range of 1.5 m at 13.56 MHz	3-DES, Triple DES	A standardized encryption method consisting of three DES loops for increased security, with a key length of 112 bits or 168 bits (see web links)
ISO/IEC 18000-6	International standard for a contactless label interface with a maximum range of 3–7 m, operating in the UHF band and/or at 2.45 GHz		

Lichfield Electronics


The Corn Exchange, Conduit St. Lichfield, Staffs. WS13 6JU
Tel: 01543 256684 E-Mail: sales@lichfieldelectronics.co.uk

LED Flashing Kits

Arrow Chasing Light 21 LED

A simple but fun kit to build an LED pointing Arrow, ideal for near exits or as an indicator?
£9.99 2.9"x2.2", 9-12V

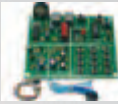6 program 4 channel DC chasing light. 12V 100W. (FK144) **£15.99**
Electronic Windmill 25 LED, adjustable speed. (FK153) **£9.99**
4 way traffic light. 12 LED. How do they work? (FK148) **£9.99**
Two Way Chasing Light 35 dot. Uses LED display. (FK151) **£7.99**
240V flasher. 2CH 1400W, adjustable speed. (FK144) **£7.99**
Two way V.U. Meter. 10 LED. Displays volume (FK102) **£4.99**



Telephone kits

Build Your Own Telephone

This great kit lets you build a tone/pulse phone With mic and ear piece, no batteries required.
£28.99 A great kit to build and use.

Telephone In Use indicator. Requires phone lead (FK318) **£2.99**
Telephone Interceptor: Listen in on phone calls. (FK306) **£8.99**
Telephone Radio Transmitter (FM 88-108 Mhz) (FK320) **£8.99**
10W Telephone Ringer, drives bell or speaker not inc(FK305)**£9.99**
Phone Ring Signal 500W Flash a lamp when the phone rings**£12.99**
Dual Station Intercom with speakers (FK313) **£10.99**



Switch and control kits

Infrared Remote Relay

Control 1 10A Mains device by infrared Remote control. Range: 25ft. (on/off)
£18.99 2ch 50ft version also available

Light Dimmer 500W: uses a Triac. With LED (FK415) **£5.99**
Light Sensor with 5A 250V relay. With LED (21-053) **£6.99**
Touch Switch 10A 240V Touch on/touch off (FK405) **£8.99**
Voice control switch 7A 240V, clap on/clap off (FK409) **£9.99**
Water Pump Level Control with 7A 240V relay. (FK425) **£9.99**
Electronic Code Switch & relay. 7A 240V 4 digit. (FK422) **£14.99**

Postage

Order Value	P&P Cost
£4.99-12.99	£2.00
£13.00-22.99	£3.00
£23.00-49.99	£8.00
£50-£150	£10.00

Above prices UK Only.
Phone or e-mail for Ireland.
Payment by cheque, card or P/O

Power Supply kits

0-30V 3A Variable Regulator

Build a high quality variable voltage regulator Using this simple to assemble kit.
£15.99 30VDC or 2x12VAC required



0-30V 1A Variable Regulator, as above but 1A. (FK808) **£7.99**
Variable DC Regulator 0-12V from 12V. 500mA. (FK807) **£4.99**
DC Down Converter. 12v to 6 or 9V. Uses 7806 (FK805) **£3.99**
Power Supply 6-9-12V 0.3A. Inc transformer (FK801) **£8.99**
Mini Emergency Light. When mains fails, it lights(FK802) **£5.99**
12V Low battery alarm. Suit car or boat. (FK915) **£6.99**

Power Amplifier Kits

15+15W Power Amp

This quality kit uses 2X TDA200SR IC's, Includes heat syncs and full instructions.
£24.99 Requires only a 12V power source.



Power Amp. OTL. 30W Mono R1%: Req 50VDC (FK656) **£14.99**
Power Amp. BTL. 15W Mono. Req 12VDC (FK607) **£14.99**
Power Amp. IC 8+8W Stereo. 12VDC TDA200SR (FK605) **£13.99**
Power Amp. IC 8W Mono. 12VDC TDA2030 (FK604) **£8.99**
Power Amp. 2+2W Stereo 3-12V DC TBA820M (FK603) **£9.99**
Power Amp 2W Mono 3-12V DC TBA820M (FK602) **£5.99**



Our Shop

Located in the city centre of Lichfield We are within easy reach from Birmingham. All stock is carried on site and is on display. If you have any questions our staff would be happy to help.

Open Mon-Tue & Thur-Sat: 9:15-5:00
Closed Wed & Sunday

133 Kits in stock!!!

Intruder Alarms

Magnetic Switch Alarm

Make a digital burglar alarm with this great Kit, simply attach the magnet to a door and the switch to the surround, hide the control board, arm it and wait.
£16.99



Passive Infrared Sensor & relay 5A 250V delay off (FK510) **£27.99**
Infrared Burglar Alarm/relay. Make an IR tripwire. (FK505) **£24.99**
Intruder Alarm with delay function & speaker. (FK501) **£9.99**
Visitor Chime with speaker. Ding Dong. Req switch (FK502) **£7.99**

Radio kits

Shortwave Radio Receiver

A great kit to make a short wave receiver for 2.2 - 7Mhz. Easy to build. Uses the 4007 IC.
£9.99 9V (21-020)



Walky Talky Kit, pair. 27Mhz. 150mW to 1W (FK711) **£34.99**
Advanced AM/FM Radio & case. Req Freq Gen (21-027A) **£16.99**
Simple FM Radio 88-108Mhz. Uses TDA7000 (FK707) **£14.99**
Advanced AM Radio & case. Req freq generator (21-028A) **£13.99**
FM Wireless Mic: Very simple transmitter. 9V (FK702) **£6.99**
Pocket Transistor Radio: Uses MK484 clone IC (21-001) **£9.99**

Everything Else

Aoyue 909 Hot air gun, soldering iron & 0-15V PSU. **£99.99**
Aoyue 850C Hot Air Rework station for SMD Components **£54.99**
Aoyue 936 Temp controlled soldering iron with stand. **£24.99**
DIY Digital Multimeter: with transistor checker. (03-150K) **£16.99**
Stereo Simulator: Splits source based on frequency. (FK651) **£14.99**
Video Amplifier 1 to 4 ch. Adjustable gain. 12V (FK655) **£12.99**
Human to Robot Voice Changer with speaker. (FK930) **£12.99**
Rat and Cockroach Banisher circuit with speaker (FK929) **£8.99**
Bass Booster. Mono.(Audio) 12V DC (FK642) **£6.99**
Electric Shock Machine. Low Power. 9V (FK901) **£5.99**
Two tone door bell with speaker. (FK238) **£5.99**
Police Siren with speaker. (FK234) **£5.99**

And this is only 59 of our kits



See the web site for the rest>>>

WWW.LICHFIELDELECTRONICS.CO.UK

PicoScope 3000 Series PC Oscilloscopes

The PicoScope 3000 series oscilloscopes are the latest offerings from the market leader in PC oscilloscopes combining high bandwidths with large buffer memories. Using the latest advances in electronics, the oscilloscopes connect to the USB port of any modern PC, making full use of the PCs' processing capabilities, large screens and familiar graphical user interfaces.

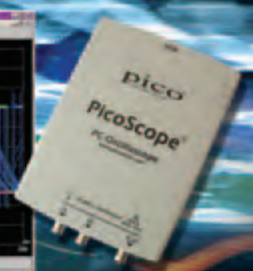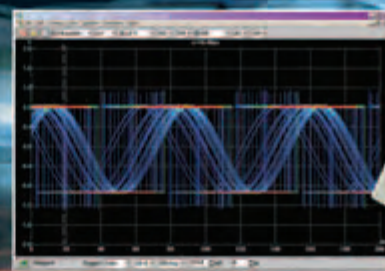- High performance: 10GS/s sampling rate & 200MHz bandwidth
- 1MB buffer memory
- High speed USB 2.0 interface
- Advanced display & trigger modes
- Compact & portable
- Supplied with PicoScope & PicoLog software



PicoScope	3204	3205	3206
Bandwidth	50MHz	100MHz	200MHz
Sampling rate (repetitive)	2.5GS/s	5GS/s	10GS/s
Sampling rate (single shot)	50MS/s	100MS/s	200MS/s
Channels	2+Ext trigger	2+Ext trigger/Sig gen	2+Ext trigger/Sig gen
Oscilloscope timebases	5ns/div to 50ns/div	2ns/div to 50ns/div	1ns/div to 50ns/div
Timebase accuracy	50ppm	50ppm	50ppm
Spectrum ranges	0 to 25MHz	0 to 50MHz	0 to 100MHz
Buffer memory size	250KB	512KB	1MB
Resolution / accuracy	8 bits / 3%		
Range	±100mV to ±20V		
PC Connection	USB 2.0 (USB 1.1 compatible)		

Tel: 01480 396395

www.picotech.com/scope353

pico
Technology Limited

RFID Card Quest



Does your free RFID card win a prize?

This issue of Elektor Electronics magazine comes with a free RFID card. With a little luck, your card contains a number that links it to a fantastic prize!

Elektor Electronics magazine, Philips, distributor ACG and card manufacturer VisionCard come up with the goods — a free credit-card sized active RFID card is secured to the front cover of this magazine. Inside the flat plastic card hides an electronic circuit consisting of a printed antenna and an integrated circuit. Each Philips 'MIFARE Ultralight' IC contains a unique sequence of 14 hexadecimal numbers (7 bytes), which are read-only, i.e. cannot be changed (see 'The Elektor RFID Card' on page 22).

The UID number may win a prize if you are able to read it. Among the prizes we've gathered for our RFID Card Quest are a plasma TV set and a versatile DVD recorder.

Read the card and win

So there's the excitement and tension — all you have to do now is participate in the quest. Simply read the number stored on your card using an RFID reader unit. You may want to build one yourself, see the design on page 26. Alternatively, get in touch with a fellow *Elektor* reader and use his/her Card Reader. Additional information concerning our RFID Card Quest will appear soon on the Internet at www.elektor.com/rfid. The winning hex numbers need to be completed, however, by **an extra number** which is easily found by answering the following question: *how many turns does the antenna coil on the RFID card consist of?* (no need to cut open your RFID card — just carefully browse the pages of this magazine...)

If you can prove you have an RFID card linked to a prize, please send us a letter (not an email) stating the prize-

winning hexadecimal number sequence and the extra number. Our address is found in the colophon on page 6. The card is returned to you together with the prize.

More prizes waiting at 'electronica 2006'

There are even more prizes than the ones shown on these pages — our RFID Reader offering yet another chance to win! Bring your card to the 'Electronica' exhibition held in Munich, Germany, between 14 and 17 November 2006 and visit the Elektor booth no. A5.531 in Hall A5.

Conditions for participation

The closing date for reporting winning cards by post is **10 November 2006**. The competition is not open to employees of Segment b.v., its business partners and/or associated publishing houses. A prize can only be claimed if the associated card UID can be read and verified on the RFID Reader used by Elektor editorial staff. Legal procedures barred.

Errors and omissions excluded.

(060205-1)

Special service from Elektor Electronics

An extra service is offered to those of you not capable of reading their own card or using a fellow reader's card reader. Send your RFID card in a closed, properly sealed envelope to: *Elektor Electronics RFID Quest, Regus Brentford, 1000 Great West Road, Brentford TW8 9HH, England*. Elektor Electronics staff will read the code on your card enabling you to participate in the RFID Card Quest and qualify for a prize. However, you only participate if you answer the extra question (number of turns of the antenna coil on the RFID card). Write the answer, together with your email address, **on the back of the envelope**. Envelopes are **not opened** by Elektor Electronics staff (wireless reading is employed). You will receive a return email from us if your card contains a winning number. Unfortunately we are unable to return cards checked using our reader.

1st Prize:



A Philips 42-inch Plasma Widescreen TV set worth £1550!

This TV offers the latest display technology for razor-sharp images and brilliant colours, not forgetting 2x15 watts of audio power and of course HD-ready! The main prize is sponsored by leading postal services supplier DHL Global Mail who look after the mail distribution of our magazine to all subscribers within Europe. Winning number: 04C5F259EE0280 (plus extra number)

2nd Prize: A Mio C170 Navigation System worth £345.



The C170 comes with full European coverage (24 countries) and features integrated Bluetooth handsfree communication, an MP3 player and a photo viewer. Prize sponsored by Conrad Electronics Netherlands (conrad.nl).

Winning number: 04B71559EE0280 (plus extra number)

8th and 9th Prize: A VMD HD player worth £110.



Get access to the newest technology beyond the DVD! This unit not only plays all known CD and DVD formats, but also the latest 'VMD' discs (versatile multilayer disc), offering a capacity of 20-100 gigabytes. Prize sponsored by NME (New Medium Enterprises).

Winning numbers: 047B5361EE0280 and 04DC4159EE0280 (both plus extra number)

3rd Prize: A Liteon LW5045 GDL DVD Recorder worth £245.

Show-view-driven recording on a 160-

gigabyte hard disk; disk burning and playback of all current DVD standards. Prize sponsored by Conrad Electronics Netherlands (conrad.nl).

Winning number: 0498F361EE0280 (plus extra number)



10th to 13th Prize: An E-blocks Starter Kit Basic from Matrix Multimedia, worth £96.

The price-conscious gateway to E-blocks technology using an USB Multiprogrammer (with PIC16F877) and Flowcode Home Edition.

Winning numbers: 0407A459EE0280, 04B96129EE0280, 04C34A29EE0280 and 04FDAC61EE0280 (all plus extra number)



4th to 7th Prize: E-blocks Starter kit Professional from Matrix Multimedia, worth £166.



The ideal way to step into E-blocks technology using the main modules and the graphics-oriented Flowcode Professional software.

Winning numbers: 0445F961EE0280, 047BF159EE0280,

04945A29EE0280 and 04EE4761EE0280 (all plus extra number)

14th and 15th Prize: A Parallax RFID Starter Kit.



The kit contains the well-established 'Board of Education' (Full Kit version) together with an RFID reader for 125-kHz tags, a mains power supply, two round and two rectangular tags.

Prize sponsored by Antratek (www.antratek.nl) Winning numbers: 04B77359EE0280 and 04BE9929EE0280 (both plus extra number)

The Elektor Electronics

Contactless transaction card using MIFARE® Ultralight IC

By Gerhard H. Schalk

The free 13.56MHz RFID smart card given away with this issue is designed around the Mifare Ultralight IC (MFO IC 01), the smallest member of the Mifare product family from Philips Semiconductors. Key applications of this IC are public transport passes, loyalty cards and entry tickets for special events. Its advantages over older technologies (such as magnetic stripe cards) are greater user-friendliness, increased security, shorter transaction time, lower maintenance costs and fewer terminal equipment errors.



The heart of the RFID smart card is a silicon chip that is thin enough to be embedded inside a piece of plastic or paper. Once encapsulated in a usable form it is known as a 'module'. Even the smallest member of the Mifare family provides comprehensive functionality, as the block diagram in **Figure 1** shows. The Mifare Ultralight Card IC comprises a 512-bit EEPROM read/write memory, an RF interface and control logic with command interpreter

and anti-collision logic. The article on the *Elektor Electronics* RFID Reader elsewhere in this issue gives information on building a contactless interface for connecting to the reader unit.

Memory layout

Figure 2 shows the memory diagram of the 512-bit EEPROM read/write memory, which is organised in 16 pages of four bytes each. Each card has its own unique 7-byte serial number (the UID or Unique Identification Number), programmed by the chip manufacturer into pages 0 and 1. Philips guarantees that this number will never occur more than once worldwide. For security reasons this serial number is protected and cannot be altered by the user.

Page 3 is the 32-bit OTP (one-time programmable) area, where each individual bit can be programmed irreversibly from logic state 0 (preset at production stage) to a 1. This means the bits cannot be reset back to 0 afterwards. A sample use for the OTP area would be reducing the number of trips remaining on a multi-ride ticket by one after each journey.

Pages 4 to 15 constitute the 384-bit application data memory, also preset to all zeros at the time of manufac-

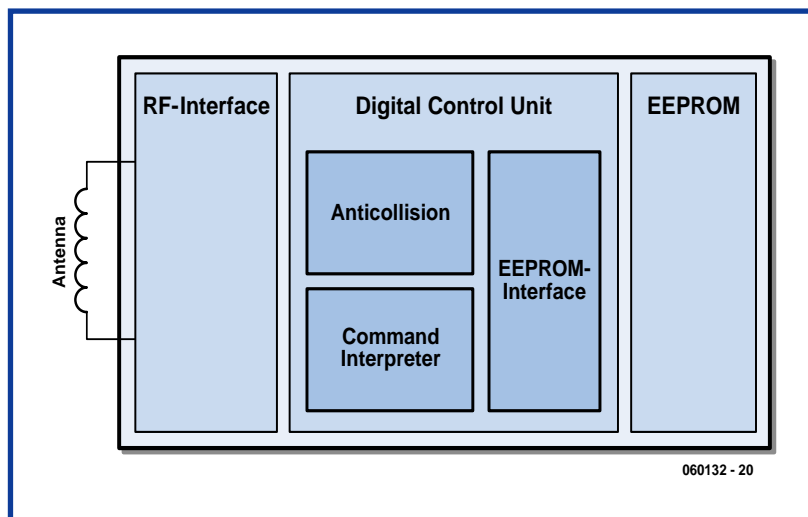


Figure 1. Block diagram of the Philips Mifare Ultralight RFID IC.

s RFID Card using the Philips



ture. This memory can be both read and written to by the reader. Two lock bytes, Lock0 and Lock1, enable individual pages of the application data memory and OTP Page to be frozen, with the data still readable but no longer capable of alteration.

Command set and card activation

The command set of the Mifare Ultralight card is fully compatible with standard Mifare cards; the latter, however, are equipped with larger EEPROM memories (1 kByte or 4 kBytes) and additional crypto functionality. For this reason standard Mifare cards employ extra instructions for card authentication and special commands for EEPROM memory operations.

Fundamentally the command set of Mifare cards divides into two groups, commands for activating the card and commands for memory manipulation (see inset). The process of card activation follows the ISO 14443-3 standard. When a compatible card comes within range of the reader unit, the first task is to establish communication between the card and the reader. During the process the command set takes regard of the fact that more than one card may be in range of the reader simultaneously or

Figure 2. Layout of the EEPROM memory in the Mifare Ultralight IC.

Characteristics of the Mifare Ultralight IC

- 100% MIFARE compatible
- Supports anti-collisions process specified in ISO/IEC standard 14443-3 A
- Read/write range up to 10 cm
- 106 kbit/s data speed
- Each card chip has its own unique 7-byte serial number for anti-cloning support
- High data integrity: 16-bit CRC, parity, bit coding, bit counting
- 512-bit EEPROM, organised in 16 pages of 4 bytes each
- 32 bits user-definable OTP (one-time programmable) area
- 384 bits User Area (read/write memory)
- EEPROM READ-ONLY function programmable by the reader unit
- Supports DESFire SAM (Secure Access Module) security system

Command set of the Mifare Ultralight IC

For card activation (compatible with ISO/IEC Standard 14443-3A):

REQA
WUPA
ANTICOLLISION of Cascade Level1
SELECT of Cascade Level1
ANTICOLLISION of Cascade Level2
SELECT of Cascade Level2
HALT

For memory manipulation:

READ
WRITE
COMPATIBILITY WRITE

Byte Number	0	1	2	3	Page
Serial Number	SN0	SN1	SN2	BCC0	0
Serial Number	SN3	SN4	SN5	SN6	1
Internal / Lock	BCC1	Internal	Lock0	Lock1	2
OTP	OTP0	OTP1	OTP2	OTP3	3
Data Read/Write	Data0	Data1	Data2	Data3	4
Data Read/Write	Data4	Data5	Data6	Data7	5
Data Read/Write	Data8	Data9	Data10	Data11	6
Data Read/Write	Data12	Data13	Data14	Data15	7
Data Read/Write	Data16	Data17	Data18	Data19	8
Data Read/Write	Data20	Data21	Data22	Data23	9
Data Read/Write	Data24	Data25	Data26	Data27	10
Data Read/Write	Data28	Data29	Data30	Data31	11
Data Read/Write	Data32	Data33	Data34	Data35	12
Data Read/Write	Data36	Data37	Data38	Data39	13
Data Read/Write	Data40	Data41	Data42	Data43	14
Data Read/Write	Data44	Data45	Data46	Data47	15

060132 - 21

that communication may be in progress already with another card. As soon as a card has picked up sufficient energy from the RF field of the reader it assumes a quiet or idle state. In this condition the card will respond only to the commands REQA (Request) or WUPA (WakeUp), to avoid disturbing any communication between the reader and another card. A valid REQA or WUPA command causes the card to respond with the ATQA Block (Answer to Request) and enter the READY1 state. All the time that a reader unit has not received an ATQA Block it sends a REQA or WUPA command every 5 ms as it searches ('polls') for new cards in its reader field. When the reader picks up an ATQA Block, it

begins the anti-collision process by sending the first ANTI-COLLISION1 command, ensuring that each card within range of the reader is handled individually without data corruption for other transactions in progress. A more detailed description of this ingenious operation can be found in the Philips product description at http://www.semiconductors.philips.com/acrobat_download/other/identification/M028630.pdf. For further information on the Mifare RFID family visit the Philips website www.semiconductors.philips.com/products/identification/mifare/ and the open Mifare Forum <http://mifare.net>.

(060132-2)

RFID chip card with printed antenna


Up to now techniques used for implementing antennas on RFID chip cards have had serious shortcomings from a manufacturing point of view. The antennas themselves employ either wound or inlaid wires or else are etched in copper. Both processes impose limits on production throughput and require additional production equipment. Opportunities for cost reduction using this approach are difficult to find since the process itself is relatively static.



The RFID card given away with this issue of *Elektor Electronics* (who else?) is produced by German company ACG using an entirely new technology: the printed antenna. In this application the antenna layout is imprinted onto a PVC carrier film in a special silver paste, using standard screen-printing techniques. The special silver paste is a viscous (printable) base carrier containing metallic silver particles that remain conductive once the paste has solidified and allow electric currents to pass through this layer. A similar process is used in the automotive industry for applying electric heater elements onto rear window glass.

A patented technology enables the contacts and terminals to be connected to the chip module. The print layout of the antenna can be varied for each type of chip and module and is easily adapted. The only redesign necessary is to the silk-screen print material.

Contact is made to the chip module and the finalised card is laminated using holding strips and a plastic overlay foil.

The printed antenna offers many advantages. Speed of production is far higher than with wire-wound antennas. Several different printed antenna types can be manufactured simultaneously, raising production throughput significantly. Printed antennas also avoid the environmental disadvantages of etching with the variety of chemicals (some highly toxic) involved in that process. This new printing technology is still in its early stages of development and offers great potential for further optimisation and cost reduction. Crucial to this is the print materials used. Intensive research is already under way to substitute lower-cost copper particles for the expensive silver used at present. Printed antennas can be applied to all current modules in the 13.56-MHz arena. The RFID cards with printed antennas manufactured in-house by ACG are subjected to constant quality checks and production can be adapted very flexibly to end-users' requirements.

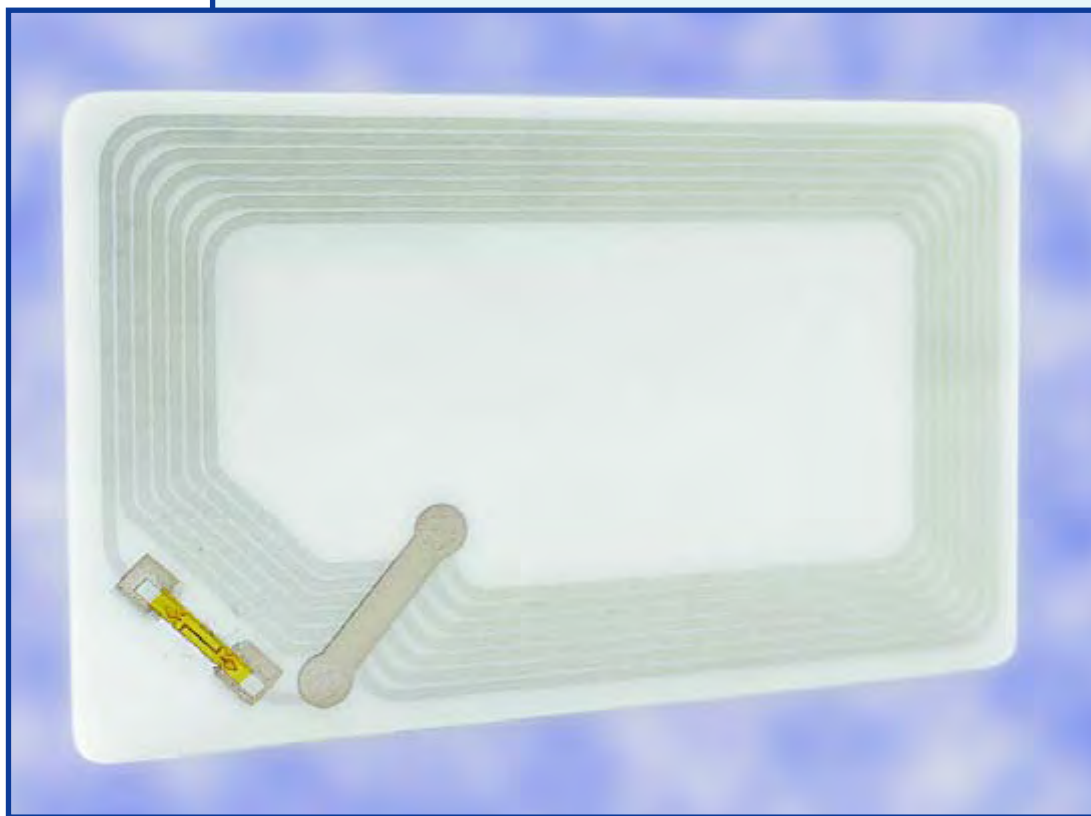

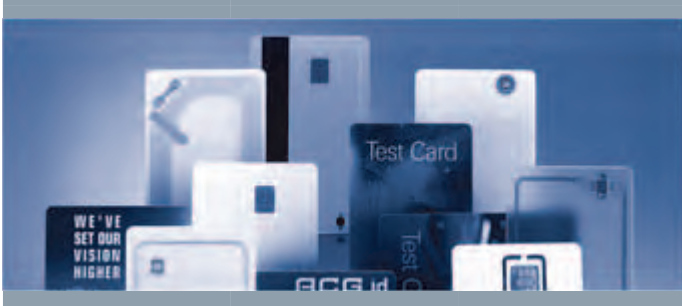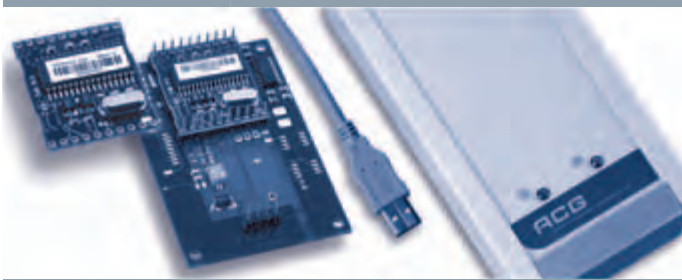

YOUR IDEAL IDENTIFICATION TECHNOLOGY PARTNER

- ▶ Reader ICs
- ▶ Reader Modules
- ▶ Desktop Readers
- ▶ Transponder ICs
- ▶ Smart Cards / Tickets & Transponders

Official Distribution Partner for Philips RFID Products

ACG

ACG Identification Technologies
 phone: +49 6123 791-0
 eMail: RFID@acg.de
 web: www.acg.de

ANDRE LAMOTHE'S
XGAMESTATION
 LEARN STEP-BY-STEP HOW TO BUILD
 AND DESIGN YOUR OWN VIDEO GAME CONSOLE!

Design inspired by the
 Atari 800/2800, Sinclair ZX Spectrum,
 Apple II & Commodore 64!

Parallel 52 Ray Compatible!

INCLUDES:

- Two, Games & Emulator
- Great for Prototype AND Students
- The Best Way to learn Embedded Systems
- Fully Assembled PCB (Price £1000) Build
- Complete Software Development Kit
- Attack on Designing the K05 Console
- Cables and Power Supply included!

WWW.XGAMESTATION.COM
 PH: 925.736-2098 | SUPPORT@NURVE.NET

NURVE NETWORKS LLC
 402 GARDEN AVENUE WEST
 DANVILLE, CA 94526 USA

**PCBs in
 24 hours
 from £30.00**

www.PCBTrain.com

Tel: 01635 40347 Newbury Electronics Ltd
 Fax: 01635 36143 Faraday Road Newbury Berks RG14 2AD
 e-mail: circuits@newbury.com.co.uk www.newburyelectronics.co.uk

NE
 Approvals: ISO 9002/1A

PCB-POOL®
 SERVICING YOUR COMPLETE PROTOTYPE NEEDS

1 EUROCARD
 (160 x 100 mm)
 + Tooling
 + Photoplots
 + VAT
€49

Price example
 Any size and contour possible!

Optional:

- Soldermask
- Fast-turnaround
- Silkscreen
- 4-Layer Multilayer
- 6-Layer Multilayer

**DOWNLOAD OUR
 FREE LAYOUT SOFTWARE!**

Freephone 0800-3898560
 Tel.: +353 (0)61 701170
 Fax: +353 (0)61 701165
 pcb-pool@beta-layout.com

Beta LAYOUT

Simply send your files
 and order **ONLINE:** **PCB-POOL.COM**

ELEKTOR RFID Reader

For MIFARE® and ISO 14443-A cards

Gerhard H. Schalk

RFID cards are becoming increasingly popular in many fields where previously barcodes and chip cards were used. They open up many new possibilities, such as applications in travel cards or even banknotes. As befits a premier electronics magazine, *Elektor Electronics* is offering its readers with this issue not only a free RFID card but also a professional RFID reader for your own applications. The design described here can both read from and write to all types of RFID card that are compatible with the MIFARE and ISO 14443-A international standards.

In developing the *Elektor Electronics* RFID reader we have aimed to make the device as universal as possible. So, for example, the reader can be used in

conjunction with a PC over a USB connection, or in stand-alone mode using its liquid crystal display. It is very simple to use the free PC-based program

'MIFARE Magic' to read and write all kinds of MIFARE cards without installing special software in the reader.



Specifications

Elektor Electronics RFID reader:

- Near-field reader for 13.56 MHz RFID cards
- Compatible with MIFARE and ISO 14443-A cards
- Allows both reading and writing
- USB interface for connection to PC
- Ready for immediate use without programming
- Free PC-based software available
- Stand-alone (including portable) operation using LCD module
- Dedicated MF RC522 reader IC
- Dedicated microcontroller on reader board
- SPI and I²C interfaces
- Spare 8-bit microcontroller port
- Buffered switching output

- Available as ready populated and tested SMD circuit board
- Can be modified for user applications
- Programming tools available

MF RC522 reader IC:

- Highly-integrated single-chip reader for ISO 14443-A and MIFARE cards
- Supports contactless data transmission at 106 kbit/s, 212 kbit/s and 424 kbit/s
- 50 mm approx. read/write range (depending on antenna)
- Integrated MIFARE Classic cryptography
- Programmable over UART, I²C or SPI
- 64 byte transmit and receive FIFO buffer
- Programmable reset and power-down modes
- Programmable timer
- Internal oscillator allows direct connection of 27.12 MHz crystal

MIFARE Magic directly supports a range of contactless 13.56 MHz MIFARE cards, including the Philips MIFARE UltraLight, MIFARE 1K and MIFARE 4K. The MIFARE Magic window (Figure 1) also offers the facility to send individual commands to the card with a click of the mouse. This allows you to determine the characteristics of different cards very easily. Examples of compatible cards include the MIFARE UltraLight RFID card supplied with this issue, and described in more detail in a separate article, and smart cards used on many public transport systems all over the world — for example, the London Underground Oyster card

In stand-alone operation, for example in an access control application, the reader can be used directly with the firmware we have developed. On switch-on the reader immediately looks for cards within the range of the antenna (a few centimetres) and reads any cards it finds in that area. The LCD (if connected) then shows the card type along with its serial number, and the switching output of the reader is activated.

The reader is constructed around the newest Philips reader IC type MF RC522 and a type LPC936 microcontroller. Since the reader IC is only available in an HVQFN32 package, we have decided to solve the problems of mounting and soldering by making available ready populated and tested

reader boards fitted with pre-programmed microcontrollers.

The *Elektor Electronics* RFID reader is naturally ideal for experimenting with the free MIFARE UltraLight card. The system includes a powerful microcontroller and I²C, SPI, UART and USB interfaces, and free development tools

are available. This makes it suitable for developing dedicated applications such as door and gate openers, membership card systems, storing passwords and configuration data, payment systems, security for domestic appliances such as televisions, video recorders and PCs, monitoring battery

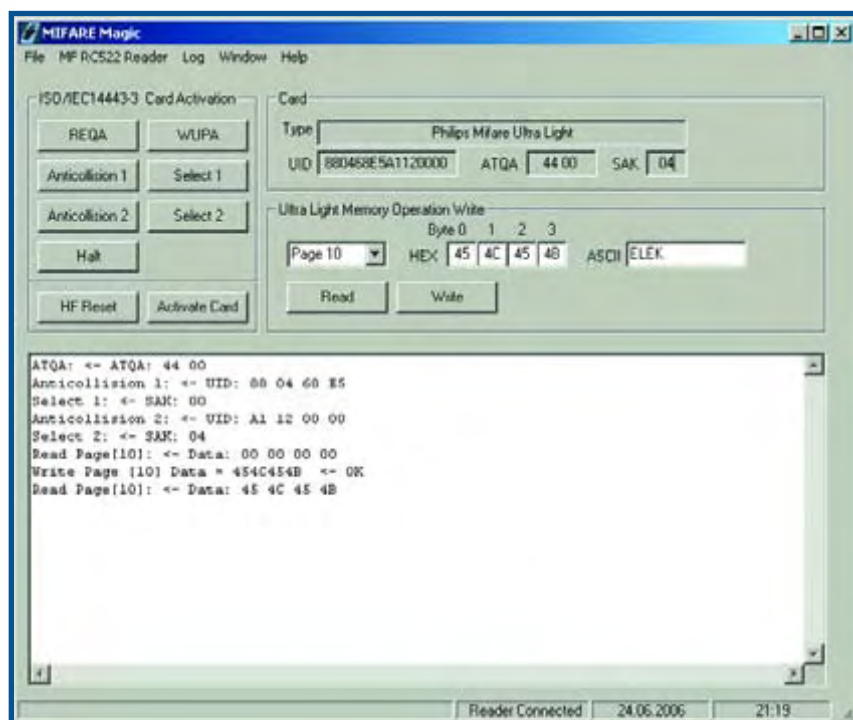


Figure 1. The MIFARE Magic program developed for the *Elektor Electronics* RFID reader allows MIFARE and ISO 14443-A RFID cards to be read, written and programmed.

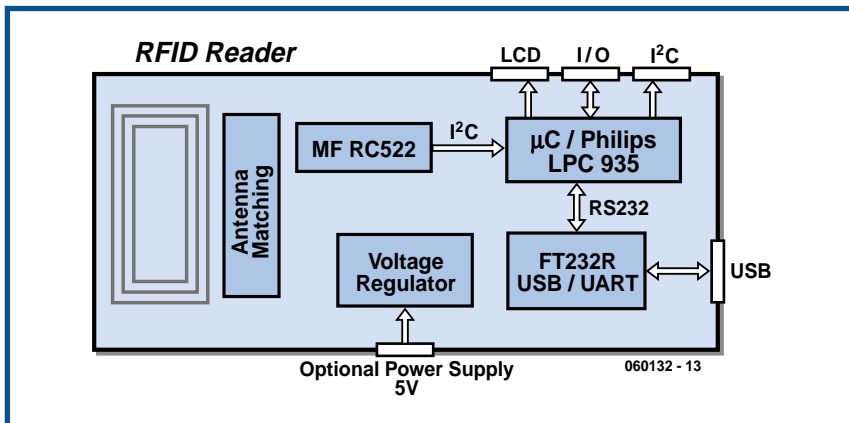


Figure 2. Block diagram of the Elektor Electronics RFID reader.

packs and much more besides. The combination of secure identity, data storage and contactless interface opens up many opportunities for novel applications.

Reader hardware

Figure 2 shows the block diagram of the reader. The basic reader functions, including the creation of the HF magnetic field, modulation and demodulation, and the generation of the ISO 14443 data stream, are carried out in the MF RC522. It is simplest to think of the MF RC522 as a contactless UART driven directly by the microcontroller. In the *Elektor Electronics* reader we have used an 8051-compatible LPC936 microcontroller from Philips. The CPU takes only two cycles per instruction and is clocked at 16 MHz. This speed and the 16 kbyte Flash

memory are sufficient for an enormous range of possible applications. Programs for the microcontroller can be simply written using any 8051 compiler. Communications with the PC are handled by an FT232R USB/RS232 interface chip from our friends at Future Technology Devices (FTDI).

The full circuit diagram is shown in Figure 3. When connected to a PC, power is taken from the USB via mini-connector K1. The FT232R USB interface chip is configured to report the reader as a high-power device when the bus is initialised (during 'enumeration'). As a bus-powered device the reader can then draw a current of up to 500 mA. When enumeration is complete the /PWRNEN signal on pin 11 of IC1 changes state, making P-channel MOSFET T2 conduct. The 5 V supply is then passed through to voltage regulator IC5. The output of the LM2937 pro-

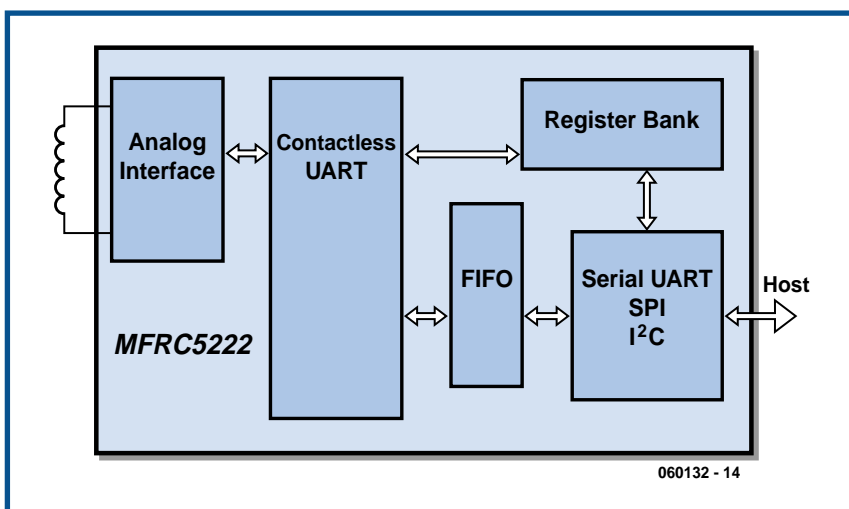


Figure 4. Block diagram of the Philips MF RC522 reader IC.

vides the 3.3 V supply for the LPC microcontroller (IC3) and the MF RC522 (IC4). Red LED D6 shows when the 3.3 V supply is present. If 5 V power is not provided via the USB connector Schottky diode D4 allows an external power supply to take over automatically. Either four AA-size cells (the enclosure suggested in the parts list will accept these) or a 5 V mains supply capable of delivering at least 300 mA can be used.

Figure 4 shows an overview of the internal functions of the MF RC522 reader IC in the form of a (greatly simplified) block diagram. The output drivers of the device allow direct connection of transmit and receive antennas without external active amplification circuitry. A few passive components provide the essential matching to the antenna characteristics. The analogue interface handles demodulation and decoding of the reply data sent by the card. The digital block is responsible for constructing the ISO 14443A or MIFARE protocol frames and accompanying error detection (parity and CRC). The FIFO buffer allows 64-byte blocks to be sent and received in ISO 14443 mode ('T=CL' protocol). In MIFARE mode the largest data blocks exchanged are at most 16 bytes long, and so there is no need for the microcontroller to split up the command packets. The registers of the MF RC522 can be programmed over the SPI, asynchronous serial or I²C interfaces. Since the LPC936 microcontroller only has one asynchronous serial interface, and this is required for communications with the PC, the I²C interface is used to talk to the MF RC522.

If desired an LCD module can be connected to port P0 of the LPC936 via connector K2. P0.0 is buffered by a transistor and provides a switched output, and the SPI and I²C interfaces of the microcontroller afford plenty of opportunities to expand the reader by adding extra hardware. For example, a real-time clock could easily be added to allow for time monitoring, and the switched output could control a door opener; see also the pages about the RFID reader on the *Elektor Electronics* website.

Get started

The double-sided printed circuit board for the *Elektor Electronics* RFID reader is shown in Figure 5. It is only possible to reflow solder the reader IC, and so we are making the board available

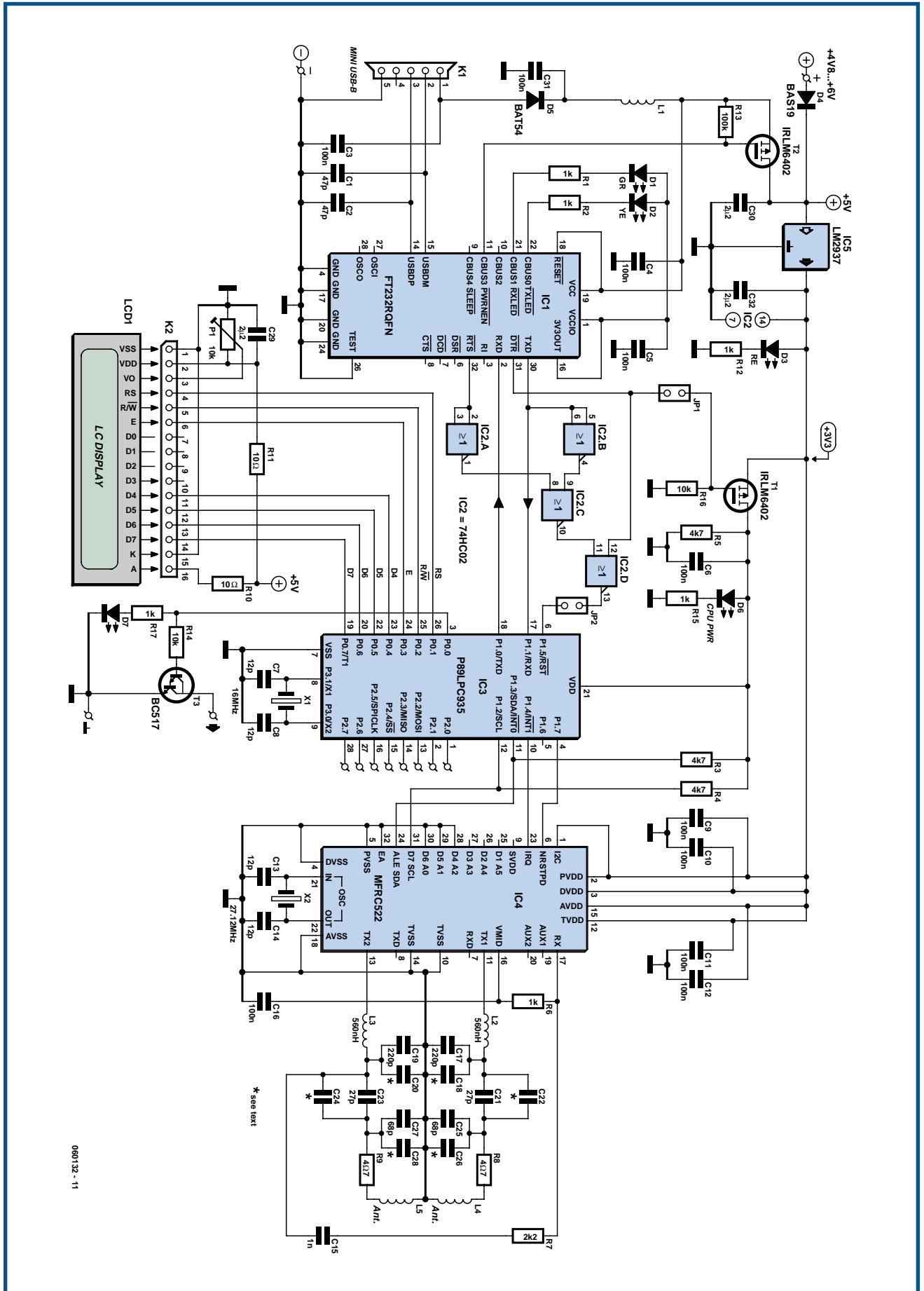


Figure 3. Complete circuit diagram of the reader, which can operate either in stand-alone mode, using the LCD module, or in conjunction with a PC using the USB interface.

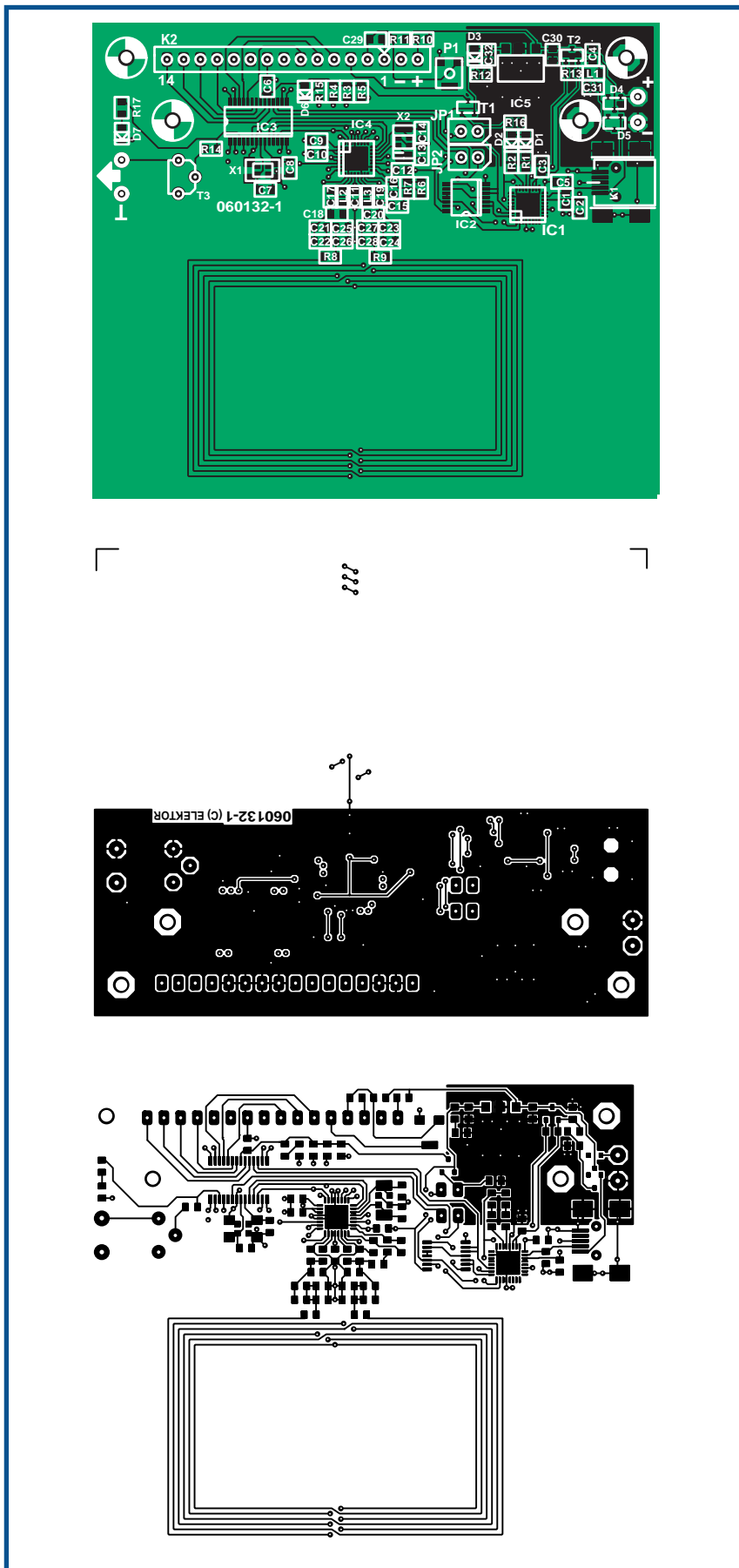


Figure 5. The double-sided printed circuit board incorporates the antenna. The reader IC is not suitable for hand soldering and so the board is available ready populated and tested.

ready populated and tested. Instructions are also provided for building the unit into the suggested enclosure, which we can also supply.

The two jumpers on the reader board (JP1 and JP2) are not fitted for normal operation. Assuming the LCD module is connected to the reader board, the unit is ready for operation as soon as power is applied, and the serial number of any RFID card within range of the reader's antenna will appear on the display. If the display appears blank, the contrast should be adjusted using P1.

To use the reader with a USB connection to a PC, the free CMD-FDTI-USB driver must be downloaded from the *Elektor Electronics* website. This particular driver is required because the FT232R contains the *Elektor Electronics* Vendor ID and Product ID.

When the RFID reader is connected to the PC using the supplied USB cable Windows will automatically detect the new USB device. The freshly-downloaded driver should be selected for the unit. If problems arise, the 'Installation Guide' on the FTDI website (www.ftdichip.com) can be consulted for assistance: this guide is also applicable to the modified driver.

Installing the CMD-FTDI driver installs both the 'D2XX' (direct) and 'VCP' (virtual COM port) drivers. The VCP driver allows the USB link to be treated from the point of view both of the PC and of the microcontroller as an ordinary RS232 connection.

The D2XX driver is required if it is desired to modify the unit in a way that requires changes to the internal configuration data stored in EEPROM in the FT232R. This can be done using the PC-based program MPROG, available as a free download from the FTDI website: MPROG will work only with the D2XX driver.

MIFARE Magic

Once the driver has been installed, MIFARE Magic, a specially-written PC-based program for the *Elektor Electronics* RFID reader, can be run. This is also available as a free download, from www.elektor-electronics.co.uk. After downloading the program the contents of the ZIP file must be copied into a subdirectory of your choice. Start the program with a double-click on MifareMagic.exe, with the reader already connected to the USB port. This allows MIFARE Magic to find the reader automatically. There is no need

COMPONENTS LIST

Resistors

(all SMD case 0805, 5%)

R1,R2,R6,R12,R15,R17 = 1k Ω

R3,R4,R5 = 4k Ω

R7 = 2k Ω

R8,R9 = 4 Ω

R10 = 270 Ω

R11 = 10 Ω

R13 = 100k Ω

R14,R16 = 10k Ω

P1 = 10k Ω -preset, SMD, 4 mm SQ

Capacitors

(all SMD case 0805, 16 V, ceramic)

C1,C2 = 47pF NPO

C3,C4,C5,C6,C9,C10,C11,C12,C16,

C31 = 100nF

C7,C8,C13,C14 = 12pF NPO

C15 = 1nF NPO

C17,C19 = 220 p NPO

C18,C20 = not fitted

C21,C23 = 27pF NPO

C22,C24 = not fitted

C25,C27 = 68pF NPO

C26,C28 = not fitted

C29,C30, C32 = 2 μ F2

Semiconductors

D1 = SMD LED (0805) green,
low-current

D2 = SMD LED (0805) yellow,
low-current

D3,D6,D7 = SMD LED (0805), red,
low-current

D4 = BAS19 (200 mA; SOT23)

D5 = BAT54S (30V / 300 mA; SOT23)

T1,T2 = 6402 (p-channel MOSFET, 20V /
3.7A; SOT23)

T3 = BC517 (npn Darlington; TO92 case)

IC1 = FT232RQFN (QFN32 case, FTDI)

IC2 = 74HC02 (TSSOP14 case; NOR
gate)

IC3 = P89LPC936FDH-S (SSOP28 case;
Philips)

IC4 = MFRC52201HN1 (HVQFN32case;
Philips)

IC5 = LM2937 (low-drop, 3V3, SOT223
case)

Miscellaneous

X1 = 16MHz quartz crystal (18pF parallel
capacitance; 5-3.2mm)

X2 = 27.12MHz quartz crystal (18pF
parallel capacitance; 5-3.2mm)

K1 = miniature USB-B socket, SMD,
5-way

L1 = SMD ferrite (1.5 A; 0805 case)

L2,L3 = 560nH SMD inductor (0805 case)

JP1,JP2 = 0.1-in. jumper (see text)

LCD1 = LCD module with 2x16 characters
and backlight



Enclosure, dim. 146x91x33 mm with LCD
window and battery compartment for 4
AA batteries

PCB, order code **060132-91** (populated
and tested, including USB cable; see
Elektor SHOP pages and
www.elektor.com)

Compatible LC display (see Elektor SHOP
pages and www.elektor.com)

89LPC936 source & hex code files; free
download from www.elektor.com

Mifare Magic PC software incl. source
code; free download from
www.elektor.com

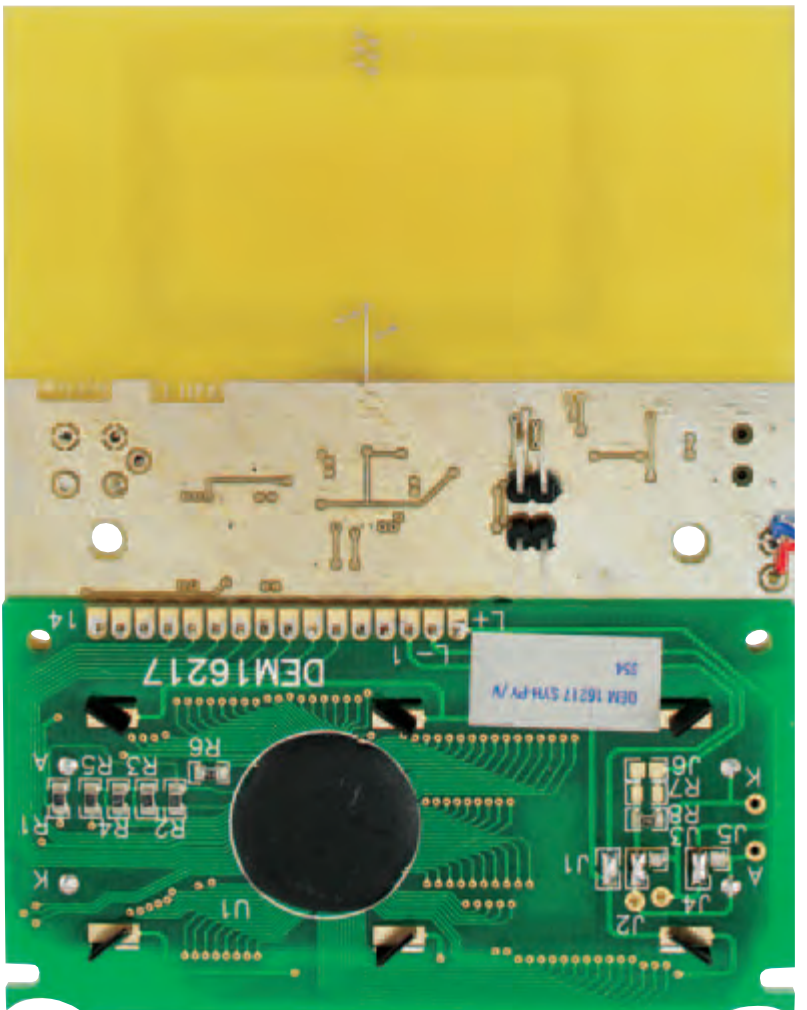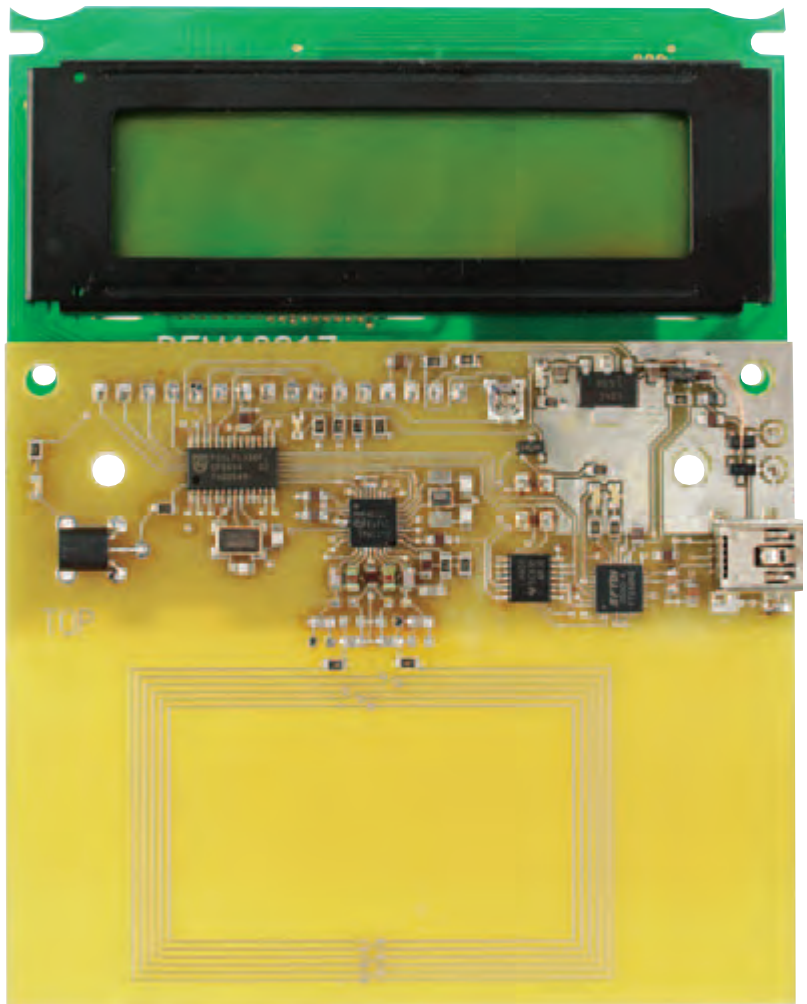

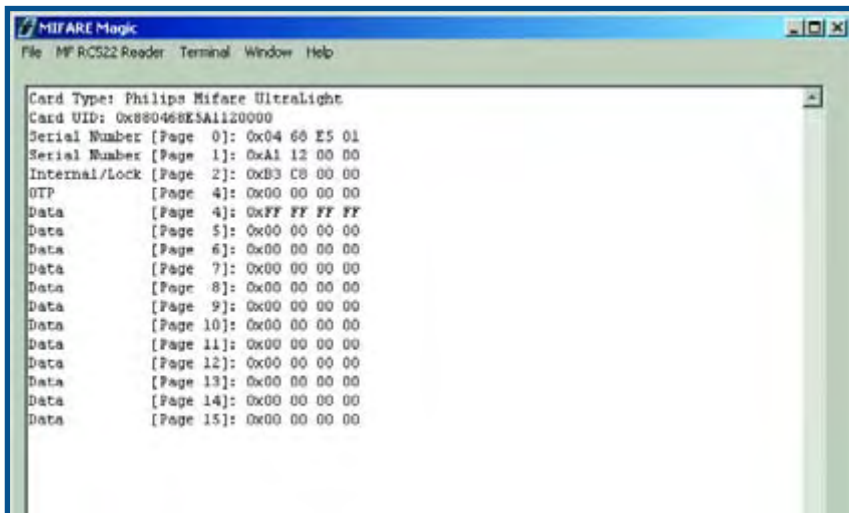


Figure 6. The 'Terminal' view of MIFARE Magic shows all the characters sent by the reader over the USB interface.

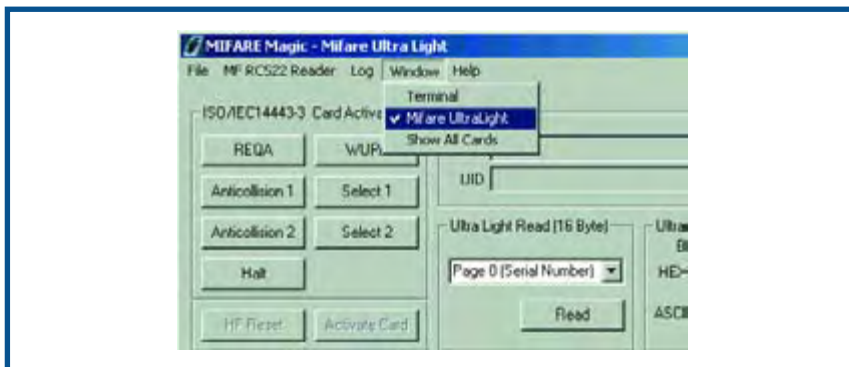


Figure 7. The 'MIFARE UltraLight' and 'Mifare Standard' windows allow simple programming of the RFID card.

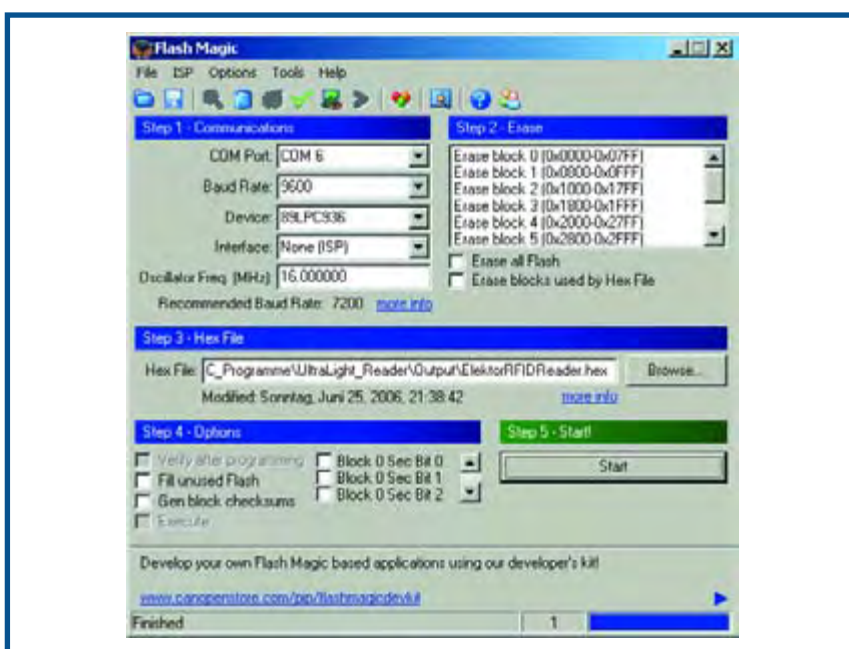


Figure 8. The free PC-based Flash Magic program can program the LPC microcontroller over the USB interface of the Elektor Electronics RFID reader.

to select a COM port, as MIFARE Magic uses the D2XX driver internally. **Figure 6** shows the 'Terminal' view of MIFARE Magic. This mode emulates a VT100 terminal and displays all the characters sent by the LPC microcontroller over the FTDI interface.

The firmware in the LPC microcontroller defaults to 'terminal' mode on power-up. As soon as the reader detects a new card within its field it activates the card. The reader determines whether the card is a MIFARE UltraLight, MIFARE 1K or MIFARE 4K. The entire memory contents of the card are read out and displayed on the MIFARE Magic terminal. For MIFARE 1K and 4K cards the standard MIFARE key is used. If the card uses a different key the data stored in certain sectors will not be readable. To use a different terminal program instead of MIFARE Magic (such as HyperTerminal or the built-in terminal in the LPC Flash Magic programming tool), the VCP driver must be used and the terminal program must be told the number of the relevant COM port. The parameters for the port are as follows: 115200 baud, no parity, 8 data bits and one stop bit.

The 'Window' menu allows MIFARE Magic to be switched between the 'Terminal' view, the 'MIFARE UltraLight' and the 'Show All Cards' views. The 'MIFARE UltraLight' window (see **Figure 7**) allows various card commands to be executed with a click of the mouse. This makes it easy to program a MIFARE UltraLight card, such as the sample supplied free with this issue. When this window is opened the firmware in the LPC microcontroller on the reader board switches from terminal mode into PC reader mode. Here the microcontroller waits for a card command from the PC and calls the corresponding function in its software. This mode is useful when developing applications on the PC. The 'Show All Cards' window displays the serial numbers of all cards currently detected by the reader. This is useful for testing reader range and the capacity of the reader to deal with multiple cards simultaneously.

Program-it-yourself

For dedicated applications it is possible to modify or completely rewrite both the firmware in the LPC936 and the software running on the PC. Any updates to the reader firmware will also require reprogramming the

LPC936. The most up-to-date software will always be available on the *Elektor Electronics* website for free download. Updates will be reported on the news pages of the website and in the magazine under 'Corrections and Updates'. The LPC on the reader board can be programmed directly over the USB port using the free PC program 'Flash Magic' (see **Figure 8**). This program, from Embedded Systems Academy (www.esacademy.com) and sponsored by Philips (www.semiconductors.com) supports a range of Philips microcontrollers.

Both jumpers JP1 and JP2 must be fitted on the reader board before the LPC microcontroller can be programmed. Interested readers will find a detailed discussion of how to program the device on the *Elektor Electronics* website along with a list of all the MIFARE UltraLight reader and card commands. The reader firmware was developed using the Keil mVision3 C compiler for the LPC microcontroller. All the commands necessary for developing dedicated applications are made available as functions and so it is not necessary to deal directly with the individual registers of the MF RC522.

The listing shows the code necessary to activate a MIFARE UltraLight card and read a data block. The data will be transmitted using the serial interface of the microcontroller.

As mentioned above, the PC reader mode of the LPC firmware allows a PC application to invoke card functions. Using this mode function invocation is done using a very simple serial protocol to communicate with the program running in the microcontroller. When the function has been executed the response is returned to the PC. The naming and parameters of the functions are identical in the PC software and in the microcontroller firmware. The source code for the PC-based MIFARE Magic program and for the microcontroller software can be downloaded for free from the *Elektor Electronics* website.

Listing

```
while(1)
{
    status = ISO14443_Request(WUPA, &bATQ);
    if(status != STATUS_SUCCESS)
        continue;

    status = ISO14443_Anticoll(Level1,0,&abSNR[0]);
    if(status != STATUS_SUCCESS)
        continue;

    status = ISO14443_Select(Level1, &abSNR[0], &bSAK);
    if(status != STATUS_SUCCESS)
        continue;

    // Check if UID is complete
    if((bSAK & 0x04) == 0x04)
    {
        // UID not complete
        status = ISO14443_Anticoll(Level2,0,&abSNR[4]);
        if(status != STATUS_SUCCESS)
            continue;

        status = ISO14443_Select(Level2, &abSNR[4], &bSAK);
        if(status != STATUS_SUCCESS)
            continue;
    }

    // Read UltraLight Block 0..3
    status = Read(0,abDataBuffer);
}
```



(060132-1)

Experimental RFID

Martin Ossmann

After the first sample Mifare cards were received in our editorial office, there was a lively discussion about whether any information could be extracted from these RFID cards using simple resources. Hardly anyone could imagine that a reader could be built without using a special reader IC. But it can be done, and with a commonly available microcontroller to boot! This article describes the protocols and coding in detail. The software for this project is thus quite suitable for use in your own designs.

The readily available Atmel ATmega16 is used as the processing unit. It is easy to program via the ISP interface using public-domain tools, such as the AVR Studio development environment, the WinAVR compiler and the PonyProg programming adapter (refer to the 'Mini ATmega Board' article in the May 2006 issue of *Elektor Electronics*). The experimental reader described here can also be upgraded to read ISO 15693 cards. Such cards are frequently used for applications such as product identification.

(Un)available information


The first question is how to obtain the information you need to design your own reader. The definitive reference is of course the ISO standard, but it is not exactly cheap. However, ISO documents pass through the public 'Final Committee Draft' (FCD) stage before being designated as official standards, with the result that they are partially available on the Internet. It also helps a lot if you have an operating reader available for making measurements. Here the author would like to express his special thanks to Mr Schalk at Philips for his active support. Additional information is also available from manufacturers of ISO 14443 cards and reader ICs. Combined with a good deal

of software for coding and decoding the protocols, that ultimately leads to a successful result.

Test transmitter

If you examine the data sheet of the Mifare Ultralight card, you will see that the simplest response of the card is a reply to a Request Command Type A (REQA command) after a power-on reset (POR). Once you have attained this first objective, you can examine the reply from the card and try to decode it. Of course, you have to understand how commands are sent to the card before you can actually send the command. The ISO 14443 standard describes how the commands are coded as bit sequences and sent to the card. The card is powered by a magnetic field generated by a coil. The nominal carrier frequency (f_c) of the field is 13.56 MHz. This carrier is modulated with 100% amplitude modulation to transfer data to the card. **Figure 1** shows the simple circuit we used for our first test.

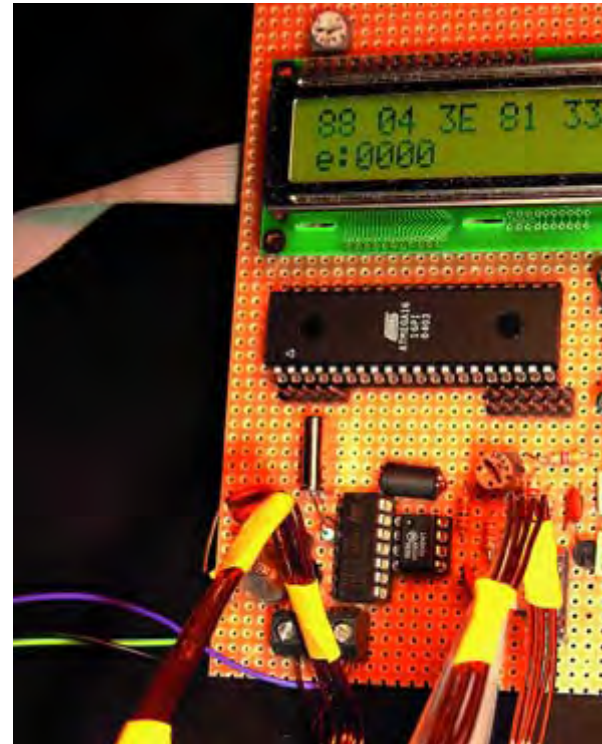The carrier frequency f_c is generated by a crystal oscillator, and this signal is also used as the clock for the microcontroller (in this case an ATtiny2313). One port pin acts in conjunction with a NAND gate (74F00) as a simple amplitude modulator. The 74F00 can



supply sufficient current to energise a Mifare card using a simple transmitter coil (note that a 74H00 can't manage this). **Figure 2** shows the assembled circuit in the test setup.

The bits sent from the reader to the card are transferred using a bit interval for each bit of $t_{\text{bit}} = 128 \div f_c = 9.439 \mu\text{s}$. This yields a bit rate of $13.56 \text{ MHz} \div 128 = 105.9375 \text{ kbit/s}$. That is close to 100 kbit/s, or 100 microseconds per bit. **Figure 3** shows how the individual bits are arranged.

Bit coding

The bit interval t_{bit} can be imagined to be divided into four equal intervals of approximately $2.5 \mu\text{s}$. There are three possible waveforms within each bit interval, which are designed X, Y and Z. With waveform X, the carrier is briefly keyed off starting at the middle of the bit interval. With Y the carrier is not keyed off, and with form Z it is keyed off at the start of the bit interval. A logic 1 is indicated by waveform X. The first zero of a sequence of logic 0 bits is coded using the Y wave-

Reader Masterclass RFID decoding



form, and the successive zeros are coded using the Z waveform. A series of bits always starts with Z (as the start sequence) and ends with a zero bit followed by Y (the details are given in the standard).

The REQA command consists of 7 bits and has the value 025H in hexadecimal notation. The bits of each byte are transmitted with the least significant bit first. That yields the waveform shown in **Figure 3**. Here the carrier is keyed off for approximately one quarter of the bit interval, which means around $2.5 \mu\text{s}$. The standard specifies the form of the pulses more precisely. The chosen transmission protocol fulfils several requirements. First, the carrier is keyed off only briefly to ensure that the card continues to receive sufficient energy on average. In

addition, the bit clock can be recovered easily from the signal.

Now it's interesting to take a closer look at the waveform at the moment when the carrier is keyed off. For this purpose, we placed a card under the transmit coil and used a 'sniffer coil' (described in more detail below) to view the waveform on an oscilloscope (see **Figure 2** and **Figure 4**). As our transmit coil is not accompanied by a capacitor to form a resonant circuit, it can be keyed without generating overshoots or undershoots. However, an overshoot is clearly visible after the carrier is switched off (left cursor line in **Figure 4**) when the transmit coil is close to the card. This overshoot is generated by the resonant circuit in the card.

Response

If the REQA command is sent correctly and with sufficient power, the card must naturally send a sequence of two bytes in reply. Load modulation is used to send data back to the reader. The card generates this modulation by intentionally increasing the load on the

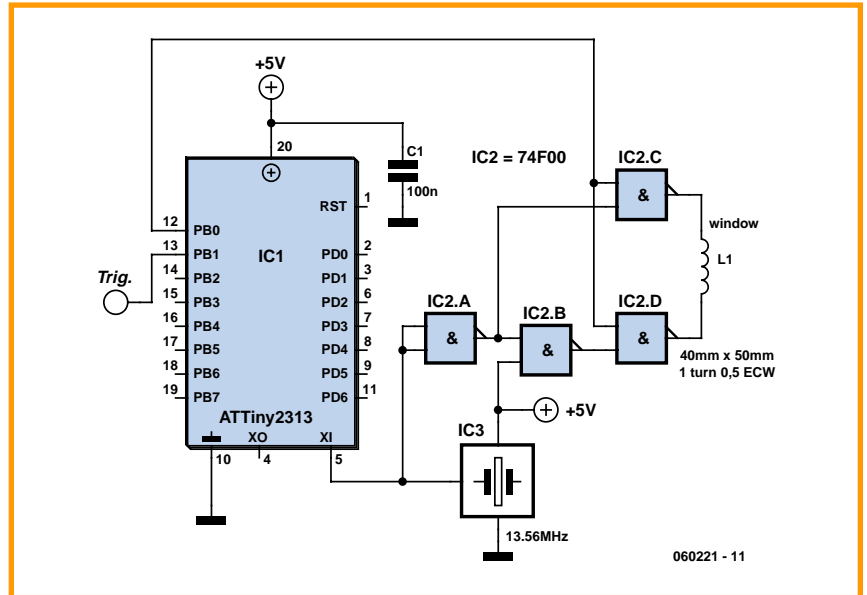


Figure 1. A simple Mifare test transmitter.

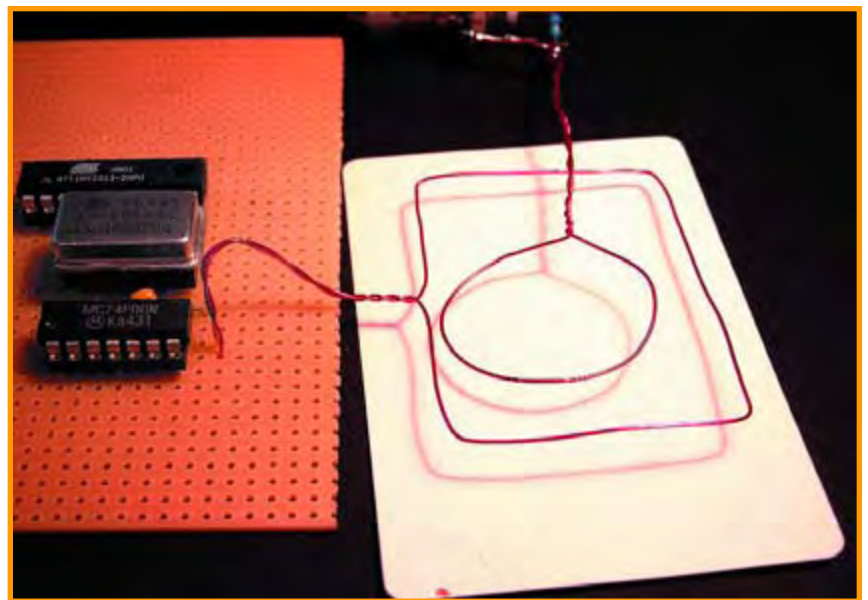


Figure 2. Transmitter circuit with Mifare card and sniffer coil.

reader field. The modulation frequency used for this purpose is $f_m = f_c \div 16 = 847.5 \text{ kHz}$. The bit interval is again (in the simplest case) $t_{\text{bit}} = 128 \div f_c = 9.439 \text{ ms}$. Here a '1' is encoded by applying load modulation during the first half of the bit interval

(the first half-bit). A '0' is coded by applying load modulation during the second half of the bit interval. The load modulation can be observed readily using the sniffer probe.

The signal from the sniffer probe is shown in more detail in **Figure 5**. The

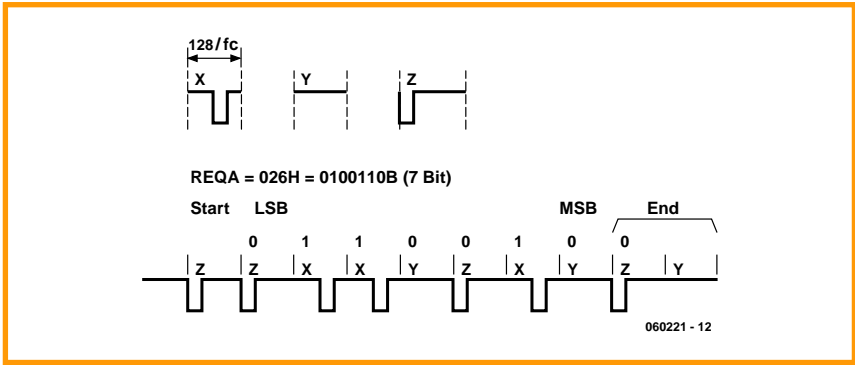


Figure 3. Bit coding scheme for transmitting data to the card.

upper trace shows a relatively long portion of the signal. The seven carrier keying pulses of the REQA command can be seen at the left. The load modulation is faintly visible at the far right end of the upper trace. It is shown magnified in the lower trace. The first bit of the reply from the card is visible between the cursor lines. The first half (approximately 5 μ s) is modulated with exactly four cycles of f_m . This is followed by the unmodulated half-bit of the '1' bit. As you can see, the '1' bit is followed by two '0' bits.

Reader design

After this observation session, we had a clear idea of how to build a simple reader. The transmitter could remain almost as is, but the output stage had to be somewhat more powerful to ensure reliable card reading. Here we used a second coil to enable load modulation to be detected properly. The card is inserted between the two coils. The load modulation is detected by amplitude demodulation of the signal picked up by the second coil. The design of the analogue portion is thus easier to explain than the digital components, which consist of a suitable microcontroller and a good deal of software.

Which microcontroller?

The microcontroller must be able to not only generate the transmit signal, but also receive and evaluate the response signal from the card. That requires a fast microcontroller, and not just for transmitting. The received bits arrive at a rate of approximately 100 kbit/s. The amplitude of the modulation signal should be sampled at least four times for each bit to enable proper detection of '0' and '1' bits. It helps that we know exactly when the card transmits and that it does not transmit an especially large number of bits. That means the detected signals can first be collected in memory and then evaluated later. A microcontroller with sufficient memory is thus useful. As the protocols include niceties such as parity bits, block checksums and CRC checksums, pure assembly-language programming would be rather laborious. It is thus better to generate most of the code in C. We decided on an Atmel ATmega16, which has everything we need: sufficient processing power, ready availability, free software (WinAVR), and a simple pro-

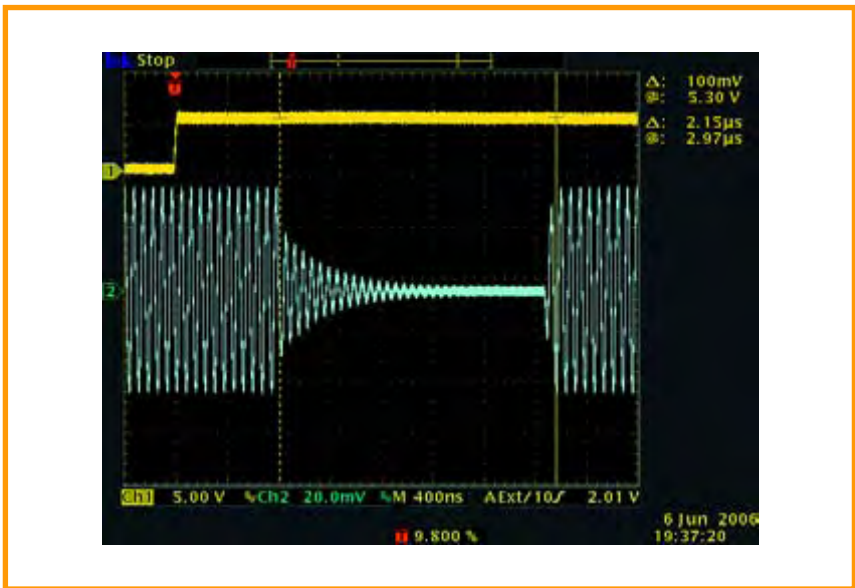


Figure 4. Sniffer probe signal with carrier keying.

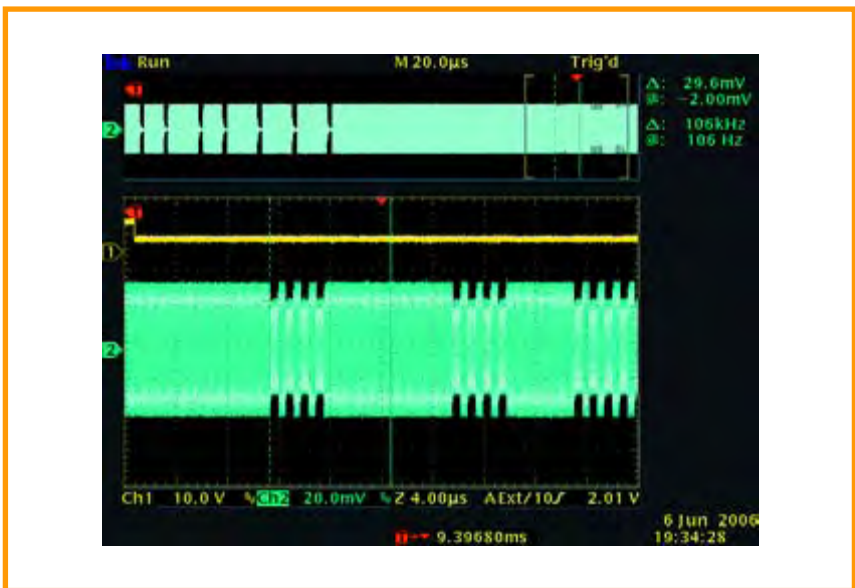


Figure 5. Sniffer probe signal with load modulation.

gramming interface. That should certainly be enough! We thus arrived at the overall design of our complete DIY RFID reader, which consists of three subcircuits.

Transmitter circuit

As you can see from **Figure 6**, the transmit portion is still simple. IC1 generates the 13.56-MHz clock, and the microcontroller modulates (keys) this signal using the MOD signal (port B.0 pin). The 13.56-MHz signal provided by the 74HC00 passes through a push-pull stage formed by two simple, small MOSFETs (T1 and T2). It then arrives at the series-resonant circuit L1/C4. R2 damps the resonant circuit to reduce the duration of overshoots when the carrier is keyed off. Here we can remark that the reader does not necessarily have to be operated at 13.56 MHz. Experiments showed that the Mifare cards will accept any signal between 12 MHz and 16 MHz. However, as the microcontroller in our reader also derives the baud rate from the clock frequency, the serial communication routines in the software must be reconfigured if you use a non-standard frequency, which means the program has to be recompiled.

Receiver circuit

The receiver circuit (**Figure 7**) has to demodulate the load modulation and provide the result to the microcontroller as a digital signal.

Coil L3 receives the load-modulated signal, which is rectified by D1. Resonant circuit L4/C6 has a resonant frequency of approximately 847 MHz, which matches f_m . It is important that the bandwidth of this resonant circuit is sufficiently large to pass the modulation signal, which has a bit rate of approximately 100 kHz. This is achieved by damping it with resistor R6. Transistor T3 amplifies the signal, and resonant circuit L5/C7/R8 provides additional filtering. The modulation present on the signal can then be detected by a rectifier (diode D2). The rectifier is followed by a three-stage RC low-pass filter and a comparator. The reference level is set using R13. The digital signal at the output is provided to the microcontroller for evaluation in the form of the DEMOD signal. The internal comparator of the ATmega16 could have been used instead of comparator IC2, but

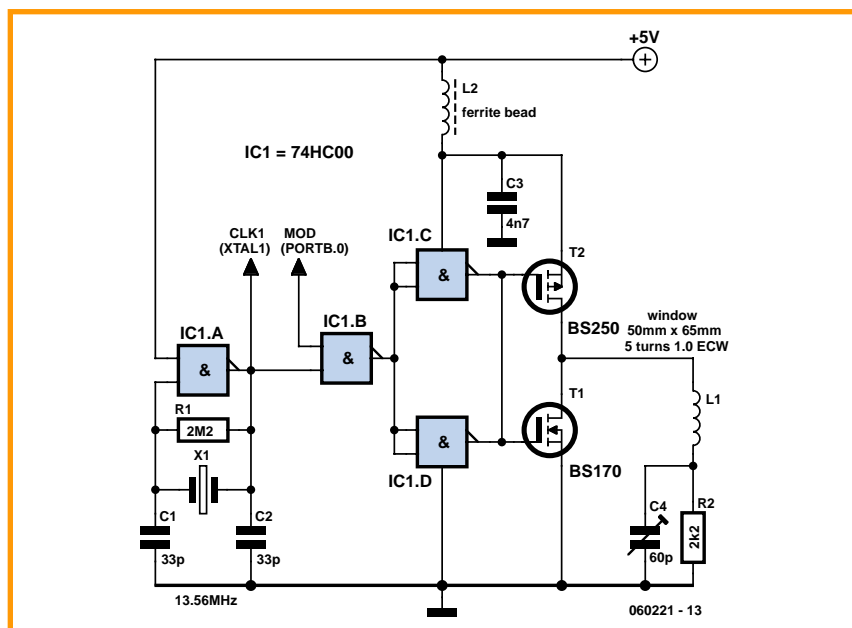


Figure 6. Clock generator and transmitter portion of the experimental reader.

using an external comparator makes it easier to examine the signal with an oscilloscope when the circuit is first put into service and check that it is operating properly.

Digital portion

The digital portion of the circuit, as shown in **Figure 8**, does not have any unusual circuitry. A MAX232 supports an RS232 interface. A two-line LC display enables the data from the card to be displayed for stand-alone operation. A simple voltage regulator circuit with a diode for protection against reverse polarity allows the circuit to be powered by a simple AC adapter. Switch S1 acts as a reset switch, and connector K2 provides access to the ISP port for in-system programming.

Construction and coils

The prototype (see the photo at the head of the article) was constructed on a piece of Vector board. Note that the portions of the circuit that process RF signals must be adequately decoupled with capacitors. The two rectangular coils (50 mm x 65 mm) spaced 30 mm apart, each consisting of 5 turns of 1-mm enamelled copper wire, are a special feature. The Mifare card should be placed between the two coils. The optimum position can be determined experimentally. Other configurations are also worth trying. It may be necessary to adjust the trimmer accordingly.

Software and initial operation

The software for the microcontroller can be downloaded from the *Elektor Electronics* website (www.elektor-electronics.co.uk). You will find the appropriate file and all supplementary information on the project page for this article, which you can access via the issue table of contents on the *Elektor Electronics* website or our RFID summary page at www.elektor.com/rfid. The software is accompanied by a comprehensive PDF document that addresses the following topics:

- programming the Atmel microcontroller
- building a sniffer probe for field strength measurements
- transmitter alignment and functional checks
- receiver alignment
- software tools and tips
- security method
- collision detection

ISO 15693 RFID devices

Besides ISO 14443, ISO 15693 is the most commonly used standard for RFID devices operating at 13.56 MHz. Although both standards use the same frequency, they differ considerably in other regards. ISO 14443 defines a contactless interface for smart cards with a range of at most 10 cm, while ISO 15693 defines a contactless label interface with a range of up to 1.5 m.

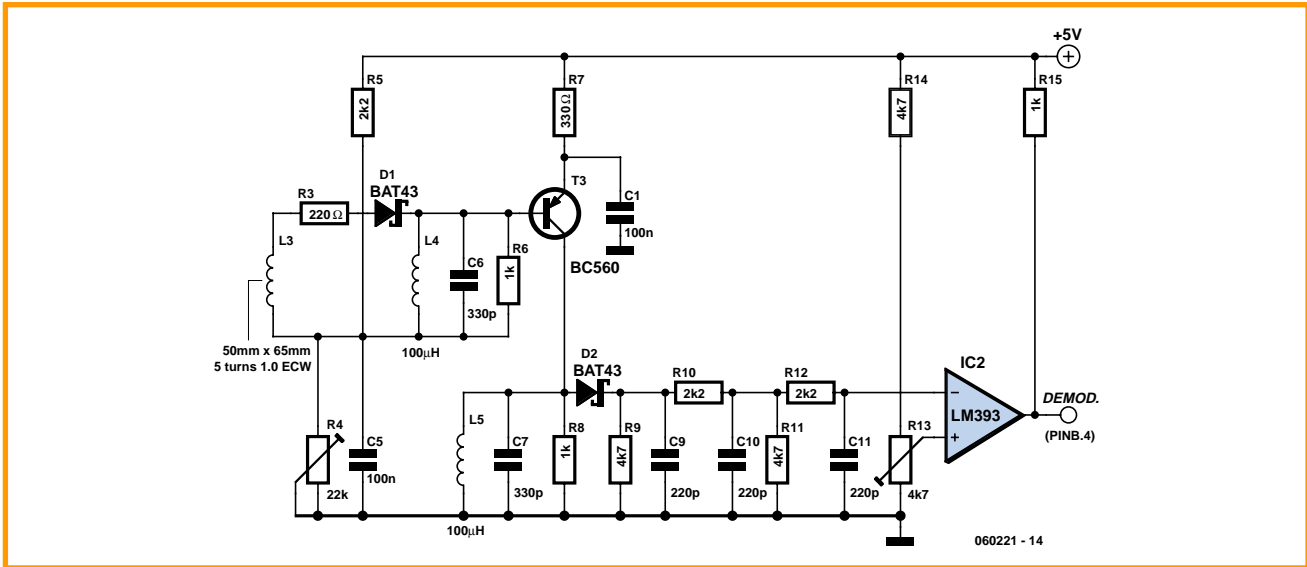


Figure 7. Receiver and demodulator circuit.

In other words, you will find ISO 15963 on the products in your shopping basket once barcode scanners at cash points have been replaced by RFID scanners, while you may already have ISO 14443 in your customer card. Our initial experiments indicated that the experimental reader could also be upgraded to read ISO 16963 RFID

labels. As these labels use a different auxiliary carrier frequency, LC circuits L4/C6 and L5/C7 would have to be modified. It would also be necessary to use completely different software, as the modulation and coding methods are significantly different from those used for ISO 14443. However, the different auxiliary carrier frequency and

bit rates also make it possible to build a selective reader with a wider range, and possibly also with collision detection. If our efforts to develop an ISO-15693 version are successful, you will hear about it in a future issue of the magazine and via the *Elektor Electronics* newsletter.

(060221-1)

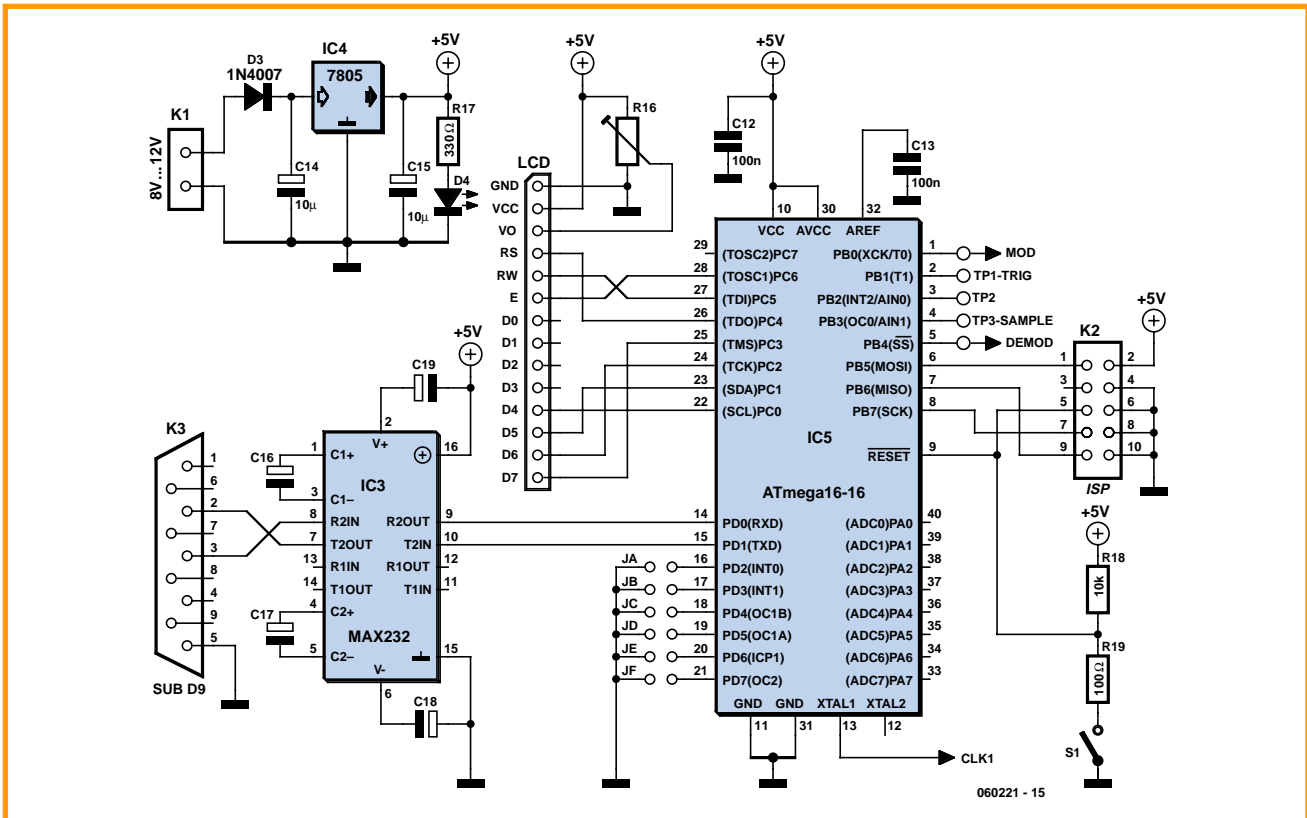


Figure 8. Digital portion with RS232 and LCD.

Cyclone economics

just got more
economical.



Cyclone II The lowest-cost FPGAs ever.

Building on the success of the original Cyclone™ family, the 90-nm Cyclone II family gives designers more density, more features, and more speed than ever before, all at a lower price. Cyclone II devices are the lowest-cost FPGAs ever, making them ideal for a wide range of volume-driven applications and creating a compelling alternative to ASICs for high-volume designs.

When you need a company to rely on, Altera delivers. For high performance, more capabilities, fast time-to-market, and a price that will blow you away, contact us today at www.altera.com/cyclone2.



- Densities up to 3.5x the original Cyclone family
- Dedicated DSP circuitry
- Average of 60% faster than the competition
- 90-nm devices shipping in volume

ALTERA®

The Programmable Solutions Company®

www.altera.com/cyclone2

Distributors

Arrow Electronics (UK) Ltd: 01279 626777
EBV Elektronik UK: 01793 849933

Copyright © 2005 Altera Corporation. All rights reserved. Altera, The Programmable Solutions Company, the stylised Altera logo, specific device designations, and all other words and logos that are identified as trademarks and/or service marks are, unless noted otherwise, the trademarks and service marks of Altera Corporation in the U.S. and other countries. All other product or service names are the property of their respective holders. Altera products are protected under numerous U.S. and foreign patents and pending applications, mask work rights, and copyrights.

Leading through innovation.



Cubesats into Free Orbit

Satellites for home use (well, almost)

Thijs Beckers


Communicating with America on the 70-cm and 2-m bands? This is only possible if you use a satellite or the moon. The first Dutch amateur satellite, Delfi-C³, offers its transponder and even asks amateurs to actively participate in its space mission. Taking your own pictures from space will soon be possible with the Compass-1, another amateur satellite. But can we shoot our own satellite into space?

How would that be, your very own satellite in space? Not likely, you say? A number of university students and staff are making this a reality. They are busy developing their Delfi-C³ satellite [1] intended to be launched next year. Launching may be overstating it — the satellite actually hitches a ride on a Russian SS-18 rocket. However, a lot has to be done yet, because preparing the electronics for the rough journey is a big job. Fortunately the team members are very motivated and they can rely on support from Technical University Delft, The Netherlands and others.

Project

The Delfi-C³ project began in 2004 as a final year project in the faculty of Air and Space Technology at TU Delft. The Delfi-C³ Cubesat is a predecessor of the

research program MISAT, which aims to implement and test new developments for use in space travel. This proved an excellent method for university graduates to gain experience in the actual work involved. In addition, it allowed TUDelft to flex its muscles. Delfi-C³ is, after ANS (1974), IRAS (1983), YES (1997) and Sloshsat (2005) actually the fifth Dutch satellite and the very first student/university satellite to go into space. Delfi-C³ is a very small satellite, which measures only 34×10×10 cm and involves three separate research projects. In addition to the home-grown linear frequency transponder, it contains a solar sensor from TNO and a new type of thin-film solar cell from Dutch Space. The official project names are: 'Advanced radio transceiver (Delfi-C³)', 'Autonomous, wireless solar sensor' (TNO) and 'Thin film solar cells' (Dutch Space). All three still have to prove their functionality in a vacuum. Unfortu-

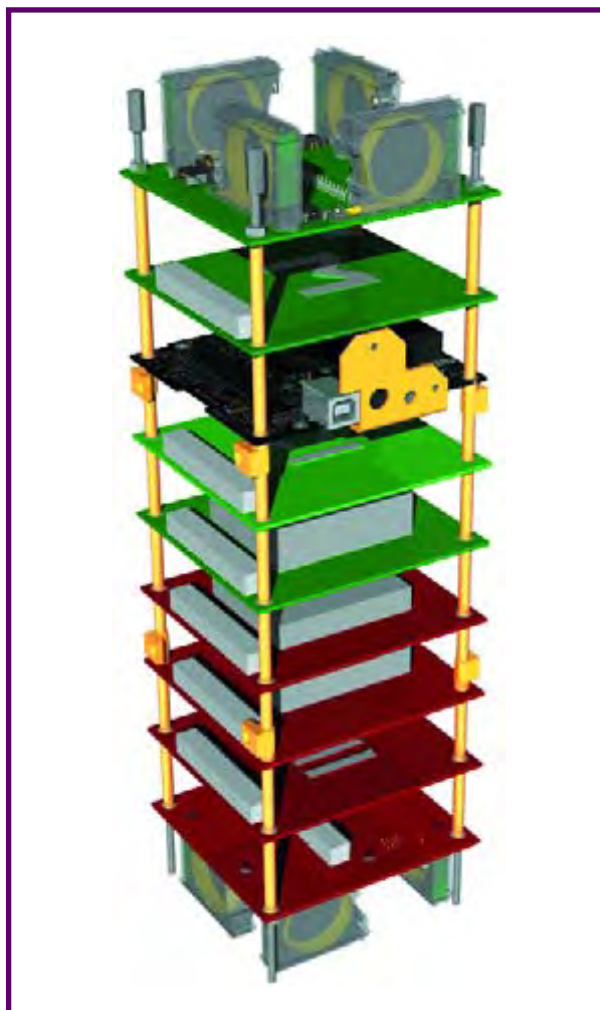

The three units of Delfi-C³ are jam-packed with electronics, as can be seen in this CAD drawing.

nately the three research projects will never come back in one piece. The Cubesat will burn up on re-entry in the atmosphere.

Depending on the altitude, it could actually take quite a while before this happens. At an orbit height of 500 km, for example, the satellite can be expected to be in space for about 25 years. At a height of 1000 km, it could even be hundreds of years before the satellite returns.

Overview


The ground station for Delfi-C³ is located on the top of the 22-storey tower building of the faculty of Electrotechnical Engineering of TU Delft. The base station, jointly built by the faculties of Air and Space Travel, Electrotechnical Engineering, Mathematics and Computer Science, allows students and staff to gain experience with satellite communications to their hearts content. The system can, among other things, autonomously track Low Earth Orbit (LEO) satellites that operate in the VHF, UHF and S bands. In addition, the system can decode telemetry data from these satellites. The team will use their base station to send commands to the Delfi-C³ and receive telemetry information. The transceiver developed by Delfi-C³ will receive control commands from the Delfi ground station and return telemetry data back to earth.

About once a second, Cubesat sends a data word to earth, which contains all the information regarding the housekeeping of the satellite. The data word contains the


Delfi-C³ specs

- 3-unit Cubesat 34x10x10 cm
- 3 payloads:
 - Thin-film solar cells (Dutch Space)
 - Autonomous wireless solar sensor (TNO)
 - Advanced radio-transceiver (Delfi-C³ group/TU Delft)
- 4 solar panels, 5 gallium-arsenide solar cells per panel, power 2.5 watts
- 145 MHz 1200 baud AX25 packet radio BPSK down-link
- 400 mW transmitter power
- Linear mode VHF/UHF radio amateur transponder
- Passover 6x per day on average, of which 3x are useful because of (solar) energy
- 10 to 15 minutes of communication time per pass-over
- Height of orbit 500-1000 km
- Orbit time 1.5 hours

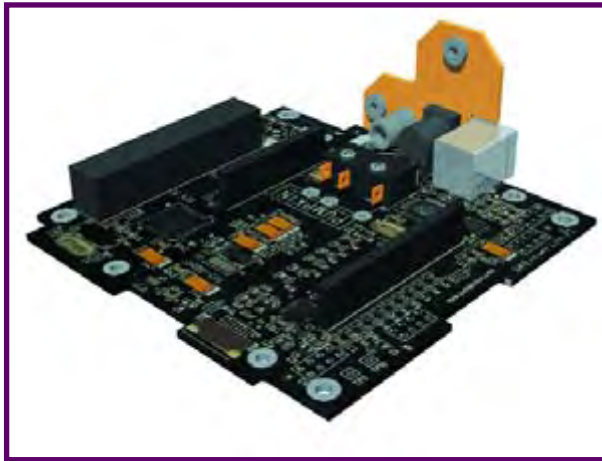
All the PCBs are modelled on the computer in advance. This is a view of the bottom PCB.



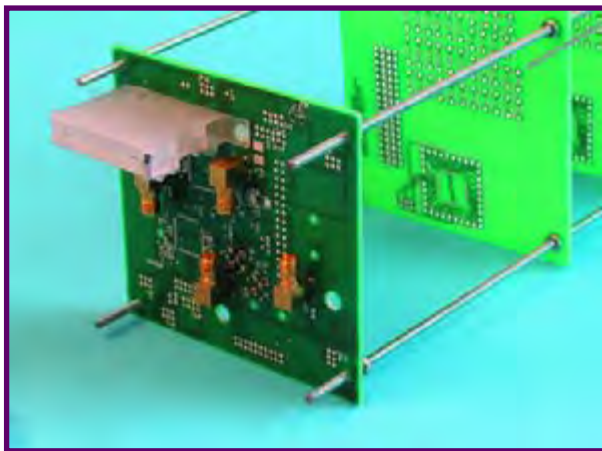Close-up view of the positioning of the antennas in the Delfi-C3 satellite.



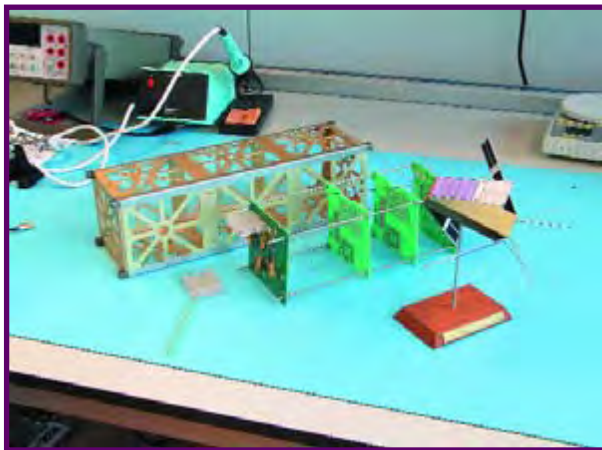From left to right: skeleton of the 3 unit Delfi-C3 Cubesat, early prototype of the internals and on the right a model of the final version.



The satellite is very small indeed!. The one euro coin gives a good impression of the size.



on-board voltage, the on-board temperature, the various currents that flow and all the information from the other two projects. In this way, for example, it is possible to determine the temperature and the very important I/V curve of the solar cells.

The satellite has no data storage capability on board, so all data is immediately transmitted down to earth. The transceiver uses amateur radio frequencies for this purpose, which are also permitted for use with amateur satellite traffic (145 MHz and 435 MHz). The satellite is compatible with AMSAT standards and its linear transponder is available for radio amateurs, allowing them to make cross-continent contacts, for example between Europe and North America, when the satellite flies above the Atlantic Ocean. In exchange for this, the Delfi-C3 crew ask all radio amateurs to send received data from Delfi-C3 to the base station in Delft.

Work is currently in progress on software that allows radio amateurs to process the data at home. In this way, data can be collected when the satellite is out of range of the ground station.

The research project of TNO is a new type of solar sensor with a wireless interface. This is an important experiment for size critical applications because there will be no need for wires running through the satellite.

The solar cells from Dutch Space are also new types, which have to be tested in the tough environment of space. Delfi-C3 is a great opportunity for both companies to test the theories of the drawing table in practice.

Technology

Nanosatellites have little opportunity for energy generation. There is very little room for batteries and scarcely any surface area for solar cells. That is why the on-board electronics has to be very extremely thrifty with energy. The transceiver that is being developed by the Delfi-C3 team has an antenna amplifier which operates with integrated transformers in the negative feedback loop. This allows the efficiency of the amplifier to be increased while trading off linearity. This non-linearity is then corrected with negative feedback. In this way an antenna amplifier has been created that has both greater efficiency and better linearity. This improved linearity is very important in satellites, because multiple frequency bands are often used for the data traffic allowing more data to be transmitted.

Many of the electronic parts used are standard components. Everything works well by using these parts in clever ways. The antennas, for example, are made from the same material as that used for a tape measure. A few things to take into account are operating temperature range, operation in a vacuum and radiation hardness. For example, electrolytic capacitors cannot be used in space, tantalum capacitors have to be used instead. Cosmic radiation can also have a significant influence. It is therefore necessary to add additional screening. For this you need to consider the desired operating life time and the total dose of radiation that the component will have to endure over a certain period. Delfi-C3 has been designed for an operating life of three months. Testing of this design target is done with simulation software, calculations and various radiation sources in a test enclosure. Incidentally, the use of standard components has been proven by a previous successful implementation. OSCAR-7 (an amateur satellite which was launched in 1974) was built with the first generation of CMOS ICs and is still functioning.

Construction handbook DIY satellite

- Think of a technical design subject or a circuit with which you would like to carry out experiments in space.
- Establish a business. Only if you are in business can you apply for a subsidy at the NIVR. You will get a 75% subsidy for industrial research for space technology.
- Look for a wealthy sponsor who is prepared to provide the remainder of the finance.
- Many hands make light work, so look for multiple participants, preferable those with the means to contribute financially as well.
- Buy a Cubesat, costs about € 5000. For that you get an aluminium box that has undergone special treatment and has a Teflon coating on the outside. The structure is qualified and has been tested for launch.
- Solar cells for power generation cost a few hundred euro per cell and are not all that expensive for such a crucial element.
- The internal electronics you buy from the local electronics shop, that works well and is also cheap.
- Printed circuit boards can be made with FR4 substrate. They work well with a little treatment.
- The greatest expense by far is labour. Keep this in mind when you cannot complete the task by yourself and start to employ other people. Of course, you can also look for help at various organisations. There you can always find enthusiasts who will only be too happy to give you a hand in their spare time.

Cold Space?

Another problem that you certainly wouldn't pause to think about in the first instance, is the dissipation of heat. The satellite generates about 2.5 W, of which about 0.4 W is the radio signal transmitted from the antenna. So about 2 watts have to be dissipated as heat somewhere. Since convection does not take place in a vacuum, heat can only be dissipated via radiation and (internal) conduction. And then, 2 W is suddenly quite a lot. In addition there is heating from the sun (some 1000 W/m²).

The only possibility to control the temperature is to choose the surface material of the satellite just right (for example, consider the reflectivity of a surface). The thorough simulation of what comprises the best configuration and the location of where an isolating or radiating surface should be is so complex that it was the thesis for a student from the Delfi-C³ group.

Not the only one

The group from Delft is not unique. In Aachen (Germany) there is also a project which uses a Cubesat. Using the name COMPASS-1 the Fachhochschule Aachen will launch a satellite that besides taking pictures of the earth will also test a new bus system for space vehicles [2]. The equipment on the Compass-1 comprises a GPS, a camera, an energy backup source, a 3-axis magnetometer, five solar cells, some 12 temperature sensors (five of which are on the outside, one near the battery pack and the others integrated in ICs), current and voltage sensors, and a fieldstrength meter. The latter is used to measure the received signal strength of the uplink signal. The orientation of the satellite is adjustable with air coils which act on the earth's magnetic field. The coils are custom manufactured. The insulation material of the wire consists of polyurethane that melts at a temperature of about 180 °C. By melting the polyurethane the windings can be held in place without making a short circuit, a technical *tour de force*.

Technology 2

Compass-1 also operates at 145 and 435 MHz. Just as with Delfi-C³, this satellite is also allocated its own fre-

quencies within the 70-cm and 2-m bands by AMSAT [5]. The uplink of the Compass-1 is in the 2-m band. There are two downlink channels in the 70-cm band. FSK (frequency-shift keying) modulation and the AX20 protocol are used on one channel for sending large data packets, such as photos, to earth. The other channel is available for a CW signal (Morse code).

GPS is used to determine the exact location of the satellite. The other sensors collect telemetry data which is sent to earth for analysis.

After a few months, once the Compass team has completed all their measurements and experiments, they will make the satellite available for use by anyone. That means that any licensed radio amateur can, for example, instruct the satellite to take a picture and receive the data.


In Practice

Before you can even start to think about building a satellite you will have to put a design together, including all the specifications of all the subsystems (what does the system have to do, how does it do it, with what performance, etcetera). You then progress through a sequence of steps where you will closely examine the design concept, validation, breadboard prototype, engineering model and the flight model. Once the entire sequence has been completed, the original specification then serves as the final checklist.

All systems have to be tested on the ground. Every possible fault situation has to be simulated including the environmental tests (that is, thermal tests, vacuum tests, radiation tests, shock, *g*-force and vibration tests related to the launch, etc.).

Before the launch you will need to take into account the altitude it which the satellite will be placed. The main payload satellite determines the altitude. You therefore have to be able to make last-minute adjustments to tune the satellite for the altitude.

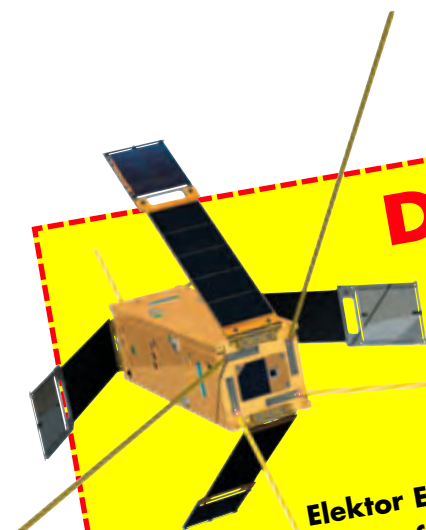Hitching a ride on a launch usually costs between 20,000 and 50,000 dollars. But sometimes, if you're lucky, you can go along with another satellite for free. JAXA (the Japanese space agency), for example, offers a number of free piggyback launches with their H-2A. From 2008 this GOSAT satellite, sponsored by the govern-



Design contest Elektor Electronics in conjunction with NERO

Elektor Electronics magazine stimulates the development and building of your own electronic circuits. NERO does the same with amateur rockets. A design contest forms an interesting combination of these two. In the spring of 2007, NERO, in cooperation with Elektor Electronics, will organise a design contest. The winning design will get a place on board of an amateur rocket, which is intended to break the altitude record in 2008. The rocket will reach an altitude of at least 40 km into the air. Further details still need to be discussed. At the beginning of 2007 we hope to make these public.

ment, will search for greenhouse gas concentrations in the atmosphere. The German Compass-1 group is sponsored by the DLR (Deutsches Zentrum für Luft- und Raumfahrt). In addition, the FachHochschule Aachen also provides a helping hand. The remainder of the money has to be gathered by the boys themselves, from sponsors. In Delft, the TNO, Dutch Space and TUDelft pay for all the costs of the project.

(060227-1)

With thanks to W.J. Ubbels from ISIS [4] (Delfi-C3 team), Jeroen Brinkman from NERO and de COMPASS-1 group from the FH-Aachen.

Weblinks

- [1] www.delfic3.nl
- [2] www.raumfahrt.fh-aachen.de/
- [3] www.amsat.org
- [4] www.isispace.nl

Professional amateurs

In addition to the activity in Delft, there are other projects in the Netherlands related to cheap space travel. From Leiden, the company Delta-Utec has already worked for 10 years with students from all around Europe, building (and launching) satellites. At this moment a second Young Engineers' Satellite (abbreviated to YES2) is being built. The object of this satellite is to show that a wire (tether) can be used to return a satellite back to earth. This works as follows. In a classical balance between gravity and centrifugal force the satellites move in circular orbits, distant satellites move slower than near ones. On the same principle it takes the moon one month to complete one orbit, but the Space shuttle takes only an hour and a half.

If you now lower, on a wire, a light satellite from a heavier one, the lower, lighter satellite, because of the wire, will move at the same speed as the higher, heavier satellite. If you now cut this wire, then the lighter satellite has actually too little speed to maintain its orbit around the earth and will therefore fall back to earth.

For this purpose, the YES2 has a thirty kilometres long Dyneema line on board, which will be used in 2007 to accurately return a small capsule back to earth. This capsule, called Fotino, weighs only 5 kg and is probably the smallest return capsule ever. It is also the first return capsule built by

students. Fotino contains scientific instrumentation to measure all the details of the unique return.


At a late stage it was decided that a parachute system had to be fitted to the Fotino to ensure a soft landing. To make a running start possible a search was made in the Netherlands for expertise in the area of building light parachute systems. This was found quickly at the Netherlands Organisation for Rocket Research (NERO), the pre-eminent Dutch organisation for rocket amateurs. In this organisation there appeared to be plenty of expertise in the area of designing and qualifying of parachute systems. The connections with suppliers and test facilities were also invaluable.

For the amateur rocket enthusiasts from NERO the opportunity to cooperate with real space projects is obviously fantastic. A multi-disciplinary project team has been formed that is supported by Delta-Utec with the design and qualification of the parachute. This system had to be designed and tested according to the requirements of the ESA, in only a few months of available time. That showed that the working procedures of the professional space industry and those of the NERO do not differ all that much. Where the professional space industry does more calculations and simulations, the amateurs do more testing. But the end result is the same: working and qualified systems. And in this way hobbyist and professionals complement each other.

More information:

www.yes2.info

www.nerorockets.org

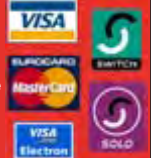

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, unipolar/bipolar stepper motors and servo motors. See website for full details.

NEW! PC / Standalone Unipolar Stepper Motor Driver

Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9Vdc. PCB: 80x50mm.
Kit Order Code: 3179KT - **£11.95**
Assembled Order Code: AS3179 - **£19.95**



NEW! Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer. Supply: 8-30Vdc. PCB: 75x85mm.
Kit Order Code: 3158KT - **£15.95**
Assembled Order Code: AS3158 - **£29.95**



NEW! Bidirectional DC Motor Controller

Controls the speed of most common DC motors (rated up to 16Vdc/5A) in both the forward and reverse direction. The range of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections.
Kit Order Code: 3166KT - **£16.95**
Assembled Order Code: AS3166 - **£25.95**



DC Motor Speed Controller (100V/7.5A)

Control the speed of almost any common DC motor rated up to 100V/7.5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H.
Kit Order Code: 3067KT - **£13.95**
Assembled Order Code: AS3067 - **£20.95**



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU445 £8.95

Serial Isolated I/O Relay Module

Computer controlled 8-channel relay board. 5A mains rated relay outputs. 4 isolated digital inputs. Useful in a variety of control and sensing applications. Controlled via serial port for programming (using our new Windows interface, terminal emulator or batch files). Includes plastic case 130x100x30mm. Supply: 12Vdc/500mA.
Kit Order Code: 3108KT - **£54.95**
Assembled Order Code: AS3108 - **£64.95**



Computer Temperature Data Logger

4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables.
Kit Order Code: 3145KT - **£18.95**
Assembled Order Code: AS3145 - **£25.95**
Additional DS1820 Sensors - **£3.95 each**



Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two and Ten channel versions also available.
Kit Order Code: 3180KT - **£44.95**
Assembled Order Code: AS3180 - **£51.95**



NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. Not BT approved. 130x110x30mm. Power: 12Vdc.
Kit Order Code: 3140KT - **£46.95**
Assembled Order Code: AS3140 - **£64.95**



Infrared RC Relay Board

Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12Vdc/0.5A
Kit Order Code: 3142KT - **£47.95**
Assembled Order Code: AS3142 - **£66.95**



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) **£15.00**
18Vdc Power supply (PSU010) **£19.95**
Leads: Parallel (LDC136) **£4.95** / Serial (LDC441) **£4.95** / USB (LDC644) **£2.95**

NEW! USB & Serial Port PIC Programmer

USB/Serial connection. Header cable for ICSP. Free Windows XP software. Wide range of supported PICs - see website for complete listing. ZIF Socket/USB lead not included. Supply: 16-18Vdc.
Kit Order Code: 3149EKT - **£37.95**
Assembled Order Code: AS3149E - **£52.95**



NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software. ZIF Socket and USB lead not included.
Assembled Order Code: AS3128 - **£44.95**



"PICALL" PIC Programmer

"PICALL" will program virtually all 8 to 40 pin serial-mode AND parallel-mode (PIC16C5x family) programmed PIC micro controllers. Free fully functional software. Blank chip auto detect for super fast bulk programming. Parallel port connection. Supply: 16-18Vdc.
Assembled Order Code: AS3117 - **£24.95**




ATMEL 89xxxx Programmer

Uses serial port and any standard terminal comms program. Program/ Read/ Verify Code Data, Write Fuse/Lock Bits, Erase and Blank Check. 4 LED's display the status. ZIF sockets not included. Supply: 16-18Vdc.
Kit Order Code: 3123KT - **£24.95**
Assembled Order Code: AS3123 - **£34.95**



DiSEqC Monitor

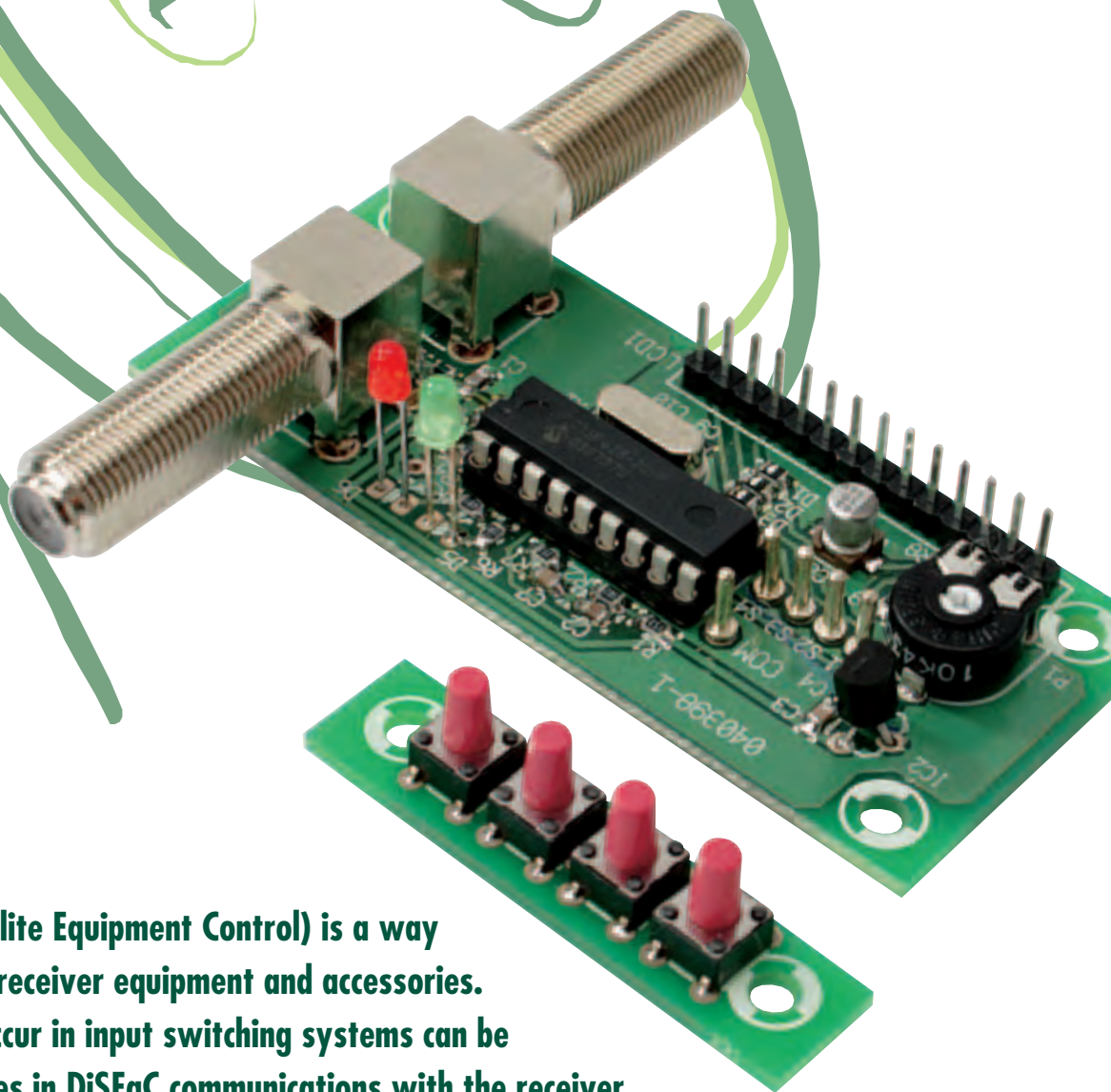PLC listens in on satellite receiver control bus



Wilfried Wätzig

DiSEqC™ (Digital Satellite Equipment Control) is a way of controlling satellite receiver equipment and accessories. Many problems that occur in input switching systems can be tracked down to failures in DiSEqC communications with the receiver. This DiSEqC monitor allows commands on the control bus to be analysed as a first step on the way to finding the fault.

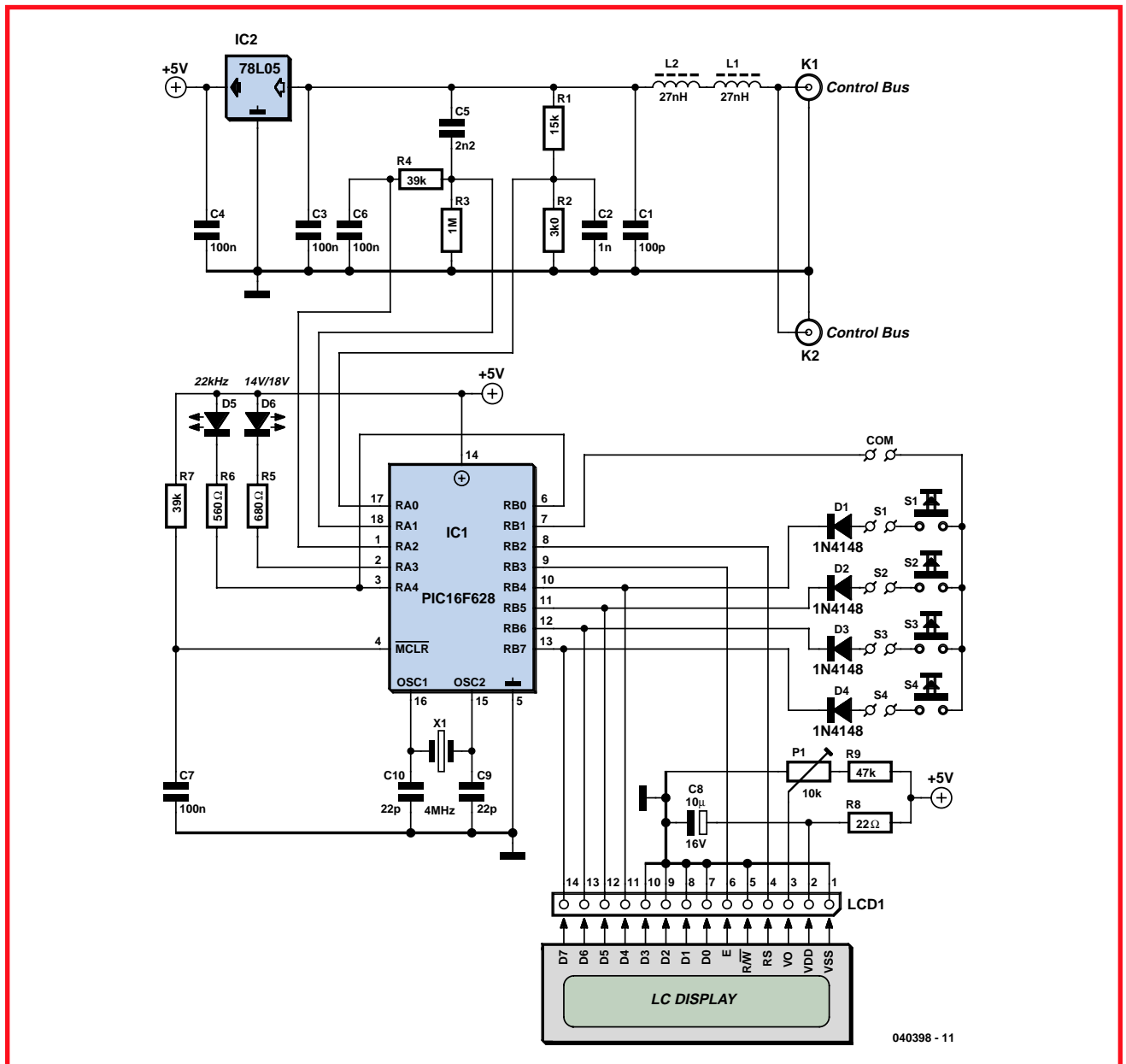


Figure 1. Circuit diagram of the DiSEqC monitor: the PIC microcontroller (or rather its software) is responsible for most of the functions.

In outline a satellite television receiver consists of two parts:

- an outdoor unit with dish and LNB (low noise block converter); and
- the receiver itself.

The two are linked by a coaxial cable which also carries power to the LNB. The LNB acts as a frequency downconverter for the two frequency bands used for satellite TV transmissions:

- low band, approximately 10.7 GHz to 11.8 GHz; and
- high band, approximately 11.7 GHz to 12.75 GHz.

The LNB amplifies the signals received from the satellite and shifts them to a frequency band between 0.95 GHz to 2.15 GHz for the receiver. As is explained in more detail elsewhere in this issue, the polarisation plane of the LNB is set by switching its supply voltage between 14 V (for vertical polarisation) and 18 V (for horizontal). With more than one LNB a switchable 22-kHz signal is superimposed on the supply voltage. If this signal is not present, LNB1 (for example) is selected; if the signal is present, LNB2 is selected. With the introduction of digital satellite television the opportunity was taken to bring all the control

functions together into a single bus, operating over the coaxial cable. This avoids the need for extra control cables, for example in the case of a motorised dish mount. The cable therefore carries:

- power for all the devices (LNB, switch, positioner etc.);
- control functions using the 22 kHz signal; and
- last but not least, the satellite signal down-converted to the 0.95 GHz to 2.15 GHz band.

In order to broaden the possibilities for using multiple satellites and LNBs a

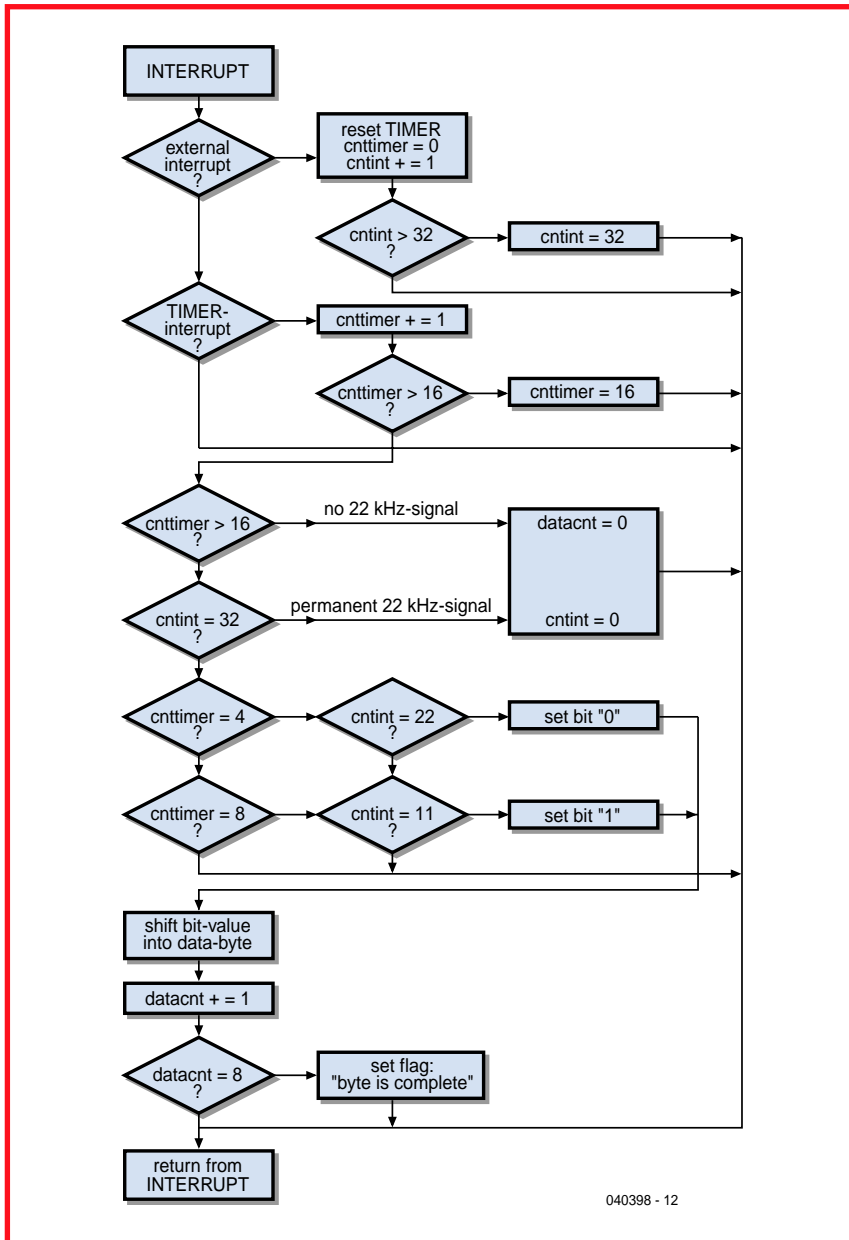


Figure 2. Simplified flowchart of the interrupt routine.

digital control system for the various devices was developed. The so-called DiSEqC system transmits data using amplitude modulation of the 22 kHz signal. Version 2.0 of the protocol was laid down by Eutelsat in 1998 [2].

In theory

The DiSEqC monitor couples a microcontroller to the control bus using a design based on an application circuit provided by Eutelsat [1]. The PIC16F628 is also connected to an LCD module with two rows of 16 characters, which displays the DiSEqC commands. The circuit is inserted in line

with the coaxial cable connecting the satellite equipment and draws power from the bus.

The PIC microcontroller eavesdrops on the bus, listening for control commands which it records in its RAM. Up to 20 DiSEqC commands (80 bytes) can be stored. When recording is over the display shows the individual commands either in hexadecimal or in the abbreviated form given in [2].

The DiSEqC monitor is useful for testing and tracking down control problems. The circuit allows you to check whether the receiver is controlling

satellite equipment such as a DiSEqC switch or LNB correctly.

Hardware

The simplicity of the circuit in **Figure 1** is a consequence of the fact that most of the functions of the unit are carried out in software by the PIC. The few external components are responsible for the following functions:

- coupling of the signals of interest from the control bus (coaxial cable);
- suppressing unwanted HF signals;
- user interface (display and buttons);
- clock generation (quartz crystal).

The connection to the control bus is via the two coaxial F-connectors K1 and K2. Since these are connected directly together, and because the low-pass filter formed by L1, L2 and C1 presents a high impedance, attenuation of the passed-through HF signal is negligible. The filter also removes the HF component from the signal seen by the DiSEqC monitor. The DC voltage of 14 V or 18 V present on the cable, used to supply the LNB, passes through the low-pass filter to voltage regulator IC2, which produces the 5 V supply for the monitor circuit. The LNB supply voltage of 14 V or 18 V is also checked by the PIC microcontroller and the status shown on LED D6. The potential divider formed by R1 and R2 scales the 14 V or 18 V to 2.3 V or 3.0 V for the comparator input RA0 on pin 17. Output RA3 (pin 2) drives LED D6, which lights if the voltage on the coaxial cable is 18 V.

Half the supply voltage, or 2.5 V, appears on RA2, the reference output of the comparators (pin 1). The potential divider formed by R4 and R3 reduces this to 2.34 V at the input to comparator 2 (RA1, pin 18). The 22 kHz signal is also coupled to this input via capacitor C5. When a 22 kHz signal is present output RA4 (pin 3) drives LED D5, as well as generating an interrupt on every rising edge via the connection to input RB0 (pin 6).

The LCD module is driven in 4-bit mode using data outputs RB4 to RB7 and control signals on RB2 and RB3. Buttons S1 to S4 are read in multiplexed fashion using input RB1 and the LCD data lines, with diodes D1 to D4 preventing operation of the buttons from interfering with the display. Quartz crystal X1 may be replaced by

a 4 MHz ceramic resonator if desired; in this case C9 and C10 may be dispensed with.

Bits and bytes

As already noted, the 22 kHz signal, which has a nominal amplitude of $0.65 V_{pp}$, is amplitude modulated to encode DiSEqC commands. A data bit on the bus is formed as follows:

'0' bit: 1.0 ms 22 kHz signal followed by 0.5 ms pause;

'1' bit: 0.5 ms 22 kHz signal followed by 1.0 ms pause.

Each data bit thus lasts 1.5 ms.

A data byte consists of eight data bits and one parity bit P, and therefore has a duration of $9 \cdot 1.5 \text{ ms} = 13.5 \text{ ms}$. The format of the DiSEqC commands is shown in **Table 1**.

Essentially the satellite receiver behaves as the bus master. The address byte selects between the various slave devices (LNBS, polarisers, positioners, switches etc.) and the command byte gives the command.

In version 2.0 of DiSEqC the slave devices can also reply to requests from the master. Some examples of commands from the DiSEqC specification [2] are also given in Table 1.

PIC software

The program in the PIC16F628 can be divided into three functional blocks:

- interrupt handling;
- loop for displaying bytes read and for reading the buttons;
- routines to output values and strings.

The 22 kHz signal generates an external interrupt every $45 \mu\text{s}$ via input bit 0 of PORTB. A continuous 22 kHz tone is recognised when more than 32 consecutive pulses of the 22 kHz signal are received.

TIMER0 counts the duration of the pauses, generating an interrupt every $110 \mu\text{s}$. If more than 16 pause interrupts occur ($16 \times 110 \mu\text{s} = 1760 \mu\text{s}$), this is recognised as a continuous pause in the signal.

A '0' data bit consists of 22 signal pulses and four gaps, while a '1' data bit consists of 11 pulses and eight gaps.

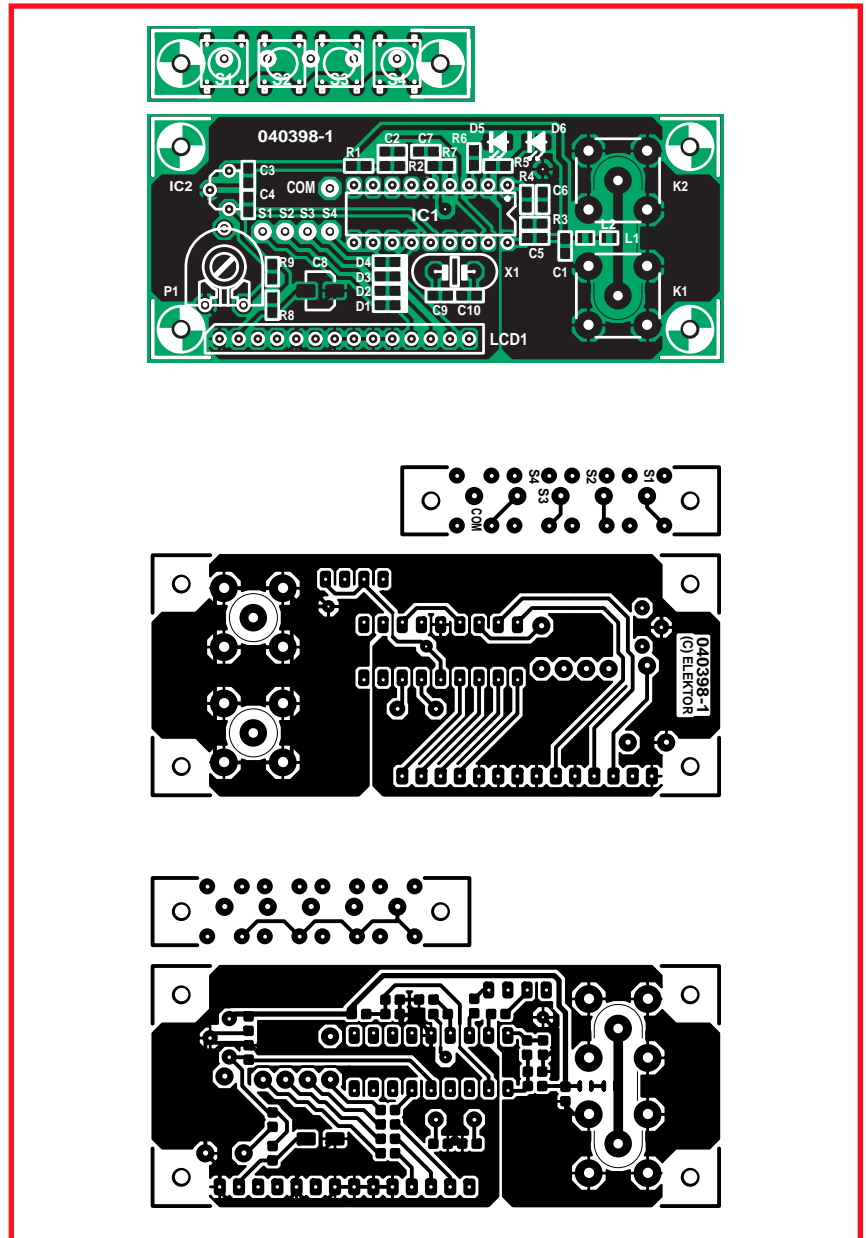


Figure 3. The compact printed circuit board mostly employs SMD components.

The bit values are packed into a byte and checked against the parity bit.

Figure 2 shows a simplified flowchart of the interrupt routine. We will now look briefly at two important parts of the code.

- The **main loop** makes periodic checks to see if a byte has been read or if a button has been pressed. If a byte has been read it is then output on the display. If one of the buttons S1 to S4 has been pressed, control passes to the corresponding routine.
- The **output routines** convert the

byte value into hexadecimal form and, depending on the function, into a command in abbreviated form with four characters (as described in [2]). For example, the command # 7 might be displayed as # 7 E01038F4 (in hexadecimal mode) or as M LNBS wrNO:F4 (in abbreviated form). This stands for 'master (E0) to LNBS (10), write to port group 0 (38), with data F4', meaning that the master (satellite receiver) is instructing all LNBS and switches to 'clear all flags' (nibble F) and 'set flag 2' (nibble 4). In the case of a switch, this command would select an input.

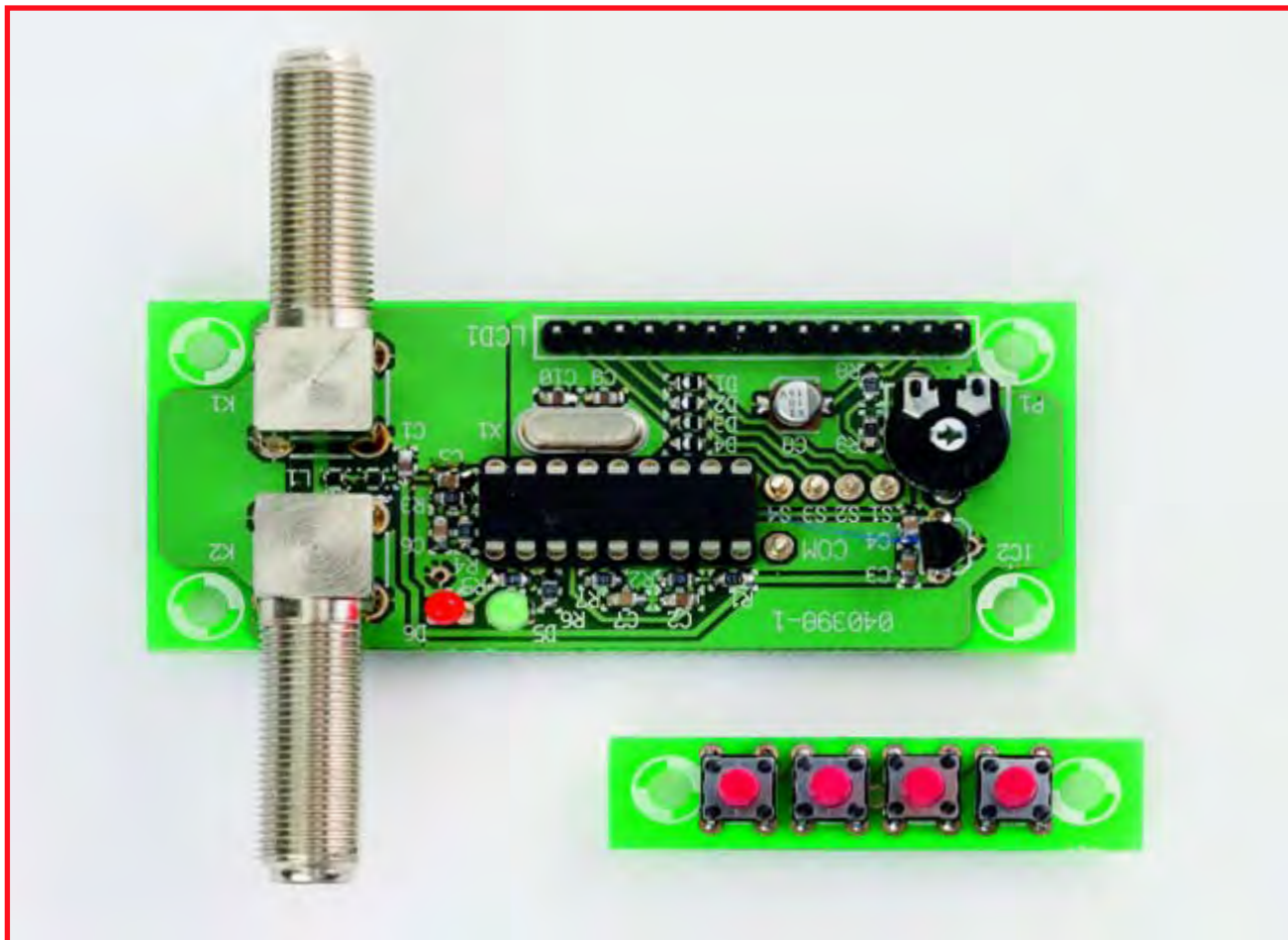


Figure 4. Our assembled prototype board.

Printed circuit board and construction

The printed circuit board (Figure 3) is

very compact and so there should be no difficulty in finding a suitable enclosure. A further feature of the layout is that the F-type sockets can be

mounted at angles of 0, 90 or 180 degrees to one another. The four buttons are arranged on a strip of board that can be detached, allowing other

COMPONENTS LIST

Resistors

(all SMD case 0805 except P1)

- R1 = 15k Ω
- R2 = 3k Ω 0
- R3 = 1M Ω
- R4 = 39k Ω
- R5 = 680 Ω
- R6 = 560 Ω
- R7 = 39k Ω
- R8 = 22 Ω
- R9 = 47k Ω
- P1 = 10k Ω preset

Capacitors

(all SMD case 0805 except C8)

- C1 = 100pF
- C2 = 1nF
- C3,C4,C6,C7 = 100nF
- C5 = 220pF
- C8 = 10 μ F 16V (SMD case B)
- C9,C10 = 27pF

Inductors

L1,L2 = 27 nH ($f_r > 2$ GHz) SMD case 0603 (e.g., Epcos B82496A3270J; Farnell # 158-604)

Semiconductors

D1-D4 = 1N4148, SMD case 0805 (e.g. TS4148, Farnell # 815-0206)

D5 = LED, 3mm, green

D6 = LED, 3mm, red

IC1 = PIC16F628A-20/P, programmed, order code **040398-41**

IC2 = 78L05

Miscellaneous

K1,K2 = F socket, angled, 75 Ω , for PCB mounting (Amphenol; Farnell # 1111377)

S1-S4 = 6-mm pushbutton, 1 make contact, PCB mount (bounce time < 4ms)

X1 = 4MHz quartz crystal

LCD1 = LCD module, 2x16 characters, general purpose 2 14-way pinheader and mating socket for LCD connection (optional, see text)

PCB, ref. 040398-1 from The PCBShop

PIC source and hex files, file # **040398-11**, free download from www.elektor-electronics.co.uk

types of button to be used, hand-wired if necessary.

The LEDs can of course also be mounted on a front panel and hand-wired.

The resonant frequency of the two coils L1 and L2 should lie above the output frequency of the LNB (or LNBs). The EPCOS types specified in the parts list are suitable.

The cathode of the SMD diodes D1 to D4 is marked on the component overlay by a thicker line.

F-type connectors are made by various manufacturers, but unfortunately in diverse pinout arrangements. For this reason we have allowed extra space in the layout. This means that if you use the types specified in the parts list, you should take care when soldering to ensure that they are symmetrically fitted.

The display is connected via 14-way headers (and possibly also a ribbon cable). This allows the display to be easily mounted at a suitable place in the chosen enclosure. Unfortunately not all display modules have the same pinout. It is not possible to use the backlight (if the display has one) as the current drawn from the coaxial cable (and thence from the satellite receiver), and which flows through the 78L05, must be kept to a minimum. The total current consumption of the DiSEqC monitor, including the LCD module (but not its backlight) is only approximately 12 mA. It is of course possible to dispense with the 78L05 and connect a regulated 5 V supply across C4 to avoid loading the satellite control bus. A display backlight could then be used.

Operation

On power-up the monitor is reset by R7 and C7. It initialises itself and shows the message

```
DiSEqC-Monitor
Elektor V.05/06
```

If nothing appears on the display, try adjusting the contrast with P1. The unit then enters data recording mode with the display showing:

```
DiSEqC raw data
```

A '*' character indicates that the bus is active and that the transmitted bytes are stored as raw data in the microcontroller's RAM. They are simultaneously displayed on the LCD in

Table 1. Format of DiSEqC commands

Master Command:	FRAMING IPI ADDRESS IPI COMMAND IPI DATA IPI	
Byte 1: framing byte	'E0' to 'E3' = master	
Byte 2: address byte	upper nibble: family (LNB, positioner, etc.) lower nibble: sub-type	
Byte 3: command byte	standardised command	
Byte 4: data byte	command-dependent data	
Byte 5: data byte	command-dependent data	
Slave reply:	FRAMING IPI DATA IPI DATA IPI	
Byte 1: framing byte	'E4' to 'E7' = slave	
Byte 2: data byte	command-dependent reply data	
Byte 3: data byte	command-dependent reply data	
Examples:		
Byte	Command name	Meaning
20	Set Lo	LNB: select low frequency band
24	Set Hi	LNB: select high frequency band
21	Set VR	LNB: vertical polarisation
25	Set HL	LNB: horizontal polarisation
38	Write NO	Switches: set four signals 'WXYZ'
Subsequent data byte:		upper nibble: clear 'WXYZ' lower nibble: set 'WXYZ'

hexadecimal form. When the RAM buffer becomes full the device automatically exits recording mode. Button S1 allows recording to be stopped and restarted. In display mode (when recording is complete) the individual DiSEqC commands, each beginning with the 'E0' framing byte, can be displayed in sequence either in forwards (button S2) or reverse (button

S3) order. Button S4 selects whether the commands are displayed in abbreviated form. Further information on satellite reception and DiSEqC commands can be found on the Eutelsat website.

(040398-1)

References and downloads

- [1] Application Information for Using a 'PIC' Microcontroller in DiSEqC™ LNB and Simple Switcher Applications (1999), PDF available from www.eutelsat.com
- [2] DiSEqC Bus Functional Specification V. 4.2 (1998), PDF available from www.eutelsat.com
- [3] Source and object files for the PIC16F628: free download from www.elektor-electronics.co.uk

E-blocks Easy ARM

John Dobson

With the introduction of an ARM-based development board, there are now three E-blocks processor platforms to choose from: PIC, AVR and ARM. The latter is a class of its own due to speed and raw processing power.

When explaining what a microcontroller is to those who have some electronics experience but who don't actually use microcontrollers I often explain it like this: if you remember back to when you had a Z80 or 6502 processor, connected to a serial I/O chip, EPROM chips, RAM chips and assorted glue logic on a double sided Eurocard: well a microcontroller performs the same function as the whole card but it is contained on just one chip. With the arrival of the Atmel ARM7 the word 'microcontroller' just took on a whole new meaning so I am going to have to think of a new metaphor. Something like: 'remember the first '386 motherboards? Well now you have the equivalent of a complete motherboard on one chip.' would be a closer approximation to describing this device. Let me explain.

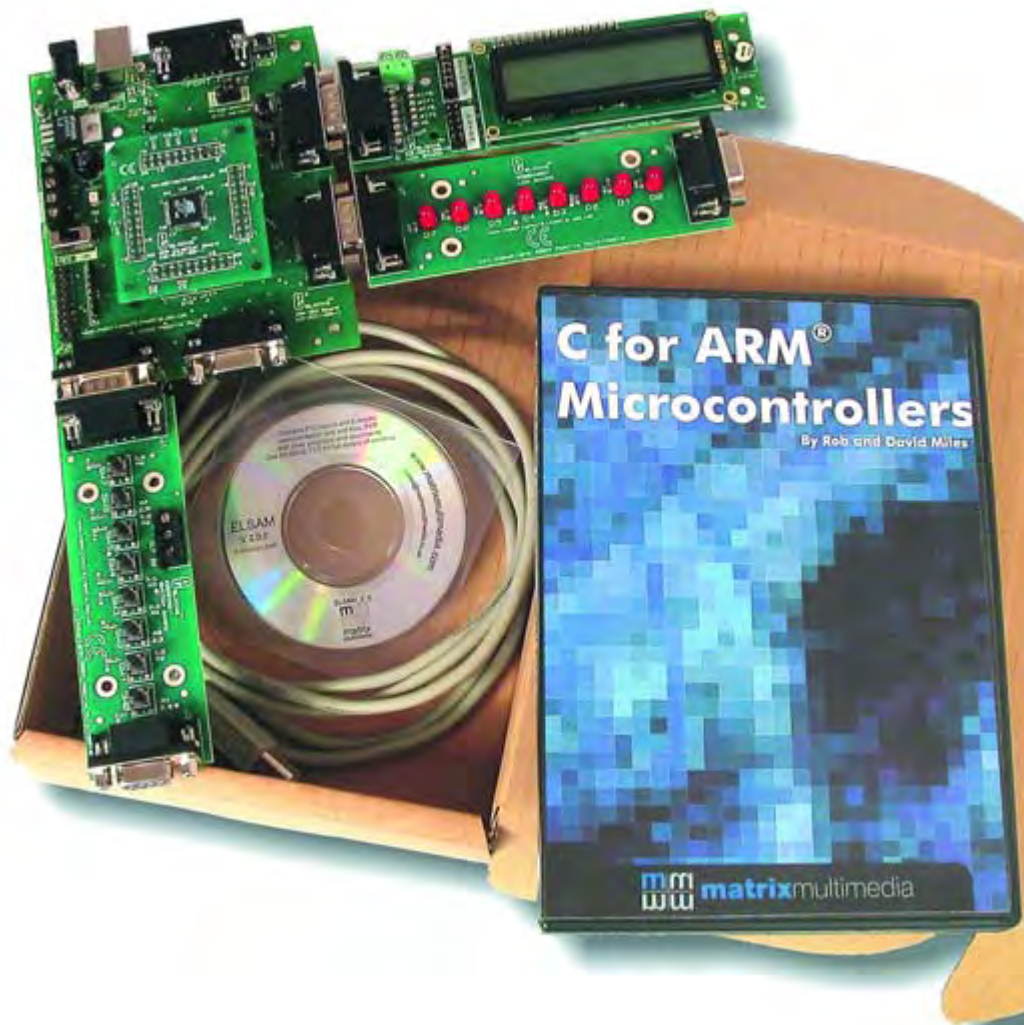


Table 1. AT91SAM7S128 quick features list

- 128 k flash ROM
- 32 k RAM
- 80 MHz internal clock speed
- 2 USARTs
- USB programming and communications interface
- 32 I/O lines
- 4-channel 16-bit PWM outputs
- 32-bit processor
- 8 x 300-kHz 10-bit A/D converters

The AT91SAM7

Until recently the ARM has still been out of reach of the non-specialist microcontroller programmer but a number of changes mean that a low cost solution

to developing projects with ARM cores in is now open to everyone. In this respect, the *Elektor Electronics* ARMee Development Sytem [1] based on the Philips LPC210x ARM CPU was a ground breaking publication.

Pack

C compiler included — it's a beast!

Firstly, developments in higher resolution semiconductor masks have meant that it is now possible to squeeze more transistors onto a given area of silicon. Users of integrated circuits effectively pay for the cost of the silicon inside the device and the packaging: so a smaller area of silicon used means lower cost. The ARM device detailed here costs only £6.50, or around 10 euros each. There is a down side here: squeezing more transistors into a given area means that the available power dissipation of the device reduces: cleverly the ARM designers have compensated for this by reducing the internal operating voltage down to 1.8 V, which means that the transistors in the chip use only an eighth of the power of a similar 5 V device. To help you along a little the device has peripheral circuitry that presents the i/o lines at a level of 3.3 V at the point where they interface to the outside world, and these i/o lines are 5 V tolerant (inputs to the micro are compatible with existing circuitry, but the output lines will only give 3.3 V).

Secondly, Atmel have released a series of devices which have built in USB 2.0 support. As a result, you don't need an expensive programmer — although if you have a JTAG programmer the device can also be programmed that way. With an appropriate shell program inside the device you can simply connect the ARM to your PC and download your program. This also allows engineers to add USB functionality to Atmel AT91SAM7 projects. USB is not the only trick up Atmel's sleeve — in fact the (greatly) abbreviated features list reads like something from an engineer's letter to Santa Clause — see **Table 1!**

If you are used to programming PIC micros, 8051 cores, or other Atmel 8-bit devices then you will agree that the AT91SAM7S128 is a real beast! Unfortunately for us, Atmel are only making these devices available in high density surface mounted packages — in this case the dreaded '64-pin LQFP' pack-

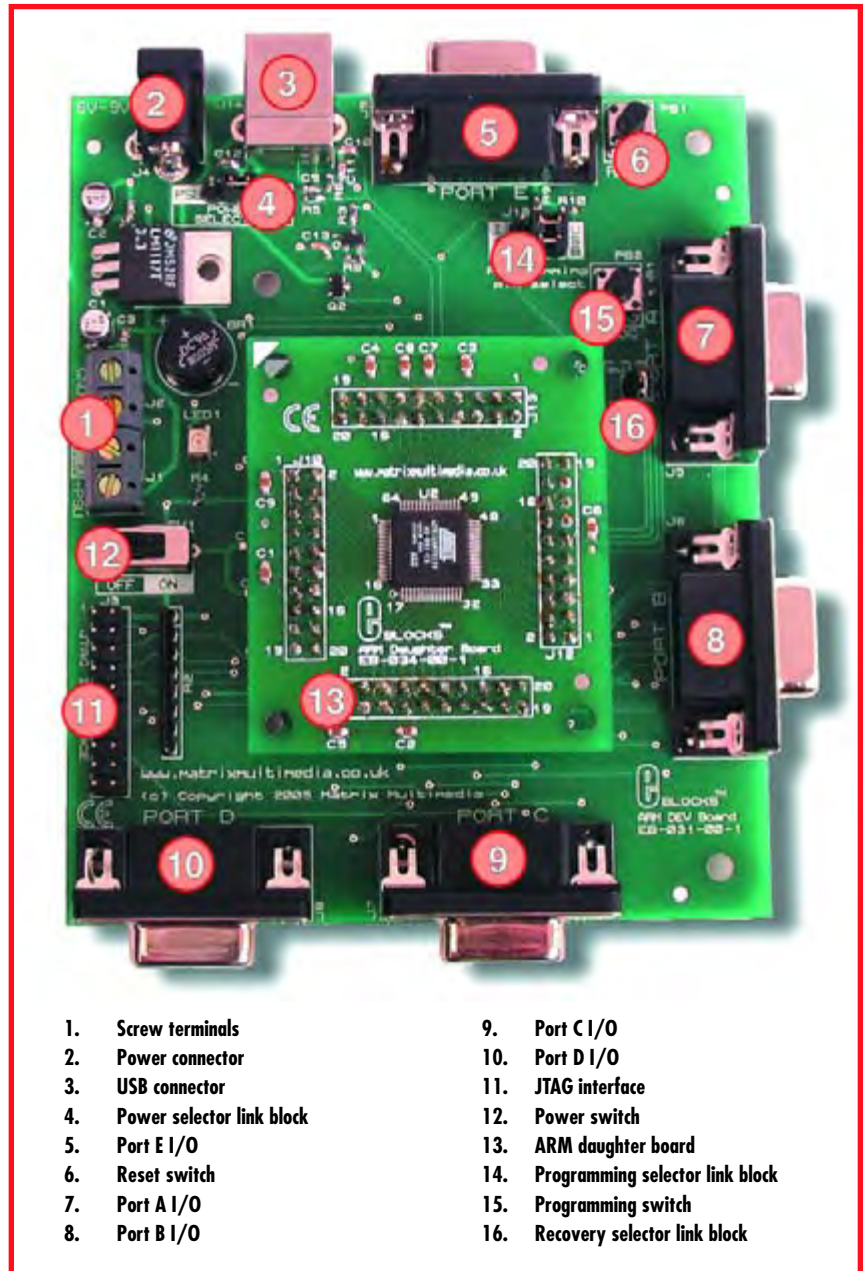


Figure 1. The ARM mother and daughter board

age. On this package, the pins are so close together that manual soldering is a bit of a lottery which brings us to our next point:

The third change here is that a low cost development platform has been

developed for the E-blocks range of products. This solves a few problems: the hardware solution contains two printed circuit boards: the device itself is placed on a daughter board which sits on top of a mother board — see **Figure 1.** The daughter board has

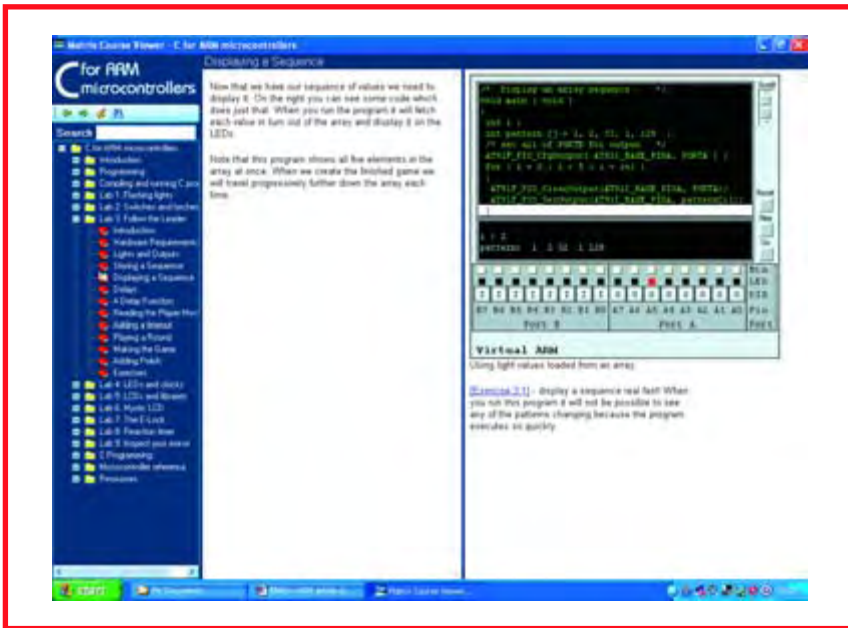


Figure 2. A screen image of the course showing the virtual ARM.

several rows of standard PCB headers with 0.1-inch pin spacing so that it can be placed on to project boards and effectively used as a component in its own right, making the technology readily usable in a range of projects.

The Atmel AT91SAM7S128 on the daughter board is programmed with a custom made bootloader program and a Windows application which allows you to easily download binary files into the device via USB onto the motherboard. The E-blocks motherboard has five E-blocks ports presenting the I/O lines on the rugged 9-way sub-D type connectors, a power supply input and a USB connector. The connections on these ports are optimised so that users can take advantage of the 25+ E-blocks downstream boards which contain a range of peripherals from simple LED boards to more complex system modules like Bluetooth, IrDA, and CAN bus. All E-blocks and related products may be found in the SHOP section of www.elektor-electronics.co.uk.

Learning ARM programming

Finally, a new CD ROM called 'C Programming for ARM Microcontrollers' has been developed which provides you with a C compiler, an Integrated Development Environment and an on-screen full course on programming the ARM device. The course is a key element of this package which is part tutorial and part off-the-shelf design elements you can use. The on-screen course also includes a number of virtual ARM simulations which will allow you to more easily understand the programming concepts involved. This is illustrated in **Figure 2**.

The CD-ROM based course also links seamlessly to a compiler and IDE which are supplied along with a number of C code examples that show you how to develop a range of programs for the ARM. These range from very simple tasks, starting with lighting a LED on a single output pin, through to tasks of medium complexity, such as programs to control LCDs using serial communications. The C compiler is based on the open source GNU compiler and it is possible to add other licence free GNU code libraries to this. An added bonus here is that the floating point library is already included in the compiler set up and the system is able to execute full floating point arithmetic.

```
int main(void)
{
    /* Set all of PORTA as an output */
    AT91F_PIO_CfgOutput( AT91C_BASE_PIOA, PORTA ) ;

    while ( 1 )
    {
        /* Set pin 0 of PORTA high */
        AT91F_PIO_SetOutput( AT91C_BASE_PIOA, PORTA0 ) ;

        /* Set pin 0 of PORTA low */
        AT91F_PIO_ClearOutput( AT91C_BASE_PIOA, PORTA0 ) ;
    }
}
```

Figure 3. A simple LED flasher routine on pin 'A0'.

ARMed with some history

The AT91SAM7 series of devices from Atmel is based on the ARM7TDMI core developed by ARM (Advanced RISC Machines Ltd.) in England. ARM, based in Cambridge, is one of the UK's greatest technology success stories of the last decade. Spun off from a company that was an original competitor of the IBM PC and Apple back in the early 80's — Acorn Computers — the ARM team of developers has become one of the world's leading designers of microprocessor cores. Unlike its competitors ARM does not manufacture any devices itself. Instead it develops the designs of microprocessors which it then licences to other IC manufacturers — including Philips, Texas Instruments and, in this case, Atmel. This business model has made ARM amazingly successful. Virtually every major semiconductor company has taken out a licence for an ARM core and many millions of ARM processors are now in use. The mobile phone industry in particular has adopted the ARM as a near de facto standard for use in mobile devices because of the ARM's ultra-low power consumption and huge processing power, and you will find ARM cores in your iPod and Gameboy Advanced.

Great strides: from 8 bit to 32 bit

The ARM is a 32-bit core which means greater processing power and support for a larger variable range and advanced mathematical operations, floating point etc. But when you just want to control eight bits on a port then writing and reading 32 bit words to memory addresses can become a little unwieldy. To get round this the CD ROM also has an 'include' file and a range of pre-written functions that allow you to use the I/O pins on the ARM like a more simple 8-bit device with ports A to E — a little like a PIC micro. These routines give you a good head start in using the ARM and also mean that your current 8 bit programs and routines can be easily ported to the ARM platform.

To give you an example of this, in **Figure 3** you can see a sample of a routine to flash a LED on port A. This is the entire program as all memory loca-

tion addresses and functions are defined for you in a separate file. If you are an 8-bit user you will notice that some of the strings used here, for example 'AT91F_PIO_SetOutput', seem a little long winded, and you might think a simple 'SetOutput' would do. However the CD-ROM's authors, Rob and David Miles, have kept the syntax of the basic functions and variables in the same style as Atmel's own code libraries. Whilst this may take you a little longer to get used to it means that what you learn in taking the course is immediately transferable to any of the Atmel ARM devices as they all share similar configurations.

Easy ARM pack

To help you get started with the ARM we have produced an Easy ARM Kit that is now available. It contains a USB lead, ARM motherboard, ARM daughter board, LED board, Switch board, and LCD board as well as a 'C Programming for ARM microcontrollers'

CD ROM. For price and ordering details, please visit the SHOP section of the Publishers' website.

Conclusion

The low-cost and high processing power of the ARM core is making it one of the most popular processors in industry today. Whilst many hobbyists and small companies have yet to start using ARMs, the ATMEL device discussed here has so many benefits to offer, that we think it will not be long before ARMs are one of the most popular processors for our readers too.

(065069-1)

Reference

[1]. ARM Development System, Elektor Electronics April and May 2005.

Advertisement

THE VERY BEST GCTV AT LOW PRICES

SYSTEM 461. 4 COLOUR CAMERAS + DVR PACKAGE
FEATURING LATEST JPG 2000 DUPLEX DVR WITH 100 FPS + CDR



SYSTEM INCLUDES:
4 hi-res indoor domes, Super 4 channel 100 FPS JPG 2000 duplex DVR with 160GB hard-drive (upgrades available) with CDR, 100M of RG59 coax cable + all necessary power supplies & connectors.

EASY TO INSTALL
Add a selection of high quality CCTV equipment...

SAVE £87
+ VAT

£ 438

SYSTEM 463. 4 COLOUR CAMERAS + DVR PACKAGE
FEATURING LATEST JPG 2000 DUPLEX DVR WITH 100 FPS + CDR



SYSTEM INCLUDES:
2 hi-res exterior 15m day & night cameras + 2 hi-res indoor domes, Super 4 channel 100 FPS, JPG 2000 duplex DVR with 160GB hard-drive (upgrades available) with CDR, 100M of RG59 coax cable + all necessary power supplies & connectors.

SAVE £80
+ VAT

£ 489

SYSTEM 905. 9 COLOUR CAMERAS + DVR PACKAGE



SYSTEM INCLUDES:
3 hi-res exterior day & night cameras + 6 hi-res indoor domes, 16 channel DVR with 160GB hard-drive (upgrades available), 100M of RG59 coax cable + all necessary power supplies & connectors.

SAVE £91
+ VAT

£ 799

All items are available separately... Call now for a free new product brochure

CRICKLEWOOD ELECTRONICS tel: 020 8450 0995

Web site: <http://www.cricklewoodelectronics.com> Fax: 020 828 1481

School of Technology

 UNIVERSITY
of DERBY

Are you passionate about your electronics?
Do you love building kit, and making things work?
Do you want a career, getting paid for what you enjoy doing?

Yes to all of these?

Then upgrade your qualifications, by studying at Derby

BSc(Hons) Electronics
BSc(Hons) Electrical & Electronic Engineering

Also Foundation Year, and HNC/HND Electrical & Electronic Engineering

- For people who love electronics, taught by people who love electronics
- Part-time and full-time study modes available
- Flexible entry qualifications, with recognition of current experience
- Easy upgrades from HNC to HND to BSc (Honours)
- Final Year options give specialist training in key topics, like digital signal processing, embedded systems, EMC, or power electronics

For further details view: <http://vertigo.derby.ac.uk/> and email or phone:
Dr Amar Bousbaine: a.bousbaine@derby.ac.uk 01332 591760 OR
Tim Wilmshurst: t.j.wilmshurst@derby.ac.uk 01332 591350



University of Derby, Kedleston Road, Derby. DE22 1GB. UK



Upgrade for Flash M

Burkhard Kainka

MICROCONTROLLER BASICS

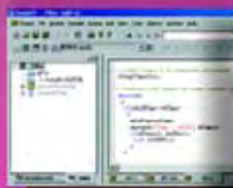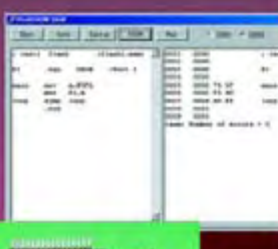

AT89S8253 supersedes AT89S8252

Burkhard Kainka

The popular AT89S8252 Flash Microcontroller Board published in the December 2001 issue of *Elektor Electronics* was developed for the 'Microcontroller Basics' course. Since then many thousands of the boards have been built. First, the bad news: Atmel have made the AT89S8252 obsolete! But now the good news: not only is the pin-compatible AT89S8253 a drop-in replacement, but it even offers enhancements over its predecessor.

Microcontroller Board

The most significant improvements are a larger flash memory, a page mode for faster programming and the option of a factor of two increase in processing speed. The table gives an overview of the new features.

A first test to show that we can replace the AT89S8252 with the AT89S8253 is as follows: take the 52-series microcontroller out of its socket, insert the 53-series device, program it with the old firmware and start it running. Everything should work exactly as before.

There is a small difference between the two devices regarding the crystal oscillator. A reduced lower supply voltage threshold and a new power-saving mode have necessitated changes to the oscillator circuit. The recommended values for the circuit around the crystal (C1 and C2 on the printed circuit board) are now 5 pF \pm 5 pF. The 22 pF capacitors previously used can be simply removed. This is not compulsory, however, as the 11.0592 MHz crystal used will still oscillate perfectly well with 22 pF capacitors connected. No changes should be made if it is desired to be able to use either the new or the old microcontroller in the same board.

Programming software

The AT89S8252 was rather slow to program, which was particularly noticeable when a full 8 kbytes of data were to be transferred. Time is money, and so Atmel have addressed this problem. The programming interface has been thoroughly overhauled: there is a new protocol which uses 'Page Mode'. A total of 64 bytes can be loaded in one operation, and then these bytes can be simultaneously programmed into the microcontroller. This makes programming much faster. While the old microcontroller took at least 12 seconds to program 8 kbytes, the new version can program the full 12 kbytes in under a second. New programming software is required to take advantage of this new mode. The most recent version of the program AtmelISP.exe (Figure 1) by Ulrich Bangert (DF6JB) already supports the new chip: simply select the desired microcontroller device and hardware code 'DK7JD' (for the *Elektor Electronics* Flash Microcontroller Board). On some PCs you may also have to set a larger 'clock delay' value. The system will then work as before. In the 'Microcontroller Basics' course we used two special download tools for the AT89S8252. These have to be replaced for use with the AT89S8253. MicroFlash53 is the new programming tool specific to the AT89S8253 (Figure 2). It allows hex or binary files up to 12 kbytes in size to be transferred.

The TASMEdit program was designed to allow easy programming in assembler. There is also a new version of this program, TASMEdit53, for the AT89S8253 (Figure 3).

If you wish to write your own programming software, you must use the new four-byte protocol in place of the previous three-byte protocol. Also, it is no longer possible to simply overwrite old bytes in memory with new, since this

Enhancements

AT89S5253 versus AT89S5252:

- 12 kbytes of flash memory instead of 8 kbytes
- Page Mode for faster programming
- Doubled processing speed using X2 clock option
- Power-on reset function and brown-out detection
- Supply voltage from 2.7 V to 5.5 V

function is not available in the new block mode. Instead the entire flash memory must be erased using a 'Chip Erase' command before programming can commence. After erasure the device must be reset and programming mode re-entered. On leaving the reset state a small delay is needed to allow the reset capacitor on the board to charge. Listing 1 and Listing 2 show the relevant lines from the Delphi source code of the new software.

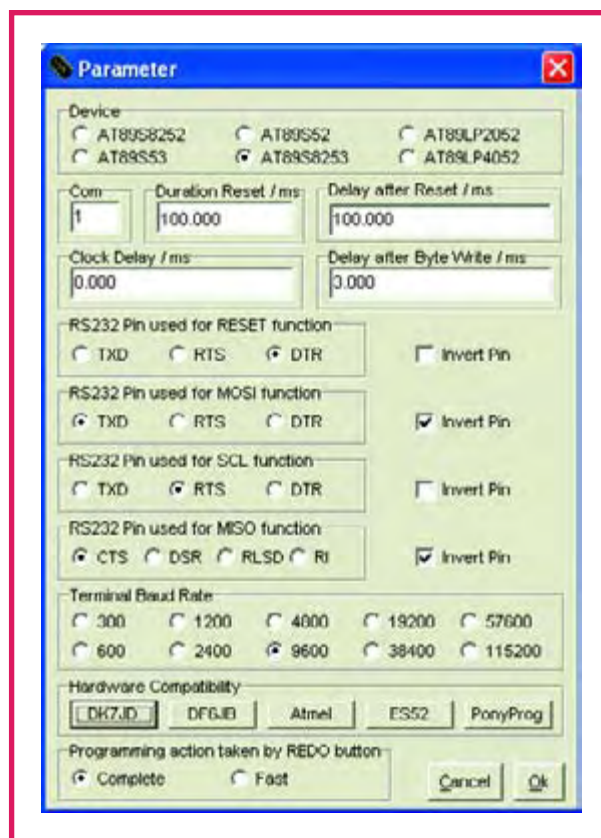


Figure 1. AtmelISP.exe


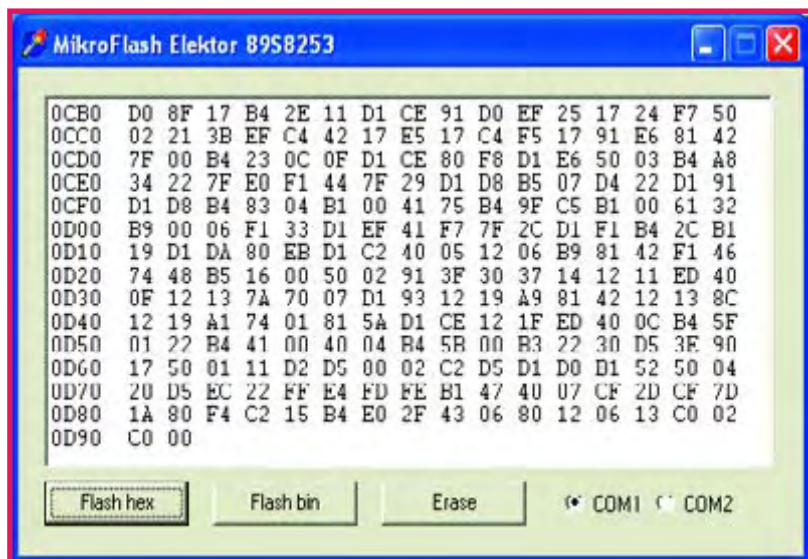


Figure 2. MikroFlash53.exe

Double speed

The AT89S8253 uses an improved version of the 8051 core. One processor cycle now takes only six clock periods rather than the previous twelve. The microcontroller is thus twice as fast as before, although this is not immediately noticeable, since the clock generated by the crystal oscillator is internally divided by two. However, there is a new register called CLKREG at address 08Fh, and bit 0 of this register, X2, can be used to switch out the divider. When the microcontroller is reset CLKREG is cleared to zero. The X2 bit is therefore zero and the divider is switched in. Since CLKREG can only be accessed as an entire byte, all eight bits must be written at once: bits 1 to 7 are 'don't care'. It is sufficient to write the value 1 into the CLKREG register to switch the processor to double speed.

Figure 3. TASMedit53.exe

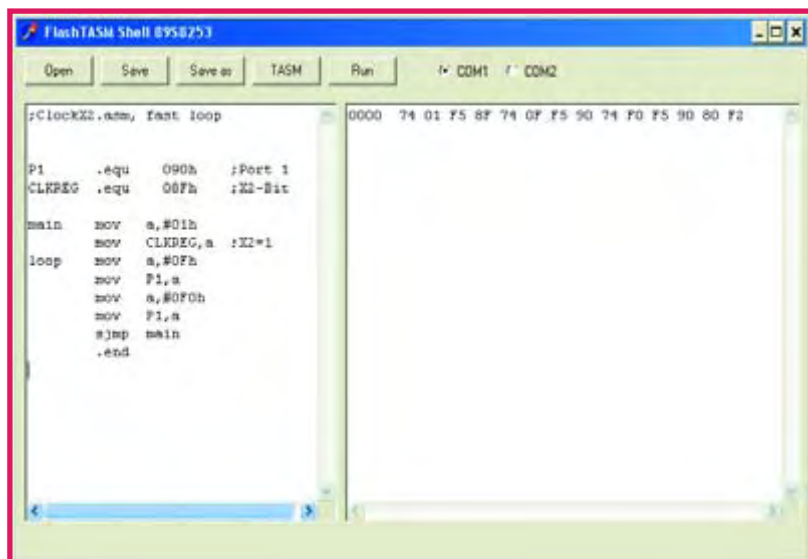

```
CLKREG .equ 08Fh ;X2 bit
mov a,#01h
mov CLKREG,a ;X2=1
```

The maximum clock speed is 24 MHz. If the X2 bit is set, the crystal frequency should not exceed 12 MHz. Since a crystal with a frequency of 11.0592 MHz is used on the flash microcontroller board, the X2 bit can safely be set.

With just three extra lines of code every program can run twice as fast as before!

Supply voltage and brown-out

The new microcontroller operates from a supply voltage of between 2.7 V and 5 V. The flash microcontroller board is based on a 5 V supply, and so a microcontroller can be programmed and tested using the board and then transferred to target hardware with a lower supply voltage.

The reset circuit has been extended to include a power-on reset function, and so the reset capacitor can be dispensed with. When power is applied the processor automatically enters the reset state for a millisecond. In addition to the reset circuit is a brown-out detection mechanism with a trigger threshold of 2.2 V. As soon as the supply voltage falls below 2.2 V the device is reset. This gives good reliability without the need for an external voltage monitor.

Conclusion

The new microcontroller is a significant upgrade to the popular *Elektor Electronics* Flash Microcontroller Board. It is compatible with all its predecessor's functions and with the programming course without modifications. An important aspect is security of supply: since the new microcontroller has only just been introduced, it should with luck be some years before it becomes obsolete itself!

(060052-1)

Downloads:

The most recent version of AtmelISP can be downloaded from the FAQ page for the 'Microcontroller Basics' course book:
www.b-kainka.de/basismifaq.htm
 (site in German only).

The modified programming software for the 'Microcontroller Basics' course to suit the AT89S8253 can be downloaded from the Elektor Electronics website as file number
 060052-11.zip.

Follow Magazine → April 2006 → Upgrade for Flash Microcontroller Board.

ELEKTOR AUDIO BOOKS 3 must-haves for all audio-enthusiasts!

Build your own Audio Valve Amplifiers

To many people, the thermionic valve or electron tube is history. However, whether it is nostalgia, interest in the technical parameters, the appeal of a gleaming amplifier chassis with softly glowing valves or perhaps the firm conviction that the sound of a valve cannot be bettered, it is a fact that the valve is making a come-back. This book contains, apart from construction projects for preamplifiers, power amplifiers, and



amplifiers for musical instruments, information on the operation of electron tubes, while the first chapter gives a short history of the valve.

ISBN 0 905705 39 4
253 Pages
£15.55 (US\$31.00)

Modern High-end Valve Amplifiers

Valve amplifiers are regarded by many to be the ne plus ultra when it comes to processing audio signals. The combination of classical technology and modern components has resulted in a revival of the valve amplifier. The use of toroidal-core output transformers, developed by the author over the past 15 years, has contributed to this revival. This book explains the whys and wherefores of toroidal output transformers at various technical levels and offers innovative solutions for achieving perfect audio quality.



ISBN 0 905705 63 7
264 Pages
£25.95 (US\$52.00)

Build your own High-End Audio Equipment


The name high-end equipment is a good indication of the prices charged for it. For those who cannot, or will not, pay these high prices, there is a solution offered in this book: build your own at considerable cost savings. This book is aimed not only at this sector of the market, but also at the many enthusiasts who want to be able to experiment and to make their own modifications to their high-end equipment. Contents include solid-state and valve preamplifiers and power amplifiers, active cross-over filters, an active subwoofer, a headphone amplifier and more.



ISBN 0 905705 40 8
262 Pages
£15.55 (US\$31.00)

C Compiler Applications for PIC & AVR Microcontrollers

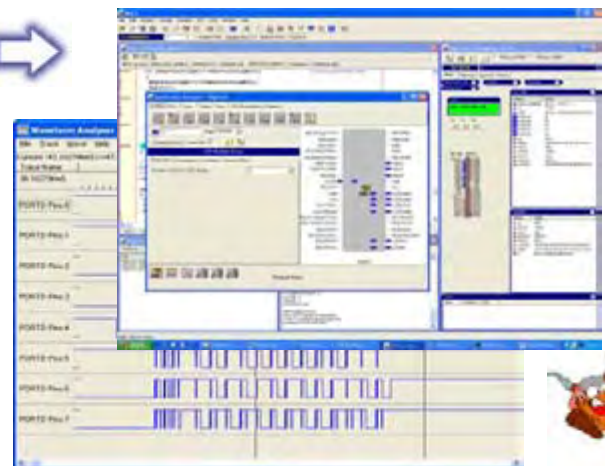- Complete ANSI C Compiler Development Environments for PIC and AVR
- Rapid Application Designer (RAD) front end - the fastest way to fully working code
- Drag & Drop interface into library routines and hardware drivers
- Link C functions into hardware events
- Hugely featured Simulator including Logic Analyser and big range of external devices



Our development systems are standalone and include RAD front end, compiler, assembler and simulator. All systems include elements/library functions for Timers, Ports, A/D, SPI, I2C, USART, Watchdog, Delays, USB, PWM, Capture, Compare, Oscillator functions, Voltage Ref, LCD modules, 7 Segment Displays, Graphic LCD, ANSI libraries and many more



Forest Electronics
www.fored.co.uk
sales@fored.co.uk
01590 - 681511

WIZ-C
Priced from
£35 to £100

FED Support the complete development Lifecycle



Learn Free manuals including C tutorials for the PIC/AVR



Design RAD front end to WIZ-C



Develop Complete integrated development environment (IDE)



Simulate Fast simulator with huge range of device types



Prototype We supply a variety of prototyping boards



Program Forest have Serial, USB and In Circuit Programmers

Debug In Circuit Debugging operates with all our IDE's

FPGA Course (4)

Paul Goossens

Welcome back to the beginner-friendly course we run in support of our extremely popular FPGA Development System. This month we examine the simulation capabilities of Quartus. Simulation makes it a lot easier to design circuits and track down errors in your designs. The accompanying examples show how you can use the audio interface of the prototyping board.



It's handy to be able to test your design during the design process. VHDL allows you to create test benches, which make it a lot easier to test and simulate VHDL designs. Unfortunately, Quartus does not support VHDL test benches. It has a graphic simulator instead. Although the simulator provides less user functionality, it is easier to use. The simulator is more than adequate for most of the sample applications in this course.

Virtual

The simulator is actually a combination of a virtual signal generator and a logic analyser. Here we use it to simulate the operation of an audio interface implemented with the hardware.

Codec

The 'ex10' sample application described in this instalment uses the

audio codec (IC12) on the prototyping board. From the schematic diagram, you can see that a 12.288-MHz clock signal is applied to this IC. The clock signal is also routed to an I/O pin (B12) of the FPGA. Unfortunately, that was not shown in the original schematic diagram.

The data transfer clock (BCKIN) is supplied by the FPGA. This clock signal must be synchronised to the 12.288-MHz clock signal.

The timing diagram for data transfers between the codec and the FPGA is shown in **Figure 1**. As you can easily see, it takes 156 clock pulses of the CODECCLK signal to transfer a set of samples for the two channels.

The frequency of that signal on the prototyping board is 12.288 MHz. If you divide that figure by 256, you arrive at a sampling rate of 48 kHz.

Counter


All communications are synchronised to this clock. The simplest approach is to first create a counter that counts how many pulses of the CODECCLK signal have been generated. This signal is assigned the name '12_288MHz' in our design.

This counter is also represented by the COUNT signal in the PCM3006.VHD file, which is declared on line 54 as an 8-bit unsigned number. This signal can thus take on values the range of 0–255, which is exactly what we need.

We let this number increment in synchronization with the CLK signal (12.288 MHz).

The NEW_COUNT signal always contains the value that COUNT must assume on the next clock pulse. This is done by the following line:

```
NEW_COUNT <=
(COUNT+1) MOD 256;
```

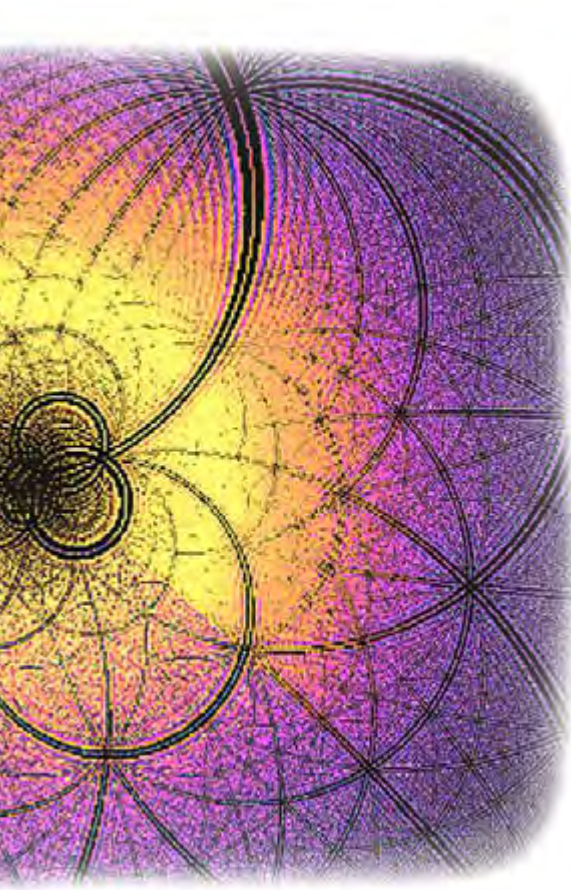

Part 4: Simulation

This line is not in a process, so the function is evaluated each time COUNT changes.

The value of NEW_COUNT is loaded synchronously into COUNT in line 71.

Simulation

Now you can test this code using the Quartus simulator. For that purpose, we created a simulation file named 'ex10-1.vwf'. If you open this file, you will see several signals in the left-hand column and plots of the input signals versus time on the right.

Before you can use this file, you must configure Quartus so the simulator can use the file.

To do that, select 'Settings' in the 'Assignments' menu. In the new window that appears, select 'Simulator Settings'. Enter the file name 'ex10-1.vwf' in the Simulation Input box.

The simulation starts as soon as you select 'Start Simulator' in the 'Processing' menu. The result of the simulation (Figure 2) is displayed after the simulation is completed.

What matters at this point is the COUNT signal. As you can see from the simulation results, this counter is indeed incremented by 1 each time a rising edge occurs on the 12.288-MHz signal line. Note that COUNT has been changed to a 7-bit number due to optimization. Later on we'll explain why that is possible. What matters now is that the counter is synchronized to the clock.

Alias

The next step is to generate the data transmission clock (BCKIN). This signal must be low for two clock intervals of the main clock signal, after which it must be high for two clock intervals. That corresponds exactly to the third bit of the COUNT signal. This signal (called BCKOUT in the VHDL file) can thus be used at the output without any further processing.

The same holds true for the LRCK signal. This signal must be low for the first 128 clock pulses and then high for the following 128 clock pulses. That corresponds exactly to the most significant bit (highest-order bit) of the COUNT signal. That means you can use bit 7 of the COUNT signal as LRCKOUT.

The new status of LRCKOUT can be defined using the following line:

```
NEW_LRCKOUT <=
NEW_COUNT(7);
```

Another way to do this is to use the 'alias' keyword, which allows a signal to have more than one name. If you write

```
ALIAS NEW_LRCKOUT : STD_LOGIC IS
NEW_COUNT(7);
```

you can use the signal NEW_LRCKOUT in the rest of the source code. The compiler will know that this signal is identical to NEW_COUNT(7).

Synchronous

Data bit reception is synchronised to the rising edge of BCK. The signal POSEDGE_BCK is used to detect the rising edge of BCK. It must indicate whether the BCK signal changes from low to high on the next rising edge of the system clock.

That requires knowing the current status of BCK and the status after the next clock pulse. These signals are COUNT(2) and NEW_COUNT(2), which are also assigned the names BCK_INT and NEW_BCK by alias statements in lines 62 and 63.

The POSEDGE_BCK signal is generated by the following line:

```
POSEDGE_BCK <= NEW_BCKOUT
AND (NOT BCKOUT_INT);
```

Data must be sent on the falling edge of BCK as shown in Figure 2. The signal NEGEDGE_BCK is generated in a similar manner for his purpose.

Glitches

Now it's time to look at these new signals in more detail. First configure the settings to have the simulator use the file ex10.vwf, and then start the simulation.

You will see the signals NEGEDGE_BCK, POSEDGE_BCK and LRCIN in the simulation results. The last signal of this group is the same as

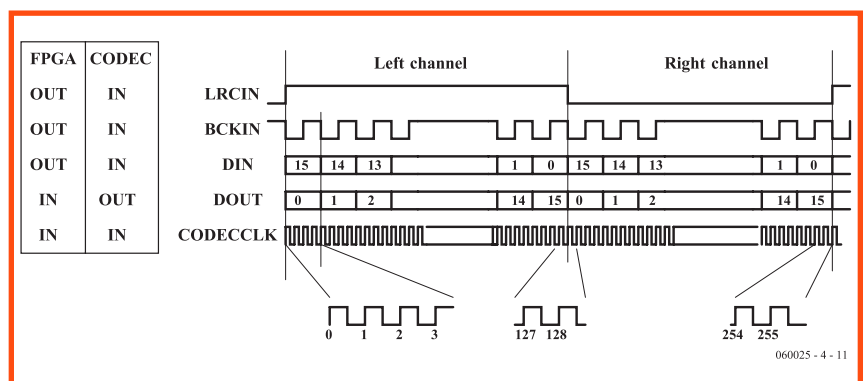


Figure 1. Timing diagram for data transfers between the codec and the FPGA.

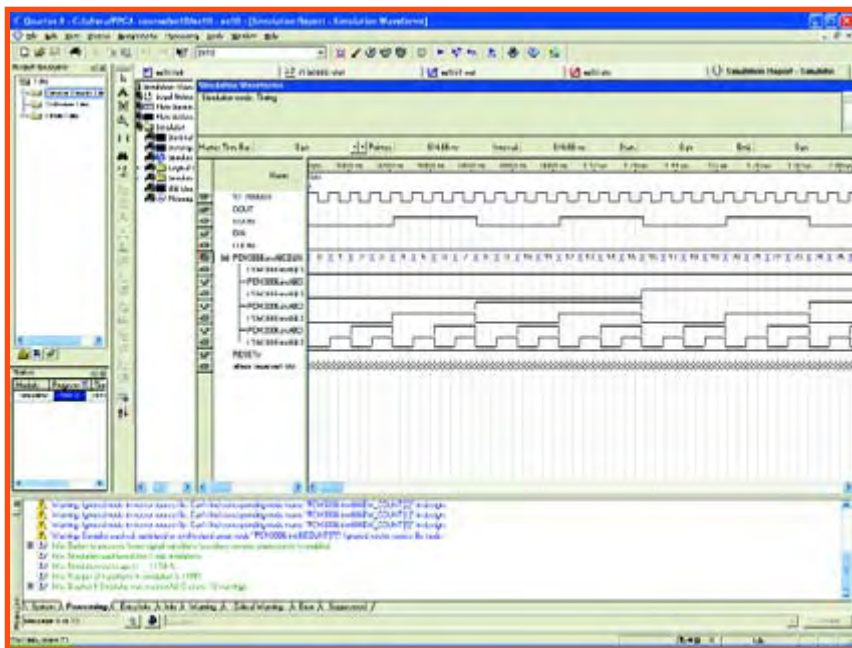


Figure 2. Data is transmitted on the falling edge of BCK, as can be seen from the simulation.

the LRCOUT signal in the VHDL design.

The POSEDGE_BCK signal and its counterpart NEGEDGE_BCK are generated using combinational logic. That means these signals are not synchronised by flip-flops. The disadvantage of this is that these signals can briefly assume an incorrect level if the input signals have different path delays. That phenomenon appears in the simulation in the form of short pulses. The technical term for these short pulses is 'glitches'.

Shift registers

The incoming and outgoing data are read in and 'pushed out' by shift registers. On each rising edge of the BCK signal, the contents of the SHIFTTIN register are shifted left by one position. The incoming data is stored in bit 0. The transmit shift register, SHIFTOUT, operates in a similar manner. It shifts the bits by one position on each falling edge of BCK. The most significant bit of this shift register is also the serial data output.

Each time a new set of samples must be transmitted, this shift register is loaded using the R_IN and L_IN signals. The contents of the receive shift register are also loaded into the LEFT_OUT and RIGHT_OUT registers.

Interface

At the same time, the NEW_SAMPLE output is set high for one clock interval. This signal indicates that a new set of samples has arrived. The peripheral logic can use this signal to process the new data.

Data must be applied to the inputs of the RIGHT_IN and LEFT_IN inputs in order to be transmitted. A high level at the LOAD input causes the data on the inputs to be stored, and it will then be sent with the next transmission.

Example

In the example, you can see that the data outputs are connected directly to the associated data inputs. The NEW_SAMPLE output signal is connected to the LOAD input.

This causes the received samples to be sent back to the codec on the next transmission. In other words, the signals at the inputs appear unchanged at the outputs after a short delay.

Another simulation

Overall operation of the circuit is illustrated by the file *ex10-3.vwf*. In this simulation, we used a random bit pattern for DOUT. The simulation clearly shows that this bit stream appears at the DIN output after approximately 31 μ s. The received data is thus sent back to the codec without any modification.

As you can easily see, several signals are missing in this simulation. The reason for this is that these signals 'disappeared' in during compilation, because the compiler attempts to generate a design that is compact a possible. As a result, certain signals may become redundant, and the compiler will not implement these signals in the FPGA. As a result, Quartus cannot simulate the signals during the simulation session.

Filter

The bypass function described above is not particularly useful in practice. A

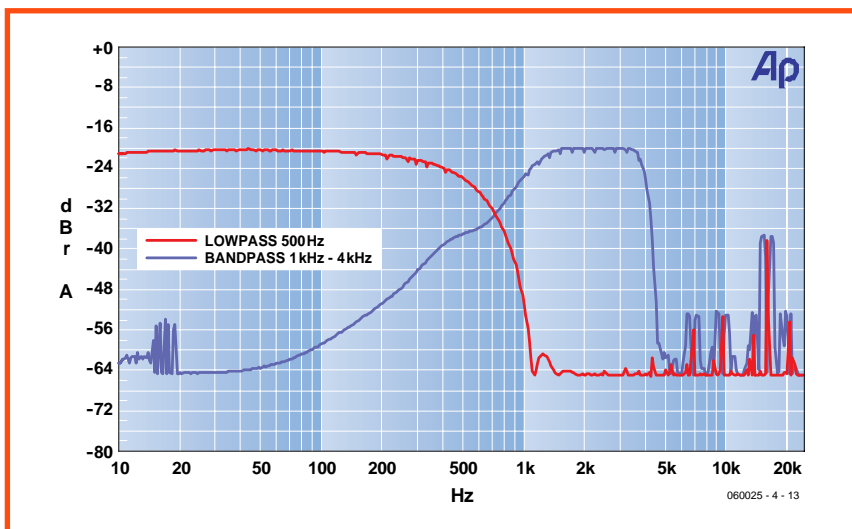


Figure 3. The characteristics of the various filter sets.

more useful technique is to process the input signal and then output the results via the codec.

The example file *ex11* implements an audio filter. Communication with the codec takes place via the previously described PCM3006.VHD core. The samples are processed in the FIR.VHD code segment. The filter operates on the FIR principle. 'FIR' stands for 'finite impulse response'. Filters of this sort are often used in digital signal processing.

In a FIR filter, the passband characteristics are determined by a set of parameters called coefficients. These coefficients can be modified as desired in Quartus. Just as in the previous instalment, the Memory Content Editor is the tool for that purpose. The coefficients are stored in the memory segment named 'COEF'. The memory segment named 'IN' holds the most recent 128 audio samples. Several hex files with coefficients are

available for the project so you can easily try out various filters. The characteristics of the various filter sets are shown in **Figure 3**.

Signal generator

The final example, *ex12*, implements a simple sinewave generator. It produces sinusoidal signals on the outputs. The signal on the right channel lags the signal on the left channel by 90 degrees.

The sinusoidal signals are generated using an arithmetic unit that can compute sine and cosine values. This unit needs an angle (*phase*) and an amplitude (*mag*) for this purpose. The unit then calculates the corresponding X (cosine) and Y (sine) values.

The arithmetic unit uses the CORDIC algorithm, which is suitable for calculating goniometric functions using simple operations. CORDIC has the unique property that it multiplies the length of

each vector by approximately 1.645. That means you have to ensure that the results fit within the range of a 16-bit signed number, so the input value must not exceed 4DD0. If you use a larger value, the resulting sinewave will be highly distorted.

Signal

To obtain a sinusoidal signal, a constant value must be applied the *mag* input. In addition, the phase must be increases slightly for each sample. That is the function of the *mag_phase_accu* block. Each time a new sample is sent, the signal *new_sample* goes high briefly. That tells this block that it must increment the value of *phase* by a certain amount. That amount can be set using the dip switches. The larger the amount, the higher the frequency at the output of the codec. The block *cordic* then performs the calculation and sends the result to the codec.

(060025-4)

CORDIC

CORDIC (Coordinate **R**otation **D**igital **C**omputer) is a method that can be used to implement goniometric functions efficiently in digital systems. It describes how to calculate goniometric functions using only add and shift operations.

CORDIC uses vectors. These vectors can be described as a combination of real and imaginary numbers (corresponding to their X and Y coordinates), or as a combination of a length and an angle.

If two vectors (A and B) are multiplied together, the length of the resulting vector (C) is equal to the length of vector A times the length of vector B. The angle of the resulting vector is the sum of the angles of vector A times and vector B. This multiplication takes the following form in X,Y notation:

$$X_c = (X_a \times X_b) - (Y_a \times Y_b)$$

$$Y_c = (Y_a \times X_b) + (X_a \times Y_b)$$

As you can clearly see, this requires using multiplications. If we ensure that these multiplications are all powers of 2, everything becomes very simple. Multiplication by a power of 2 (such as 2^{-2}) is equivalent to shifting bits. That is very easy to do using digital logic.

The CORDIC method describes how to calculate goniometric functions by multiplying an initial vector by vectors with X coordinates equal to 1 and Y coordinates that are always powers of 2. As a result, this method can be implemented very efficiently in digital circuitry.

Example

Consider the following expression as an example: $100 \times \cos(30^\circ)$. As our starting point, we take the vector (100, 0), which has length of 100 and an angle of 0° . The

desired angle is greater than the current angle, so the first operation is to multiply the vector by the vector (0, 1). Our vector now has an angle of 90° . That is greater than the desired angle.

The next step is thus to reduce the angle. For that purpose, we multiply by the vector (1, -1). Note that the Y value of this vector is negative, so angle of this vector is also negative.

After this multiplication, the angle of our vector is $(90^\circ - 45^\circ) = 45^\circ$. This is still greater than 30° , so the next step is to multiply by the vector (1, -0.5). This causes to angle of our vector to become $(45^\circ - 26.57^\circ) = 18.43^\circ$.

The angle is now smaller than what we want. We thus use the vector (1, 0.25) in the next step. That increases the angle by 14.04° . After this step, the angle of our vector is 32.47° . We get closer to 30° with each step, so the result is more accurate with each step.

Each multiplication changes the length of our vector as well as its angle. In the present case, we now have a vector with a length of $100 \times (1 \times 1.41 \times 1.12 \times 1.03) = 162.66$. That means we have to multiply this value by a correction factor. Another option would be to make the length of the initial vector 61.5 in order to finally obtain a vector with a length of 100. This multiplication factor is always the same, regardless of which angle we want.

No matter which option we choose, the desired cosine value is given by the X coordinate of our vector, while the Y coordinate represents the sine value. We get those values for free!

X	Y	Angle	Length
0	1	90°	1
1	1	45°	1.41
1	1/2	26.57°	1.12
1	-	14.04°	1.03
....



The cartridge concerned, the 51640M from HP, otherwise known as 'type-40'. According to sources on the Internet this cartridge can be refilled at least 10 times.



The still pristine yellow cartridge. A number of other cartridges looked much worse after many hours of fiercely attempting to figure out the function of the individual contacts.


Electronic Sta

Jeroen Domburg & Thijs Beckers


In this month's modding & tweaking article we delve a little more into the 'not so very useful, but nevertheless quite funny' types of circuit. With the circuit presented here you can write on water, for example, even if the message lasts for only a short time before it fades away. But whiteboards and other solid surfaces such as paper can be used as well. Curious how we did this? Read on...



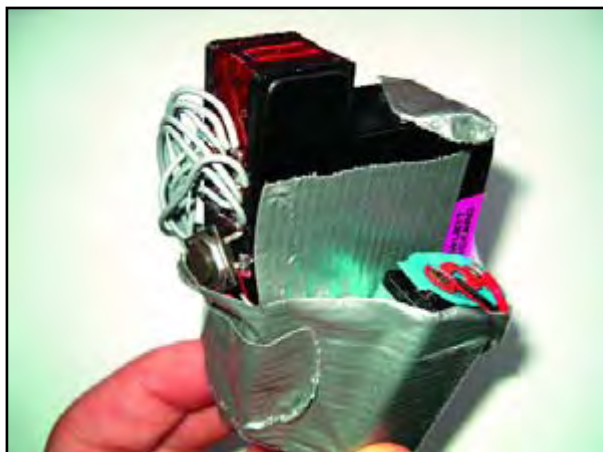
The circuit, attached to the cartridge. The activation pushbutton has been placed in an easily accessible location.



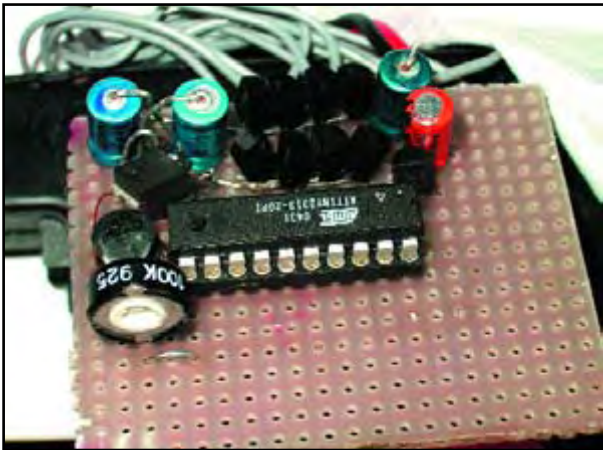For the construction the universally applicable enclosure 'duct-tape' (a.k.a. Gaffa tape) has been used. Also handy for holding the battery in place.



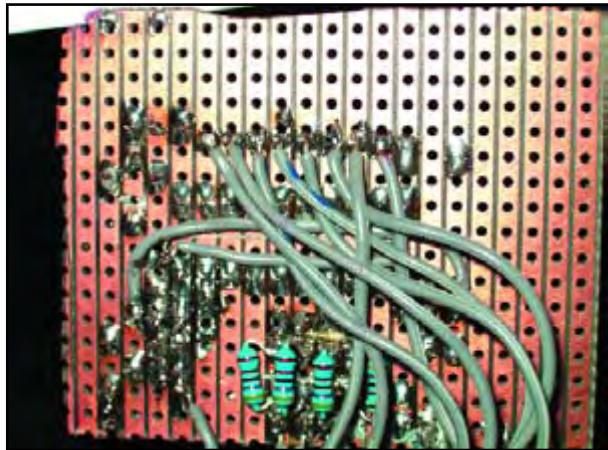The circuit was built straight away, without doing a PCB design or such, on a prototype board.



The bottom side is witness to the experimental character of the circuit as well.

mp Printing without a printer


One of the nice things of having electronics as a hobby is that the things you make do not necessarily have to be useful. It is all good fun as long as you're entertained. The present project sprang from this mentality. In good Young Ones tradition, the author was very busy scrawling meaningless mottos, maxims and sayings on a flat-mate's whiteboard and noticed that his handwriting was barely legible. In addition, the writing was also exceedingly slow. From the idea that it should be possible to complete the activity of vandalising someone else's whiteboard much faster, the idea of the 'electronic stamp' evolved. The function of the felt pen is replaced in the electronic stamp by an inkjet cartridge.

Cartridge


An inkjet printer cartridge these days is an advanced system, with perhaps hundreds of 'nozzles'. A nozzle is a small hole from which a droplet of ink is fired. The method of firing differs from manufacturer to manufacturer. In the case of the Hewlett Packard (HP) cartridge that we use in this circuit, the nozzles are operated thermally. The print head consists of a slice of silicon, where the nozzles are channels from the ink reservoir to the outside of the print head. In the middle of each tube there is a micro-resistor. By running a relatively high current for a very short time (times of only 10 microseconds are not



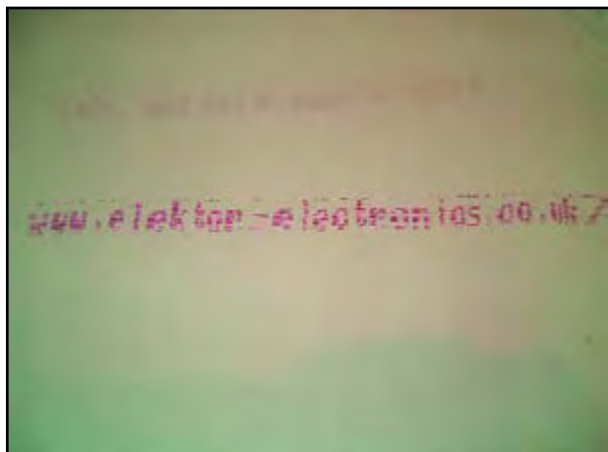This effect is created by moving the whole assembly across a piece of paper ...



... while holding the pushbutton down.

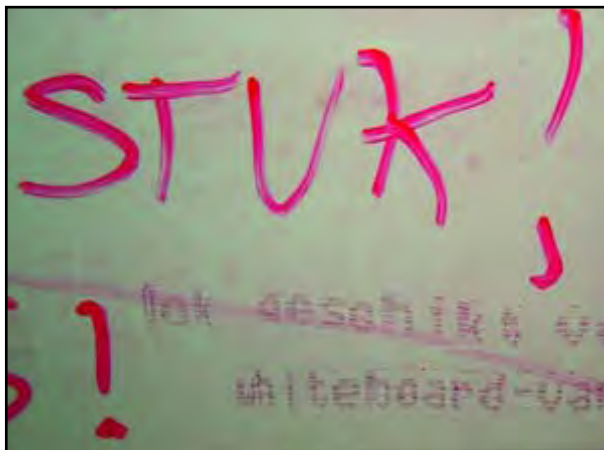

In addition to paper, this device also works quite well on whiteboards... This was the whole reason to get started in the first place.



But it is not limited to this. The object shown here is something that many students (and also many non-students) will be very familiar with.

unusual) through this resistor, the location becomes so hot that the ink that is there evaporates. Because the ink in a gaseous state occupies more space than ink in a liquid state, the (still liquid) ink at the front of the tube is pushed outside. All this happens at a very small scale, as a result of which the speed at which the drop of ink leaves the nozzle is quite high and the ink lands on the paper with high precision.

In a normal inkjet printer the print head is moved back and forth with a motor and a guiding system. If however, we want to make a manageable device then it is not convenient to integrate this entire system into an electronic stamp. That is why we use only the cartridge together with some electronics that drives the head. Moving the head itself is a job for the user. When moving it is important to hold the whole assembly straight and move with a uniform motion across the surface. After a little practice this is quite easy to do.

The cartridge that was chosen is an HP 51640M cartridge, also known as an 'HP type-40, magenta'. This cartridge is available in magenta (red-purple) as well as cyan (light blue), yellow and black. The circuit has

only been tested on the magenta and cyan cartridges, but it can be assumed that all type-40 cartridges have the same pin-out, therefore also the yellow and the black. Other HP cartridges do not appear to have the same pinout, although the operating principle is probably the same.

Nozzles

In the first generation of inkjets the cartridges had only about 24 nozzles. Driving this system was simple: one side of all the nozzle resistors were tied together and connected to one pin of the connector. The other side of the little resistors each had their own connector pin. The pin-layout for such a cartridge can be figured out with a simple multimeter.

New cartridges are more awkward. The cartridge that we use here has over 100 nozzles. The number of connecting pads is a lot smaller, however. It appears that HP has built some electronics into the print head that takes care of driving all the nozzles. And now, as electronics hobbyist you are facing a problem. What's inside that



Because the drops are so small and light it is even possible to write on water!




However, the ink sinks after ten or so seconds and becomes unreadable.



You can let the circuit loose on this too. Note: the ink is probably not all that healthy.

piece of electronics? You see, there are several methods that could be thought of to enable to nozzles to be driven individually. From shift registers and multiplexers to a simple matrix to reach the nozzles one by one. The latter method can still be figured out with a multimeter, but the other methods require at least a logic analyser to discover what is going on, or a stroke of genius. Opening the printer where this cartridge belongs leads to nothing in this case. The only thing that can be seen is that a number of connections are tied to ground and the others run into an unidentified IC.

In the end, the author, after thinking long and measuring a lot, arrived at a method copied from gene technology. Make a gene defective, observe what changes in the organism and then you know what that gene does. This is also possible with inkjet cartridges: cover some connector pads with sticky tape and look at what goes wrong. After much messing about, it appeared that with exactly three pins (one of which is ground) just one thin line was drawn by the printer. These pins are therefore enough to drive one nozzle. With this information and

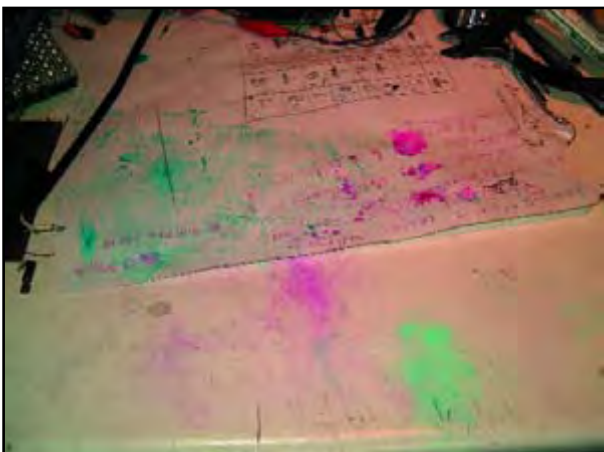

A final tip: should you have a go with inkjet-cartridges yourself, then work on a surface where it will not be a problem if it gets a bit messy.

some tinkering with a microcontroller and a lab power supply set to 20 V, it was possible to discover the exact workings of the cartridge.

In the end it appeared that the cartridge is divided into eight sectors with 17 nozzles each. The print head itself consists of two rows of holes. Each row of holes has four sectors. And each sector has its own power supply pin. When 20 V is applied to this the nozzles in that sector can be activated. Whether they actually do this depends on the nozzle inputs. When a positive voltage is applied an actual drop of ink will come out of the nozzle. If no voltage is applied to the nozzle input then nothing happens. Figure 1 shows the positions of the various inputs.

Voltage

The remainder of the circuit consists of nothing more than a microcontroller (ATTiny2313), some electronics to ensure smooth communication with the cartridge, a DC/DC converter to generate the required 20 V for the nozzles, a 78L05 for the power supply for the microcontroller and a 9-V battery as a power supply (see Figure 2).

The DC/DC-converter consists of L1, D1, T1, C4, R1 and the PWM hardware of the microcontroller. These parts together form a simple 'boost' converter. This works as follows. The microcontroller attempts to keep the voltage at PD6 at 2.5 V. It does this by making the pulses it generates on PD5 longer or shorter. These pulses cause T1 to conduct which results in a current through L1. When T1 blocks, that current continues to flow for a short time due to L1. C4 is now charged via D1. The current that flows into C4 allows the voltage across C4 to be higher than the power supply voltage. This voltage is divided via R1 and supplied to PD6. In this way the microcontroller regulates the voltage across C4 to a set value. R1 is used to adjust the voltage across C4 to the required 20 V. Start with the potentiometer in the centre position and turn towards the ground connection to increase the voltage to 20 V.

The power supply for the microcontroller is handled by the 78L05 and the necessary decoupling capacitors around it.

Control

In addition to the PWM logic that is programmed into the microcontroller, there is also a simple character generator built in. Even though it is possible to obtain quite a high resolution (32 nozzles are being controlled) the font uses just 8x8 pixels per character. This low resolution was deliberate because there is only 2 k of flash ROM available in the microcontroller. By selecting a microcontroller with more ROM a better font could be used. A considerable amount of rummaging through the junkbox was involved for this project and unfortunately the author did not have a 'bigger' microcontroller on hand.

The characters are generated based on a small sentence in the flash ROM. These are then sent to the nozzles. The sectors are made active one by one and when a sector is active only one nozzle is activated. The reason that this is done for each individual nozzle is that the print head would otherwise create a local vacuum for itself. This would result in (temporarily) no ink from the print head. By changing the nozzles, the nozzles that are not driven are given time to fill with ink again.

The sector lines of the cartridge (C1 to C4) have to be powered with a voltage of 20 V to make a sector active.

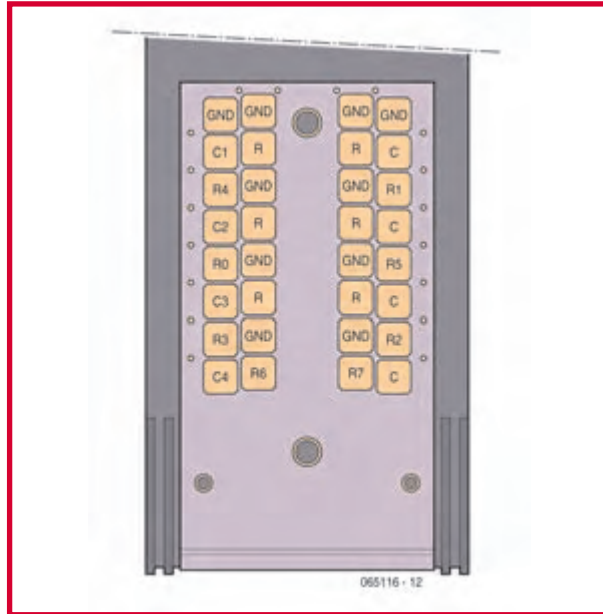


Figure 1. Here we see the layout for the print head used. Only R0 to R7 and C1 to C4 are used, the other connections are not required for this project.

We do this with T2 to T5 and T6 to T9. This double transistor stage looks superfluous at the first instance. Why not connect T6 to T9 directly to the microcontroller? This would cause problems however. In the microcontroller there are built-in ESD diodes that conduct voltage above or below the power supply voltage to 5V and ground respectively. If T2 to T5 were left out, current would flow from the emitter via the base to the 5-V power supply and this is not the intention. Hence the addition of T2 to T5 in the circuit.

Construction

The author built the circuit on a piece of experimenting board, using parts available from the closet. That is why, for example, MOSFET T1 is a rather strange type. In principle any P-channel MOSFET can be used for this, as long as it can cope with the peak current of about half an amp. The coil L1 does not have a critical value either. The author's coil comes from a backlight-inverter, but any slightly hefty coil will do. If the 20-V power supply is actually in the vicinity of 20 V, then all is well.

Additional possibilities

There are a few aspects of the circuit that could be improved. Firstly, the nozzles that have been used are not spread evenly across the cartridge. It is however quite a lot of work to figure out exactly how to drive all the nozzles and the pins used here already produce a quite legible text. Secondly, the current consumption is not really suited to a little 9-V battery. With long texts this battery is temporarily exhausted quite quickly. It is of course possible to replace it with a 9-V NiCd or NiMH battery. These have no problems delivering short-duration current spikes. Thirdly, the text that the stamp produces is fixed, defined by the code in the microcontroller. With a little bit of work it can be changed to use the EEPROM instead and be made adjustable via, for example, a serial cable.

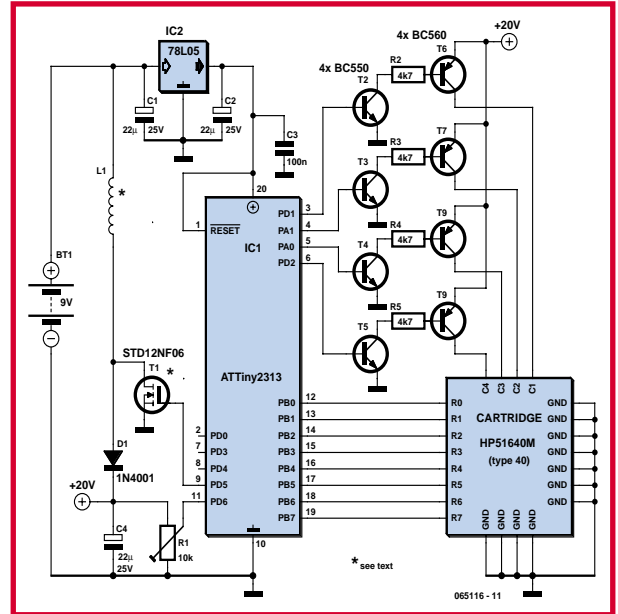


Figure 2. The circuit is not all that big and can easily be built on a prototyping board.

All this is not necessary for vandalising someone else's whiteboard and is left as an exercise for the reader. The author is keen to see any improvements in the circuit or firmware, so that others can also benefit from these. The firmware, source code and any potential updates are available for free downloading, of course ([1] and [2]). Now a final remark: inkjet cartridges are not really designed to be used continuously in the open air. It can happen that the head becomes blocked with dried ink. In that case it helps to shake the whole thing vigorously a few times (watch out for splattered ink everywhere) and to suck up the ink with a tissue from the head afterwards. It certainly helps if the cartridge is stored with the print head facing downwards as much as possible.

(065116-1)

Internet addresses

- [1] <http://sprite.student.utwente.nl/~jeroen/projects/stempel>
- [2] www.elektor-electronics.co.uk

About the author

Jeroen Domburgh is a student at Saxion Technical University in Enschede, the Netherlands. Jeroen is an enthusiastic hobbyist with an interests in microcontrollers, electronics and computers. On the monthly Modding & Tweaking pages Jeroen shows his tinkering, modifications and other interesting stuff, for which usefulness and absolute safety are not requirements while no attempt is made to win a prize for beauty of the design. Jeroen strives to create or modify circuits to achieve no more than the desired degree of functionality. Forewarned is forearmed!



Straight from the heart of electronics each month

This Issue:

FREE PHILIPS MIFARE RFID CARD

design your own application
with our matching RFID Reader

Next Issue:

FREE ELECTRONICS SIMULATION DVD

demos – trial versions – fully functional programs



Want to know everything each month?

SELECT YOUR OWN ANNUAL SUBSCRIPTION

AND RECEIVE A FREE 1W LUXEON LED TORCHLIGHT*

Fill out the Order Form with this issue today!

elektor
electronics

Subscription rates and conditions may be found at the back of this issue.

* Offer available to Subscribers who have not held a subscription to Elektor Electronics during the last 12 months. Offer subject to availability.

USB/DMX512 Converter

Jean-Marc Lienher

All amateur disc jockeys and light jockeys dream about it: a DMX512 converter not bigger than an XLR connector! But at a retail price of more than 500 pounds for this type of accessory, the dream may never come true. Here is a project that will make some on the dance floors very happy... the DMX converter of their dreams and for only a few pounds.



The USB/DMX512 converter described in this article connects to any computer equipped with a USB connector and a Windows® 98 OS or later. The USB (bus) supplies the current necessary to power the circuit we've designed. The proposed setup transmits the 512 DMX channels at a rhythm of approximately 42 frames per second using a computer equipped with a USB 2.0 interface. The maximum speed defined by the standard is 44 frames per second. Note that this transmission rate may be a little less with a USB 1.0 connection. The printed circuit board we designed for the converter measures 14 mm by 26 mm and employs SMD components.

Important note: our circuit, like many DMX converters sold in retail shops

(some of which come at exorbitant prices), does not include full electrical isolation. This is not terribly important when using a DMX device **that's operating properly**, but could prove fatal for your computer if, unfortunately, a mains phase conductor of a defective projector or floodlight should come into contact with the DMX512 line. Forewarned is forearmed!

A PIC16C745

The PIC16C745, of which the block diagram can be found in **Figure 1**, is a low-cost microcontroller. However, it was one of the first to have a USB interface. In reality, it is a type 1.1 low-speed USB interface. The transmission rate of the USB bus in low speed mode is 1.5 Mbits/second.

The DMX512 bus speed is a 'measly' 250 kbits/s. The USB is six times faster, so where is the problem? Well, for one thing the USB standard defines two data transfer modes for low speed, Control transfer and Interrupt transfer. The control mode uses all of the bus bandwidth and is, according to the standard, reserved for USB receiver configurations. The Interrupt mode is intended for data transfer but we should note that it is limited to 800 bytes per second!

Out of spec!

With the above in mind we're more or less forced to use the 16C745 in a configuration that's not found in the USB

nverter

Housed inside an XLR connector!

standard. To do so, we have selected the Control transfer mode in order to exchange data between the computer and the microcontroller.

Obviously, considering that the USB bus was not designed for that use, we had to write a special driver for this Microsoft Windows® application. The firmware source code for the microcontroller is available from our website

at www.elektor-electronics.co.uk (file # 060129-11.zip). Unfortunately, the copyrights for the driver source code rest with the author, hence this file cannot be made freely available. The pre-programmed PIC (order code 060129-41) is however available from the Elektor SHOP (on the web or in this magazine)

Circuit diagram

A quick look at the diagram in **Figure 2** allows you to better understand why the circuit can be so compact: it has only two active components! The PIC16C745 (IC2) in its 28-pin SMD SOIC version is clocked at 6 MHz by X1, a miniature resonator with integrated capacitors. The internal microcontroller frequency is set to 24 MHz, thanks to its integrated PLL, thus lowering any risk of stray radiation which might occur when using a resonator at this frequency. The PIC generates the 3.3 V voltage necessary on 1.5 kW SMD resistor R1 connected to the D- line of the USB cable. A 220-nF SMD capacitor, C2, smoothes this voltage supplied directly by the microcontroller pin. Pins D+ and D- of the PIC are directly connected to the USB bus. The second capacitor, C1, is included to suppress fluctuations in the 5-volt supply voltage caused by PIC switching. The last electronic component in the circuit, IC1, is an RS485 bus driver for which we use the SMD SO8 package version. It is connected to the USART ((*Universal Synchronous & Asynchronous Receiver Transmitter*)) of the 16C745 enabling it to be used bi-

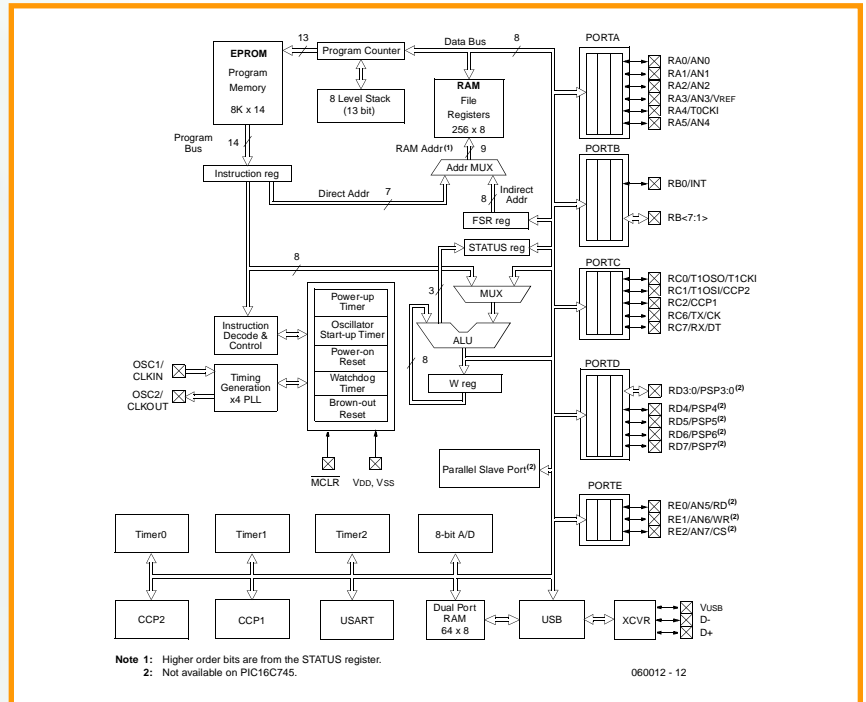


Figure 1. PIC16C745 architecture.

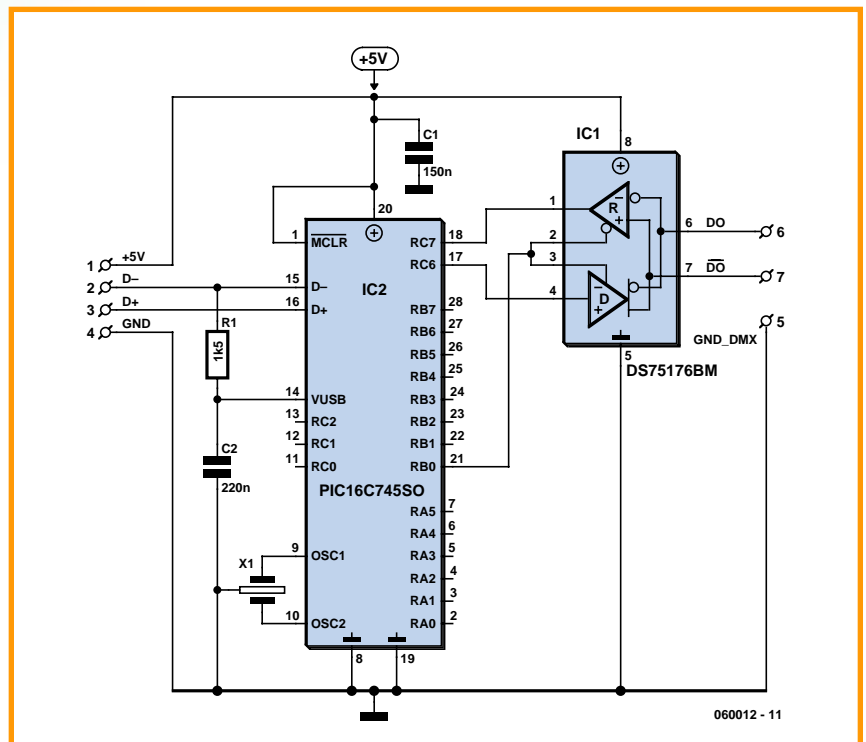


Figure 2. The circuit diagram of our converter is limited, in fact, to a PIC micro and an RS485 bus driver.

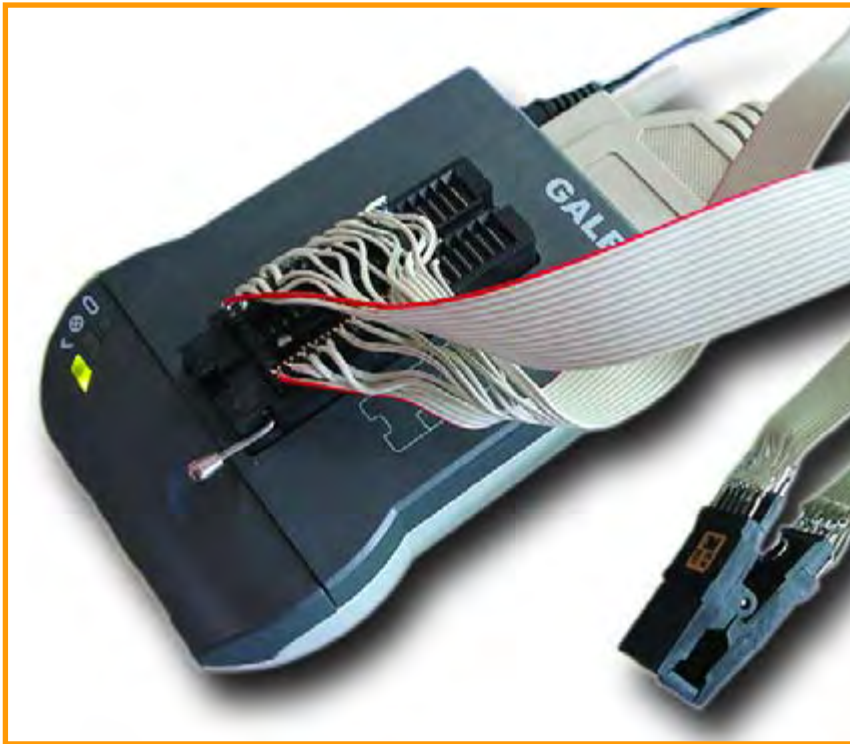


Figure 3. Not for the faint-hearted...


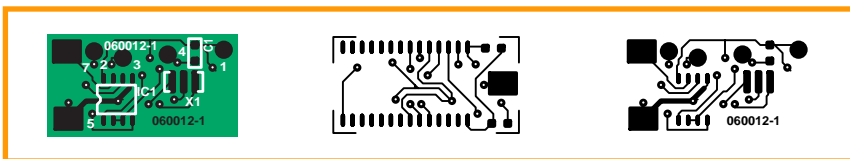


Figure 4. The PIC occupies almost all space at one of the board sides. This double-sided board is through-plated.

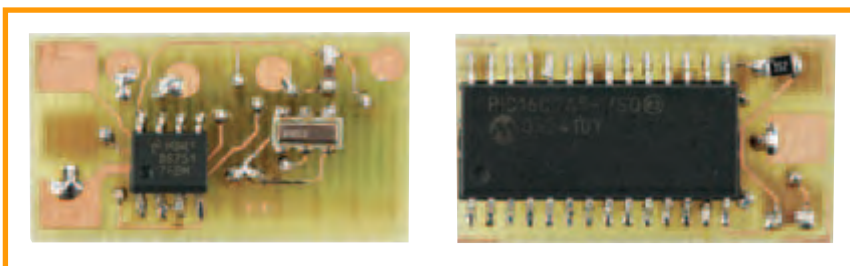

COMPONENTS LIST

Resistors

R1 = 1k Ω 0.25W 5% (0805)

Capacitors

C1 = 150nF ceramic (0603)

C2 = 220nF ceramic (0603)

Semiconductors

IC1 = DS75176BM (National

Semiconductor)
IC2 = PIC16C745-I/SO, programmed,
order code **060012-41**

Miscellaneous

X1 = 6MHz resonator, Murata

CSTCR6M00G53-R0

XLR connector, Cannon type 10HC089

(e.g. www.distrelec.com, #

112242) USB A-A cable, 1.8m,

standard

PCB, ref. 060012-1 from The PCBshop

Project software, free download #

060012-11.zip from www.elektor-electronics.co.uk

directionally, in case you would like to modify the firmware of the PIC to use it as a DMX512 input. The non-inverting buffer output of the RS485 driver is connected to pin 3 of the XLR connector and the inverter output is connected to pin 2, since pin 1 is connected to ground. As far as the USB cable and connector are concerned, this is a moulded cable sold in retail stores or the one with your old mouse (USB, of course!). It has four wires plus shielding: a pair of untwisted, fairly thick wires for the 5 V power supply voltage and two thinner wires, twisted as pair, for data transmission. XLR connectors are supplied by many manufacturers. Here, a Cannon type 10HC089 is used. It is important to use this XLR connector because a standard Neutrik connector does not have enough space to hold the circuit.

Programming the PIC

The PIC 16C745 micro has to be programmed before soldering it onto the board. If you're a home programmer, make sure you have a suitable DIL-to-SOIC adaptor with your programmer. Alternatively, as we did in our tests (see the photo in **Figure 3**), you can make one yourself using a DIL carrier, a piece of flatcable and a test clip for SOIC circuits. The hex (object code) file to burn into the PIC is called **firmware\usb2dmx.hex**. It is contained in archive file **060012-11.zip** which may be downloaded free of charge from our website. The PIC may also be purchased ready-programmed from the Elektor SHOP.

Heat up your soldering irons!

Populating the board requires some skills handling SMD parts but should not cause dramatic problems. Fortunately, the components used for this project are not as difficult to solder as, for example, an ARM processor in a BGA package with 278 balls, sized 14 mm x 14 mm!

The printed circuit board of which the top and bottom side artwork is shown in **Figure 4** is without doubt, one of the smallest we have ever published in *Elektor Electronics*.

You need to use a soldering iron with a fine tip and thin gauge solder. Start by soldering the PIC micro, IC2, into place (be careful to observe the correct polar-

ity), which then constitutes a base plane in order to solder the components on the other side of the circuit. The best option, so as to perfectly align the integrated circuit on the board, is to apply a bit of solder to two pads for corner pins of the device. Next, place the PIC and reheat the two solder terminals in order to create an initial attachment point for the component. If the component is perfectly positioned, the only thing left to do is to solder the remaining 26 pins. If not, reheat the corner pins and carefully realign the chip.

Next, solder R1 and C2 on this side by pre-tinning a pad, then placing the component with tweezers while keeping the pad at fusion temperature.

Next, solder the other connection of the component. Use the same technique to solder the remaining components (IC1, C1, X1) on the other side of the board. X1 is the component that requires the most attention because it is more usually soldered using the 'reflow' technique.

Microsurgery

Next, we cut a USB type 'A-A' cable in half and strip it. The black wire is soldered to the 0 V pad (terminal 4), the red wire to the +5V pad (terminal 1), the green wire to the D+ pad (terminal 3) and finally the white wire to the D- pad (terminal 2). You'll find that this bit of the construction requires some dexterity in handling the solder iron,

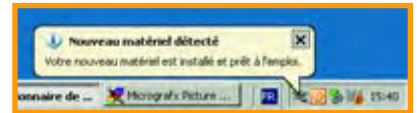
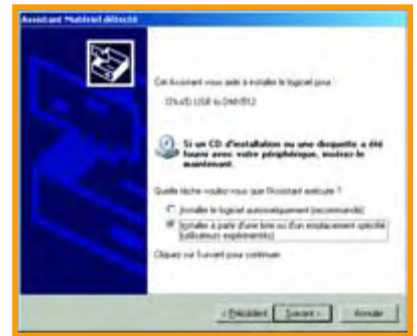


Figure 5. If you are used to installing USB peripherals, this type of screen should look familiar.

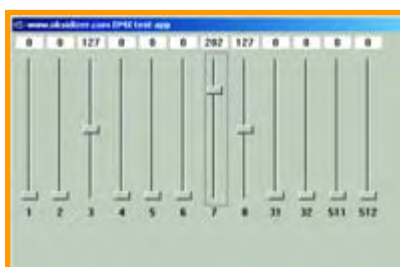
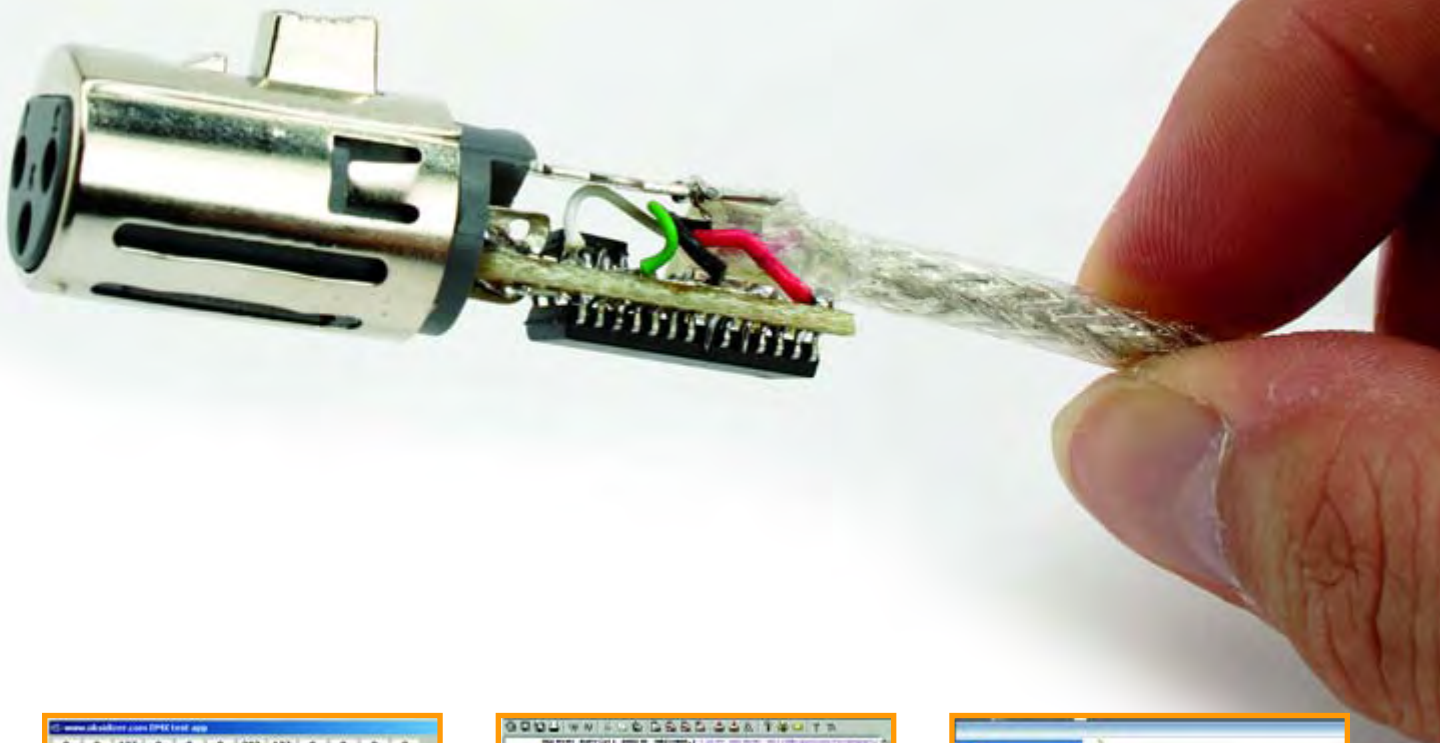


Figure 6. The 'test_cpp.exe' program is used for quick testing of our USB/DMX512 converter.

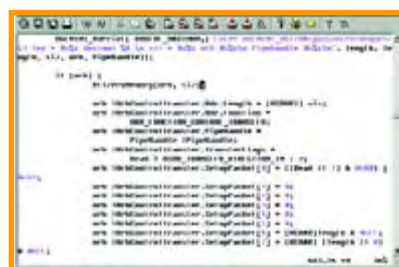


Figure 7. The purpose of the oGenInt.sys driver function is to shape the 'requests' sent by the USB bus.



Figure 8. Settings screen in FreeStyler.

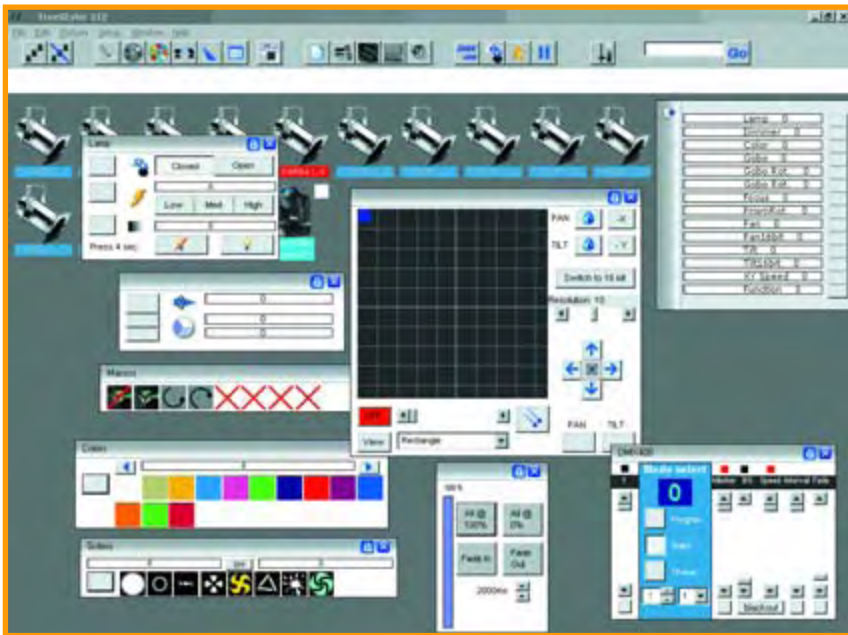


Figure 9. The number of functions available in FreeStyler makes it quasi-professional.

since there are no holes in the printed circuit. The cable shielding is soldered to the connector strip. The next step is to solder the circuit to the XLR connector, from which the rubber cable guide has been cut. Terminal 5 should be soldered to pin 1 of the XLR connector, terminal 6 to pin 3, and finally terminal 7 to pin 2.

Before applying a little glue to keep the USB cable in place and to close the XLR connector again, test the set-up by connecting it to your computer. When the new USB device is inserted for the first time, you will be asked to install the drivers provided in the .zip file **060012-11.zip** (Figure 5). Once the drivers are installed, connect the XLR plug to your DMX512 equipment and launch the program **cpp_test\bin\test_cpp.exe** which is found in the same archive file. There you have it!

Software environment

PIC firmware

The assembly code of the PIC is derived from version 1.25 of the firmware provided on Microchip's website, the manufacturer of the PIC16C745.

We used version 1.25 because version 2.00 did not seem to function with the erasable PICs we had available. The file *usb_main.asm* contains an endless loop reading batches of data sent by the computer. These data are utilised in the *dmx512.asm* file that synchronises the USB reception with the transmission on the serial DMX512 bus. Also in this file we find the code that serves to generate the pause required at the end of each DMX field.

The test_cpp.exe program

This program, shown in action in Fig-

ure 6, is used to quickly test the operation of the USB/DMX512 converter. Its source code demonstrates the way to use the unique function exported from **DLL DasHard.dll**.

The really important bits happen in the **test_cppDlg.cpp** file. More specifically, the **CTest_cppDlg::OnVScroll** function copies the value of the cursors in the **OutDmx** output buffer. And the **CTest_cppDlg::OnTimer** function, called on at regular intervals, loads the DLL and obtains a pointer on the **OksidCommand** function during its first call. During the following calls, it simply passes the output buffer to the **OksidCommand** function.

The DLL DasHard.dll

This one links it all to the driver and, provided a converter is connected to the computer, opens a data stream with it. This stream is fed by a specific thread that loops as long as the DLL is used. Refer to the source code for more details.

The oGenInt.sys driver

The driver (see the screenshot in Figure 7), of which the source code is regrettably not available, is in charge of shaping Control-type requests travelling on the USB bus. The **OGENINT.INF** file makes the driver installation possible. It creates the association between the driver with our USB module, thanks to the *Vendor ID* and *Product ID* identifiers that are specific to our application.

FreeStyler, free DMX512 driver software.

FreeStyler is software written in Visual Basic that makes it possible to drive DMX512 equipment by indifferently using an impressive variety of converters for the parallel, USB, or Ethernet port. As shown in the screenshot in Figure 8, the latest version also functions with our circuit using the reference 'Oksidizer USB2DMX'. FreeStyler is available as a free download from the website run by the author of the program. It comes with a complete user manual.

The screen copy in Figure 9 shows that FreeStyler offers a range of functions that may disconcert a beginner but will be welcomed as very useful by (DMX512)-enlightened amateurs and professionals.

Internet links :

Author's website: <http://www.oksidizer.com>

http://membres.lycos.fr/epatix/dmx_512.htm

<http://users.pandora.be/freestylerdmx/>

<http://www.beyondlogic.org/usbnutshell/>

http://ogloton.free.fr/dmx_512/index.html

(060012-1)

Pontavi-Thomson Bridge



Rolf Blijleven

A bakelite box with rounded corners, two large knobs on top and a nice small meter. Still in perfect condition, with proper Test Terminals. It was waiting to be thrown away when some colleagues were tidying up a cupboard, since the device was no longer used. 'The Rx Resistor' we called it, and it was used to measure the values of resistors used in manufacturing gas analysers. Because I found it heartbreaking to see such a magnificent piece of equipment disappear in the skip they let me take it home.

Admittedly, it stayed in the loft for the first few years. But when I finally needed it one day, it was easy to understand the German instruction manual. Its operation and application turned out to be child's play. The Pontavi-Thomson made by Hartmann & Braun is a bridge that can accurately measure low-value resistors (R_X). The measurement range is from 0.0001Ω up to

2.1Ω , and the measurement error is less than 5%.

R_X is connected directly to the terminals on the left-hand side and also to the terminals at the top via two leads — see **Figure 1**. At the right you have to connect a power source with a voltage of 2 V and capable of sourcing several amps. We're now ready to take a measurement. With the switch set to 1 Ohm, you momentarily press down button T, which is on the top-right. If the meter deflects to the left, you should turn the big dial to the right. If the meter doesn't move with the dial turned all the way it follows that the value of the resistor is greater than 2.4Ω or so, which is too large to be measured by this instrument. If the meter instead deflects to the right, you can set the switch to a tenth, a hundredth or a thousandth of an Ohm. In one of those settings you'll find that you can set the dial such that the pointer is absolutely central. The scale has been provided with a mirror to avoid errors caused



by the parallax effect — when the pointer is no longer visible in the mirror (i.e. when your eye is straight above the needle) you have removed any parallax error. The value of R_X is then calculated by multiplying the position of the dial by the setting of the switch. A piece of cake, really.

Finding out about the theory of operation (which should be included in a descriptive article like this) turned out to be less easy. The manual casually mentions 'the well-known Thomson circuit'. This may have been well-known in the sixties, but I had certainly never heard of it. Much to my surprise, a search on the Internet led me to a more modern version of the Pontavi-Thomson [1], but I still couldn't find an easy to understand description. I did discover that Pontavi wasn't, as I thought at first, an Italian colleague of Mr. Thomson, but rather a descriptive term used by Hartmann & Braun: there was also a 'Kapavi' for capacitors ('Kapazitäten'), and an Inkavi for

inductors ('Induktionen') [2]. I finally found the answer in a library book in the college, in a chapter we were allowed to skip for our exams (that's why!).

The operation comes down to the following (**Figure 2**): the resistors on either side of the ammeter have such a large value that little or no current flows through the terminals at X_E . Their contact resistance and that of the leads can therefore be ignored. The series resistance between the wiper and the negative side of the supply reduces the voltage across the bridge but doesn't influence its balance. The same applies to the resistor in the positive supply side. The bridge is balanced when the ratio of resistor S to the left of the wiper and R_X is the same as the ratio of the resistors 'below' and 'above' the wiper of W. In that state the position of W in combination with that of S returns the value of R_X . It's a marvel of simplicity and ingenuity. Inside we can see the wirewound resistors connected to decade switch W (right-hand photo). It all imparts a sense of reliability and craftsmanship; we can almost see the electrons rush round with the naked eye. It's all very different from the latest SMD boards made by robots. The old cliché has to be said at this point: they don't make them like this any more! Is there still a place in the world of modern electronics for an instrument such as this? The principle is still in use, but with servo circuits that determine the resistance automatically. There is probably a niche for this instrument in high-end audio: owners of ultra-pure platinum doped copper loudspeaker cables can make sure that the resistance of the left and right hand cables is identical, giving an even better stereo reproduction. I'll be using it for my own projects, which I can't tell you about just yet.

(065062-1)

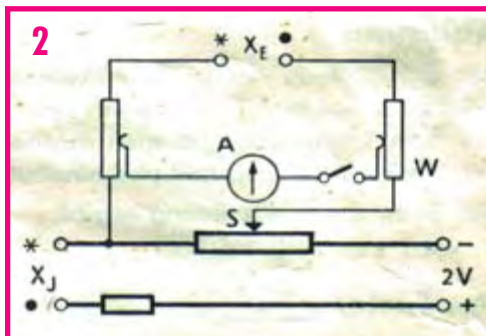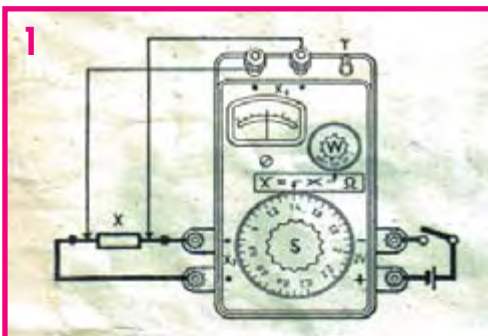

Web links and literature

- [1] www.alte-messtechnik.de
- [2] www.jogis-roehrenbude.de



Battery discharger

Gerard Guilhem

The circuit shown in **Figure 1** allows NiCd type LR03 (AAA) and LR6 (AA) rechargeable cells to be discharged in a controlled manner. The discharging (load) current is about 500 mA. The LED indicates the progress of the discharging process — it goes out when the battery is completely discharged. The current becomes zero at a battery voltage of about 0.6 V, which is perfectly acceptable for most NiCd cells. The 2.2-ohm resistors R2 and R3 are the components taking the battery current and turning it into heat.

The diagram in **Figure 2** closely resembles the first one. Here we suggest using an npn power transistor, T3, as the power dissipating component. The (pulsed) discharging current is determined by the value of resistor R1.

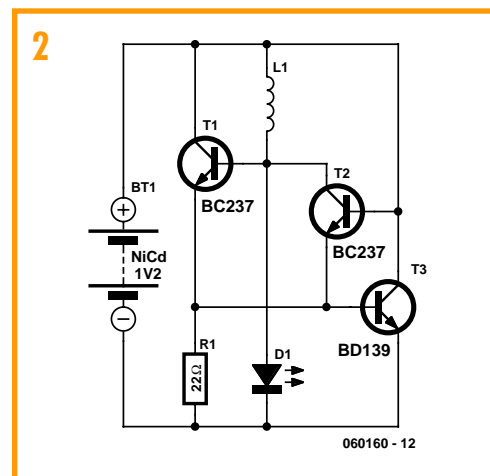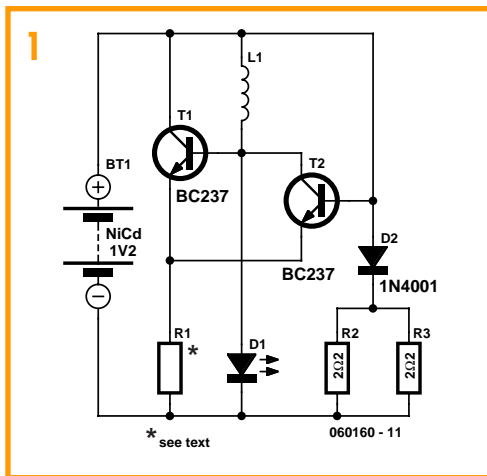Discharging NiMH (nickel metal hydride) batteries is not a problem either, since the terminal voltage is the same as NiCd cells — the only difference is the usually higher capacity compared with NiCd cells. The crucial parameter here is the



deep discharge (or 'end') voltage. Again, 0.6 V is acceptable for NiCd as well as NiMH cells. Accidental polarity reversal is a real danger, but then, only one cell is 'treated' at a time so no great losses will be suffered.

The LED goes out when the cell voltage approaches 0.9 V and that's when the battery should be disconnected. Transistors T1 and T2 of the first schematic may be just about any small-signal npn from the BCxxx series, like BC237, BC337,

BC547 and so on. Resistor R1 determines the current consumption of the circuit, as well as the current stored in choke L1 and consequently, the LED brightness. It can take a value of between 15 Ω and 47 Ω, where the lower value results in higher brightness and maximum current consumption.


The inductance of the choke is not critical and may be between 10 μH and 100 μH — you'll find that only the fre-

quency of operation will change. This will be about 200 kHz with a 20 μH choke and will vary a little due to the stray base-collector capacitance of the transistor you're using.

To prevent parasitic radiation of the circuit, it is recommended to fit a 100-nF (0.1-μF) decoupling capacitor across the battery terminals. The author employs a quadruple version of this battery discharger.

(060160-1)

Miniature tweezers for SMDs

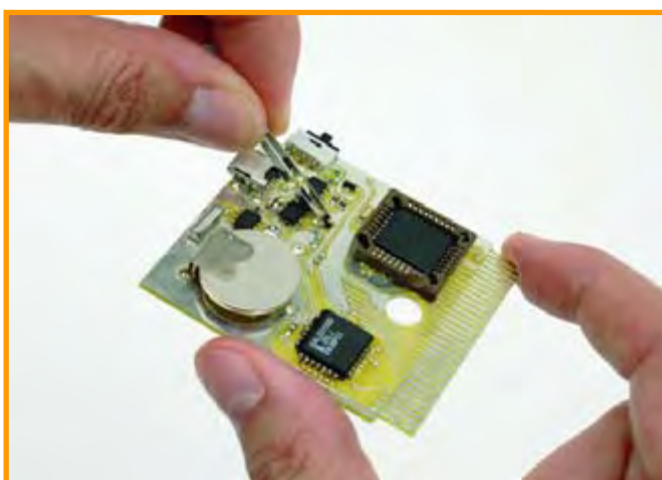

Luc Lemmens

Fitting SMD parts onto a circuit board is sure to tax your patience, eyesight and precision to a degree. In this magazine we've often described the techniques for positioning and solder-

ing of tiny parts like SMDs and will continue to share our tips and experience with you. These days, it seems you can't go round SMD parts anymore.

Although many implements and methods are available when it comes to picking up SMDs and

positioning them on a board, the humble pair of tweezers is probably one of the most frequently used tools when you're down to picking and placing SMDs manually.

Tweezers come in many shapes and sizes. However, despite their variety, they have at least one common feature: a relatively large force is required to keep the ends firmly pressed against each other. We're not talking about the physical force exerted by your fingers to close the arms, but the fact that a normal pair of tweezers will easily 'launch' a tiny part like an SMD if it is not perfectly straight in the clamps, or if you accidentally hit something while moving the part from container or reel onto the circuit board. In nearly all cases, the SMD part then becomes an easy prey for the missus' vacuum cleaner. Very annoying, and a shame to lose the part.

Fortunately, there exists a type of

tweezers that's perfect for us. Besides, it's cheap and widely available. Its small size, low spring load and flat jaws make it the tool for manual fitting of SMD parts. To cap it all, you may have already this perfect pair of tweezers — and here's a secret: it is one of the tools contained in the well-known Victorinox Swiss Army Knife!

If you want one, the good news is that you do not necessarily have to buy an SAK. The tweezers are also available as a spare part from hardware stores or outdoor sports shops. Still, choosing a tool for a certain job is subject to personal taste — what's perfect for you may be a disaster for someone else. Some of you may argue that the SAK mini tweezers are far too small but then the price of about £2.50 each can't be a real objection if you want to give it a try.

(060229-1)

Hexadoku

Puzzle with an electronic touch

Following the super complex Alphadoku in last month's edition it's time to revert back to the 'standard' level of difficulty, which is the well-known Hexadoku. This electronics-oriented variation of Sudoku is guaranteed to give you a few hours of puzzling fun. Enter the competition for a chance to win one of several fantastic prizes.

The instructions for the puzzle are straightforward. In the diagram composed of 16x16 boxes, enter numbers in such a way that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once in every row, once in every column, and in every one of the 4x4 boxes (marked by the thicker black lines). A number of clues are given in the puzzle

and these determine the start situation.

Your solution may win a prize and requires only the numbers in the grey boxes to be sent to us (see below). The puzzle is also available as a **free download** from our website (Magazine → 2006 → September).

(065070-1)

2			C			B		6			4		8	5	
6	4	5			A	8					0	D		3	
		B	1		E	C		7		0		F		9	
0				1	7			4		D				C	
		6	7	E				B			D	2		4	
		0	3	8	2			F	9			C	5	7	
B				7			5	3	C	4			A	1	E
	1	C	5			0						8		F	D
	C				8			D		A				E	F
	5			B	4		7	8	3				0		
8						D	E				9	B	6		
	B	A	6	9		5			4			7	C	3	8
	2				5	8	F		B	7					
	7	D		0						5		3			2
		3			B	4	2	A	D			F	7		
F								C	2				4		6

Entering the competition

Please send the numbers in the grey boxes by email, fax or post to

Elektor Electronics Hexadoku
 Regus Brentford
 1000 Great West Road
 Brentford TW8 9HH
 United Kingdom.
 Fax (+44) (0)208 2614447
 Email:
 editor@elektor-electronics.co.uk
 Subject: hexadoku 09-2006.

The closing date is **1 October 2006**.
 Competition not open to employees of
 Segment b.v., its business partners
 and/or associated publishing houses.

Prize winners

The solution of the June 2006 Hexadoku is: 1A6DC.
 The **E-blocks Starter Kit Professional** goes to:
 JohnHoughton
 (Richmond).

An Elektor SHOP Voucher worth £35.00 goes to:

Ian K. Rolfe (Newbury),
 Luciano Poretti (Arconate, I) and
 Richard Mansfield (Eastbourne).

Well done everybody!

Solve Hexadoku and win!

Correct solutions enter a prize draw for an

E-blocks Starter Kit Professional



worth **£248.55** and three

Elektor Electronics Shop Vouchers worth **£35** each.

We believe these prizes should encourage all our readers to participate!

ELEKTOR SHOWCASE

To book your showcase space contact Huson International Media

Tel. 0044 (0) 1932 564999 Fax 0044 (0) 1932 564998

ATC SEMITEC LTD

www.atcsemitec.co.uk

Thermal and current-sensitive components for temperature control and circuit protection;

- NTC Thermistors
- Current Diodes
- Thermostats
- Re-settable Fuses
- Thermal Fuses
- Temperature Sensors

Call today for free samples and pricing

Tel: 0870 901 0777 Fax: 0870 901 0888

BETA LAYOUT

www.pcb-pool.com

Beta layout Ltd Award-winning site in both English and German offers prototype PCBs at a fraction of the cost of the usual manufacturer's prices.



DESIGN GATEWAY

www.design-gateway.com

PalmLogic II US\$ 399.00

- Compact Logic Analyzer (L116mm x W73.3mm x T3mm)
- High sampling rate (400 MHz/ 8ch, 200 MHz/16ch, 100 MHz/32ch)
- USB 2.0 high speed mode
- 8MB memory storage
- Bus Analyzer function
- Multiple waveform windows
- Waveform save/restore



DESIGN GATEWAY

www.design-gateway.com

True PCI Starter Kit US\$135.00

- PCI Development Kit
- Based on 200,000 gates FPGA
- Extension connectors for 72 pin I/O
- Configuration support for JTAG and slave serial
- Free PCI Core for Target Mode



DESIGN GATEWAY

www.design-gateway.com

Ethernet IO US\$115.00

- 8 bits embedded network microcontroller
- 6 channels available for 10 bits ADC
- Ethernet 10 BASE T 10 Mb
- UART port RS232/RS485, Max Speed at 115200bps
- 35 bits general purpose I/O
- 500 bytes user area flash memory



DESIGN GATEWAY

www.design-gateway.com

VariClock ... US\$163.00

- Adjustable clock signal synthesizer
- 3 rotary switches for frequency setting
- Standard DIP pin arrangement
- Support both 3V/5V by on-board regulator

VC250M14P Frequency range : 25-400 MHz

Frequency setting : 1MHz step

VC100M14P Frequency range : 25-100 MHz

Frequency setting : 100 kHz step for 25-50 MHz

: 200 kHz step for more than 50 MHz



AVIT RESEARCH

www.avitresearch.co.uk

USB has never been so simple...

with our USB to Microcontroller Interface cable. Appears just like a serial port to both PC and Microcontroller, for really easy USB connection to your projects, or replacement of existing RS232 interfaces.



See our webpage for more details. Only £29.99 inc vat.

BAEC

<http://baec.tripod.com>

"The British Amateur Electronics Club Archive Website. Archiving extracts from 140+ Newsletters from 1966-2002. Currently have interesting and useful selected articles from 12 Newsletters. Also a section about built electronics projects with schematics and photos. Plus useful info., downloads and links. NO ADVERTS!"



COMPULOGIC LTD

www.compulogic.co.uk

Internet Remote Control Starter Kit £139.99

Create a simple web based remote control interface for many applications

- Miniature Web Server Module
- Analogue/Digital Module
- PSU
- Manuals, software, example HTML code



CONFORD ELECTRONICS

<http://www.confordelec.co.uk>

Lightweight portable battery/mains audio units offering the highest technical performance.

Microphone, Phantom Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

DANBURY ELECTRONICS

<http://www.DanburyElectronics.co.uk>

Transformer manufacturers since 1983. Visit our new site! Also link directly to Mike Holme's Valve/-Tube DIY amplifier site, featuring our standard Audio Transformers (Mains, Output, Chokes, PP, SE, etc).

EAGLEPICS

<http://www.eaglepics.co.uk>

Embedded Internet Solutions

- Stand alone TCP/IP module
- Platform independent
- Simple "AT-like" command set
- GPRS or modem connection
- E-Mail, FTP, HTTP, UDP
- Development board available
- Free development utilities
- Free UDP-only stack



EASYSYNC

<http://www.easysync.co.uk>

EasySync Ltd sells a wide range of single and multi-port USB to RS232/RS422 and RS485 converters at competitive prices.



ELNEC

www.elnec.com

- device programmer manufacturer
- selling through contracted distributors all over the world
- universal and dedicated device programmers
- excellent support and after sale support
- free SW updates
- reliable HW
- once a months new SW release
- three years warranty for most programmers



FIRST TECHNOLOGY TRANSFER LTD.

<http://www.ftt.co.uk/PICProTrng.html>

Microchip Professional C and Assembly Programming Courses.

The future is embedded.

Microchip Consultant / Training Partner developed courses:

- Distance learning / instructor led
- Assembly / C-Programming of PIC16, PIC18, PIC24, dsPIC microcontrollers
- Foundation / Intermediate



FUTURE TECHNOLOGY DEVICES

<http://www.ftdichip.com>

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s.

Complete with PC drivers, these devices simplify the task of designing or upgrading peripherals to USB



FUTURLEC

<http://www.futurlec.com>

Save up to 60% on

- Electronic Components
 - Microcontrollers, PIC, Atmel
 - Development Boards, Programmers
- Huge range of products available on-line for immediate delivery, at very competitive prices.




HEROS TECHNOLOGY LTD

www.herostechnology.co.uk

Introducing Modular Concept for microcontrollers.

Suitable for Developers, Pre-production, Educational and Hobby applications.

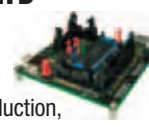- WinPIC2006 USB full speed programmer.
- CPU microcontroller modules.
- Peripheral modules for all microcontrollers.



products and services directory

JLB ELECTRONICS

www.jlbelectronics.com


Suppliers of electrical / electronic parts and consumables. Including:

- Cable ties / bases
- Tools / hardware
- Bootlace ferrules
- Connectors
- Solvent sprays & cleaners
- PVC Tape
- Heat Sink compound

KMK TECHNOLOGIES Ltd.

<http://www.kmk.com.hk>

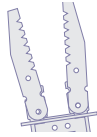Low Cost DIY Robotic Kits and Computer Controller Boards.



LONDON ELECTRONICS COLLEGE

<http://www.lec.org.uk>

Vocational training and education for national qualifications in Electronics Engineering and Information Technology (BTEC First National, Higher National NVQs, GCSEs and Advanced Qualifications). Also Technical Management and Languages.

MQP ELECTRONICS

<http://www.mqpelectronics.co.uk>

Leaders in Device Programming Solutions.

- Online shop
- Low Cost Adapters for all Programmers
- Single Site and Gang Programmers
- Support for virtually any Programmable Device



NEW WAVE CONCEPTS

www.new-wave-concepts.com

Software for hobbyists:

- Livewire circuit simulation software, only £34.99
- PCB Wizard circuit design software, only £34.99

Available from all Maplin Electronics stores and www.maplin.co.uk.



OLD COLONY SOUND LAB


www.audioXpress.com

Premier source for DIY audio for 35 years!

New catalog features:

- Books
- CDs
- Test & Measurement
- Kits

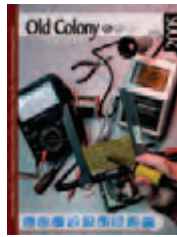Full range of products and magazines for the DIY audio enthusiast!



PCB WORLD

<http://www.pcbworld.org.uk>

World-class site: Your magazine project or prototype PCB from the artwork of your choice for less. Call Lee on 07946 846159 for details. Prompt service.

ROBOT ELECTRONICS

<http://www.robot-electronics.co.uk>

Advanced Sensors and Electronics for Robotics

- Ultrasonic Range Finders
- Compass modules
- Infra-Red Thermal sensors
- Motor Controllers
- Vision Systems
- Wireless Telemetry Links
- Embedded Controllers



SK PANG ELECTRONICS

<http://www.skpang.co.uk>

- ELM OBDII IC
 - VAG-COM Interface
 - OBDII connector and cable
 - Modtronix Micro X board
 - Embedded Ethernet Controller
 - PIC Microcontroller, CAN Bus driver
- Major credit cards taken online.



ULTRALEDS

[Ultraleds.co.uk](http://www.ultraleds.co.uk)

<http://www.ultraleds.co.uk>

tel: 0871 7110413

Large range of low cost Ultra bright leds and Led related lighting products. Major credit cards taken online with same day depatch.

USB INSTRUMENTS

<http://www.usb-instruments.com>

USB Instruments specialises in PC based instrumentation products and software such as Oscilloscopes, Data Loggers, Logic Analysers which interface to your PC via USB.



VIRTINS TECHNOLOGY

www.virtins.com

PC and Pocket PC based virtual instrument for electronics enthusiasts, students, professionals and scientists, including sound card real time oscilloscope, spectrum analyzer, and signal generator. Free to download and try.



SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business, Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just £220 + VAT (£20 per issue for eleven issues) Elektor will publish your company name, website address and a 30-word description

- For £330 + VAT for the year (£30 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour image - e.g. a product shot, a screen shot from your site, a company logo - your choice

Places are limited and spaces will go on a strictly first come, first served basis. So please fax back your order today!

I wish to promote my company, please book my space:

- Text insertion only for £220 + VAT
- Text and photo for £330 + VAT

NAME:.....ORGANISATION:.....

JOB TITLE:.....

ADDRESS:.....

.....

.....TEL:.....

PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 00-44-(0)1932 564998

COMPANY NAME.....

WEB ADDRESS.....

30-WORD DESCRIPTION.....

.....

.....

.....

.....

.....

ELECTRONIC ENTHUSIASTS

Only one magazine tests its projects and circuits in its own lab before publication

**ELEKTOR ELECTRONICS
THE ELECTRONICS &
COMPUTER MAGAZINE**

**SUBSCRIBE
TODAY!**

Contact: Worldwide Subscription Service Ltd,
Unit 4 Gibbs Reed Farm, Pashley Road,
Ticehurst TN5 7HE
Telephone: 01580 200657 Fax: 01580 200616
www.elektor-electronics.co.uk

E-blocks Starter Kits

with a 30% discount!

Free downloads available on
www.elektor-electronics.co.uk/eblocks !




C for AVR microcontrollers single user	£	118.00
E-blocks AVR multiprogrammer	£	77.65
E-blocks LED board	£	14.65
E-blocks LCD board	£	19.30
E-blocks Switch board	£	14.65
Total value:	£	244.25
Special Offer:		-30%



E-blocks Easy Internet Kit		
Flowcode Professional	£	118.00
E-blocks LED board	£	14.65
E-blocks LCD board	£	19.30
E-blocks USB Multiprogrammer	£	77.30
E-blocks Switch board	£	14.65
E-blocks Internet board	£	71.95
PIC16F877	£	10.50
Ethernet 'crossover' cable	£	5.30
Total value:	£	331.65
Special Offer:		-30% £ 232.50



E-blocks Starter Kit Base		
Flowcode student/home:	£	59.90
USB Multiprogrammer:	£	77.30
Total value:	£	137.20
Special Offer:		-30%

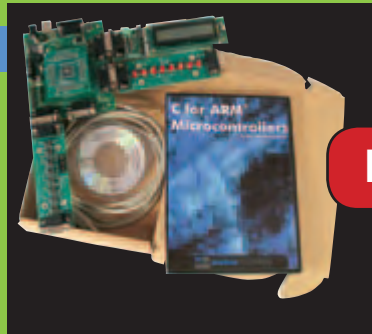

NEW

E-blocks Easy ARM kit		
C for ARM microcontrollers single user	£	118.00
E-blocks ARM multiprogrammer	£	89.20
E-blocks LED board	£	14.65
E-blocks LCD board	£	19.30
E-blocks Switch board	£	14.65
Total value	£	255.80
Special Offer:		-33% £ 171.80



Flowcode professional	£	118.00
USB Multiprogrammer	£	77.30
E-blocks LED board	£	14.65
E-blocks Switch board	£	14.65
E-blocks LCD board	£	19.30
Total value:	£	243.90
Special Offer:		-32% £ 166.00
Extra: PIC16F877 microcontroller		



E-blocks Easy CAN Kit		
Flowcode Professional	£	118.00
E-blocks LED board	£	14.65
E-blocks Switch board	£	14.65
2 x E-blocks LCD board	£	38.60
2 x E-block USB Multiprogrammer	£	154.60
2 x E-blocks CAN board	£	67.00
2 x PIC16F877	£	21.00
Total value:	£	428.50
Special Offer:		-30% £ 299.00

Learn more about E-blocks?

For more information, visit
www.elektor-electronics.co.uk/eblocks

Ordering

Use the order form at the back or go to
www.elektor-electronics.co.uk
 E-blocks will be shipped after receipt of payment.
 Prices are exclusive of postage.



Order now using the Order Form in the Readers Services section in this issue.

Elektor Electronics (Publishing)
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom

Telephone +44 (0) 208 261 4509
Fax +44 (0) 208 261 4447
Email: sales@elektor-electronics.co.uk

More information on www.elektor-electronics.co.uk

CD-ROM BESTSELLERS

Home Automation

This CD-ROM provides an overview of what manufacturers offer today in the field of Home Networking, both wired and wireless. The CD-ROM contains specifications, standards and protocols of commercially available bus and network systems. For developers, there are datasheets of specific components and various items with application data. End-users and hobbyists will find ready-made applications that can be used immediately.



£12.95 (US\$ 22.90)

ECD Edition 3

Elektor's Components Database gives you easy access to design data for over 5,000 ICs, more than 35,000 transistors, FETs, thyristors and triacs, just under 25,000 diodes and 1,800 optocouplers. All database applications are fully interactive, allowing the user to add, edit and complete component data.



£14.95 (US\$ 26.50)

Robotics


A large collection of data-sheets, software tools, tips, tricks and Internet links to assorted robot constructions and general technical information. All aspects of modern robotics are covered, from sensors to motors, mechanical parts to microcontrollers, not forgetting matching programming tools and libraries for signal processing.



£12.05 (US\$ 21.25)

Microcontroller Basics

Microcontrollers have become an indispensable part of modern electronics. They make things possible that vastly exceed what could be done previously. Innumerable applications show that almost nothing is impossible. There's thus every reason to learn more about them. This book offers more than just a basic introduction. It clearly explains the technology using various microcontroller circuits and programs written in several different programming languages. In the course of the book, the reader gradually develops increased competence in converting his or her ideas into microcontroller circuitry.

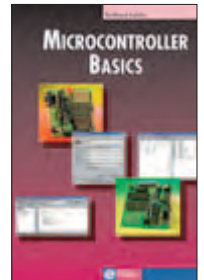

ISBN 0-905705-67-X
230 Pages
£18.70 (US\$ 33.70)

Visual Basic for Electronics Engineering Applications

This book is targeted towards those people that want to control existing or home made hardware from their computer. After familiarizing yourself with Visual Basic, its development environment and the toolset it offers are discussed in detail. Each topic is accompanied by clear, ready to run code, and where necessary, schematics are provided that will get your projects up to speed in no time.



ISBN 0-905705-68-8
476 Pages
£27.50 (US\$ 51.50)

BESTSELLING BOOKS

Top-5

- 1 **Visual Basic for Electronics Engineering Applications**
ISBN 0-905705-68-8 £27.50 (US\$ 51.50)
- 2 **Microcontroller Basics**
ISBN 0-905705-67-X £18.70 (US\$ 33.70)
- 3 **PC-Interfaces under Windows**
ISBN 0-905705-65-3 £25.95 (US\$ 22.90)
- 4 **Modern High-end Valve Amplifiers**
ISBN 0-905705-63-7 £25.95 (US\$ 52.00)
- 5 **308 Circuits**
ISBN 0-905705-66-1 £18.20 (US\$ 37.00)

More information on www.elektor-electronics.co.uk

Order now using the Order Form in
the Readers Services section in this issue.

GameBoy Programmable Logic Controller Ready-built PCB and I/O Extension (July/August 2006)

Turn your Gameboy games console into a powerful home automation controller with Elektor's GBPLC Module and the associated I/O Board.

Save £££'s

Reserve a set and beat the price!

The more reservation we get, the lower the price. Go to Quick Service on www.elektor-electronics.co.uk, click on Gameboy PLC and reserve your set. You can save tens of pounds! The Elektor website will indicate the current price, so you instantly see your discount!

GameBoy Programmable Logic Controller

Ready-assembled and tested
GBPLC Module and Programming
Interface


050190-91



GBPLC I²C I/O Box

Ready assembled and tested board

060098-91

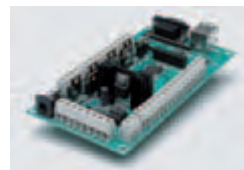

Elektor RFID-reader

(September 2006)

Ready-built and tested PCB with USB port for connection to the PC. Including USB cable; not including display and enclosure.

- Read and write 13.56 MHz RFID cards
- MIFARE and ISO 14443-A compatible
- Programmable

060132-91

£ 41.50 / \$ 77.95

LC-display


030451-72

£ 7.25 / \$ 13.65

Matching enclosure

060132-71

£ 8.90 / \$ 16.85

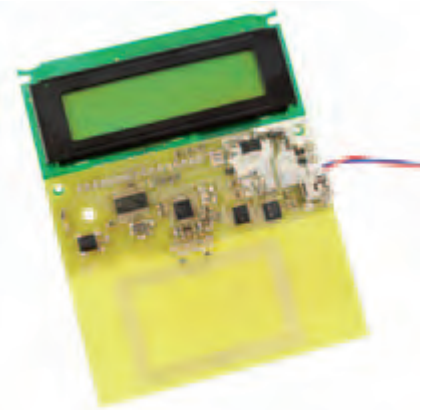

CD-ROM (all project software)

060132-81

£ 5.20 / \$ 9.75

MORE READY-BUILT PROJECTS

	£	\$
ClariTy 300-W Class-T Amplifier		
030217-91 Amplifier board with SMDs pre-fitted; cores for L1 & L2	34.50	55.70
Electrosmog Tester		
050008-91 PCB, ready built and tested	50.00	94.25
050008-71 Matching enclosure	10.25	19.30
Flash Microcontroller Starter Kit		
010208-91 Ready-assembled PCB incl. software, cable, adapter & related articles	69.00	112.50
Gameboy Digital Sampling Oscilloscope (GBDSO)		
990082-91 Ready-assembled board, incl. the PC software and related articles	103.00	183.00
LPC210x ARMeE Development System		
040444-91 Processor board, ready-made and tested	25.50	48.05
Micro Webserver with MSC1210 Board		
030060-91 Microprocessor Board, ready-assembled	75.90	142.95
044026-91 Network Extension Board, ready-assembled	44.50	83.95
044026-92 Combined package (030060-91 & 044026-91 & related articles)	117.50	220.95

NO. 358 SEPTEMBER 2006

Elektor RFID Reader

060132-91 PCB, ready assembled & tested, with USB cable	41.50	77.95
030451-72 Standard back-lit LC display	7.25	13.65
060132-71 Matching enclosure	8.90	16.85
060132-81 CD-ROM, all project software	5.20	9.75

Experimental RFID Reader

060221-11 Disk, all project software	5.20	9.75
060221-41 ATmega16, programmed	8.90	16.85

DiSEqC Monitor

040398-11 Disk, PIC source & hex code	5.20	9.75
040398-41 PIC16F628A-20/P, programmed	5.50	10.35

USB/DMX512 Converter

060012-11 Disk, all project software	5.20	9.75
060012-41 PIC16C745, programmed	6.90	12.95

NO. 356/357 JULY/AUGUST 2006

RC Servo Tester/Exerciser

040172-11 Disk, project software	5.20	9.75
040172-41 PIC16F84(A), programmed	10.30	19.40
040172-71 Kit, incl. PCB, controller, all parts	22.70	42.85

LED Thermometer

030190-11 Disk, project software	5.20	9.75
030190-41 PIC16F873-20/SP, programmed	16.50	31.00

Toothbrush Timer

050146-11 Disk, project software	5.20	9.75
050146-41 AT90S2313-10PC, programmed	6.90	12.95

Easy Home Control

050233-11 Disk, project software	5.20	9.75
050233-41 PIC16F84, programmed	10.30	19.40

Universal LCD Module

050259-11 Disk, project software	5.20	9.75
050259-41 AT90S2313, programmed	6.90	12.95

1-Wire Thermometer with LCD

060090-11 Disk, project software	5.20	9.75
060090-41 PIC16F84A-04CP, programmed	10.30	19.40

GBPLC - Gameboy PLC

050190-1+2 PCBs, bare, GBPLC Module & Programming Interface	11.70	22.00
050190-51 Programmed PAL, EEPROM and Flash IC	11.00	20.75
050190-91 Ready-built and tested GBPLC Module and Programming Interface		

GBPLC - I²C I/O Box

060098-1 PCB, bare	17.90	33.75
060098-91 Ready-built and tested board		

Binary Clock

020390-11 disk, project software	5.20	9.75
020390-41 PIC6C54-04/P, programmed	8.05	15.10

NO. 355 JUNE 2006

FM Stereo Test Transmitter

050268-1 PCB	11.70	22.00
--------------	-------	-------

Network Cable Analyser

050302-1 PCB	8.20	15.55
050302-11 Disk, PIC source code	5.20	9.75
050302-41 PIC16F874-20/P	16.90	31.85

NO. 354 MAY 2006

Onboard OBD-2 Analyser

050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, excl. LCD and Case	24.80	46.70
---	-------	-------

Due to practical constraints, final illustrations and specifications may differ from published designs. Prices subject to change. See www.elektor-electronics.co.uk for up to date information.

Onboard OBD-2 Analyser

(May 2006)

Kit of parts including ATmega board, programming adapter board, preprogrammed ATmega microcontroller and all components, but excluding LC display and Case.



050176-72

£ 24.80 / \$ 46.70

LC-display

4 x 20 characters, 60 x 98 mm, with background lighting

050176-73

£ 28.80 / \$ 54.50

Case, Bopla Unimas 160

with Perspex cover and mounting plate

050176-74

£ 15.80 / \$ 29.90

Elektor Electronics (Publishing)

Regus Brentford

1000 Great West Road

Brentford TW8 9HH

United Kingdom

Tel.: +44 (0) 208 261 4509

Fax: +44 (0) 208 261 4447

Email: sales@elektor-electronics.co.uk

Kits & Modules

OBD-2 Analyser

(July/August 2005)

Kit of parts including PCB, programmed controller, components (including IC7 ; IC3 = PCA82C250, 12 V), enclosure and RS232 cable.

OBD cable not included.

050092-71

£ 52.50 / \$ 96.95

OBD cable

050092-72

£ 27.55 / \$ 51.95



RC Servo Tester / Exerciser

(July/August 2006)

Kit of parts including PCB, programmed controller and all components.

040259-71

£ 22.70 / \$ 42.85



050176-73	LCD, 4x20 characters with backlight	28.80	54.50
050176-74	Case, Bopla Unimas 160 with Perspex cover and mounting plate	15.80	29.90
050176-42	ATmega16, programmed	10.30	19.45
050092-71	OBD-2 Analyser: Kit of parts without cable	52.50	96.95
050092-72	OBD-2 Analyser: DB9 to OBD adapter cable	27.55	51.95

Mini ATmega Board

050176-1 PCB, includes adapter PCB 050176-2

8.95 16.85

NO. 353 APRIL 2006

Simple rechargeable A Cell Analyser

050394-1 PCB, bare 4.80 9.04

050394-11 Disk, PC Software 5.18 9.75

Universal SPI Box

050198-41 AT89C2051-24PC, Programmed 7.25 13.65

NO. 352 MARCH 2006

Application Board for R8C/13

050179-92 Ready-assembled board 48.27 90.94

050179-1 PCB 13.77 25.94

030451-72 LCD with backlight 7.25 13.65

030451-73 Poly-LED display 25.50 48.05

FPGA-Prototyping board

050370-91 Ready assembled board 181.80 333.50

For subscribers 216.30 398.50

For non-subscribers 216.30 398.50

Telephone Eavesdropper

030379-1 PCB 9.05 17.05

Versatile FPGA Module

040477-91 Ready assembled plug-on module 181.80 333.50

For subscribers 216.30 398.50

For non-subscribers 216.30 398.50

NO. 351 FEBRUARY 2006

Brushless Motor Controller

050157-41 ST7MC1, programmed 3.80 7.15

A 16-bit Tom Thumb

050179-91 R8C Starter Kit 8.30 15.60

050179-C5 Set of 5 pcs. R8C13 microcontroller only 20.70 39.00

NO. 350 JANUARY 2006

95-watt Laptop PSU Adaptor

050029-1 PCB 4.80 9.05

Automatic Attic Window Controller

050139-11 Disk, PIC source & hex code 5.20 9.75

050139-41 PIC16F84A-20/P, programmed 13.10 24.65

030451-72 LCD Module 2x16 characters 7.25 13.65

030451-73 PLED Module 2x16 characters 25.50 48.05

SMD Reflow Soldering Oven

050319-11 Disk, source and hex code 5.20 9.75

050319-41 AT89C52/24JI, programmed 7.60 14.25

030451-72 LCD Module 2x16 characters 7.25 13.65

030451-73 PLED Module 2x16 characters 25.50 48.05

Timer Switch for Washing Machine

050058-1 PCB 8.90 16.70

050058-11 Disk, PIC source & hex code 5.20 9.75

050058-41 PIC16F84, programmed 13.10 24.65

NO. 349 DECEMBER 2005

From A to D via USB

050222-1 PCB 7.95 14.95

050222-41 IOW24-P, programmed 9.40 17.75

Telephone Supervisor

050039-41 PIC16F628-20/P, programmed 8.20 15.55

050039-81 CD-ROM, PIC hex & source codes, LCM First Server 6.90 12.95

NO. 348 NOVEMBER 2005

Remote Control by Mobile Phone

040415-1 PCB 6.20 11.65

040415-11 Disk, PIC source & hex files 5.20 9.75


040415-41 PIC16F84A-20/P, programmed 10.30 19.50

Products for older projects (if available) may be found on our website www.elektor-electronics.co.uk

home construction = fun and added value

Free!

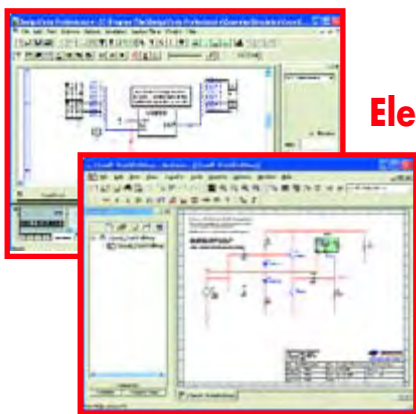Every copy of the October 2006 issue of **Elektor Electronics** will come with a **free electronics simulation software DVD**. Be sure to get your copy!



Electronics Simulation Software

Rather than building prototype after prototype, companies developing electronic products now almost invariably use software simulating the end result. E-simulation not only saves time and money in the design phase but also allows a good idea to be obtained about the operation, look and feel of the final product. The October 2006 issue of *Elektor Electronics* comes with a free DVD on which we've compiled an impressive collection of E-Simulation software — not just demos, trials and limited versions but also fully functional programs specially designed to simulate (and in some case also design) electronic circuits.

GBECG - Gameboy Electrocardioscope

We know from reader correspondence that many of you would like to see a piece of equipment (for home construction, of course) that enables an electrocardiogram (ECG) to be written on the spot. The reasons are mixed: out of technical curiosity; personal interest; to surprise one's cardiologist or the desire to step into medical proceedings in a well prepared manner. Our ECG writer is a plug-in unit for the famous Gameboy games console, type Classic, Pocket, Color or Advance.



PIC In-Circuit Debugger/Programmer *

PIC micros from the 8-bit 16F and 18F series are found in lots of equipment and the devices are very popular among *Elektor* readers as they allow interesting applications to be built using almost no hardware. Our PIC ICD/Programmer is largely compatible with Microchip's ICD2 module.

Also...

Programmable Laser Lightshow; Wireless Key*; Universal USB Driver; Zigbee with Xbee; FPGA Course (5); Hexadoku.

* due to lack of space these articles could not be accommodated in the current issue.

RESERVE YOUR COPY NOW!

UK mainland subscribers will receive the magazine between 16 and 20 September 2006.

The October 2006 issue goes on sale on Thursday 21 September 2006 (UK distribution only).

Article titles and magazine contents subject to change, please check our website.

NEWSAGENTS ORDER FORM

SHOP SAVE / HOME DELIVERY

Please save / deliver one copy of *Elektor Electronics* magazine for me each month

Name:

Address:

Post code:

Telephone:

Date:

Signature:



Please cut out or photocopy this form, complete details and hand to your newsagent. *Elektor Electronics* is published on the third Friday of each month, except in July. Distribution S.O.R. by Seymour (NS).

www.elektor-electronics.co.uk

www.elektor-electronics.co.uk

www.elektor-electronics.co.uk

Elektor Electronics on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, circuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the *Elektor Electronics* Shop you'll find all other products sold by the publishers, like CD-ROMs, kits and books. A powerful search function allows you to search for items and references across the entire website.

Also on the Elektor Electronics website:

- Electronics news and Elektor announcements
- Readers Forum,
- PCB, software and e-magazine downloads
- Surveys and polls
- FAQ, Author Guidelines and Contact



ORDERING INSTRUCTIONS, P&P CHARGES

Except in the USA and Canada, all orders, except for subscriptions (for which see below), must be sent BY POST or FAX to our Brentford address using the Order Form overleaf. On-line ordering: <http://www.elektor-electronics.co.uk>

Readers in the USA and Canada may (but are not obliged to) send orders, except for subscriptions (for which see below), to the USA address given on the order form. Please apply to Old Colony Sound for applicable P&P charges. Please allow 4-6 weeks for delivery.

Orders placed on our Brentford office must include P&P charges (Priority or Standard) as follows:

UK: £4.00 Europe: £5.00 (Standard) or £7.00 (Priority) Outside Europe: £8.00 (Standard) or £12.00 (Priority)

HOW TO PAY

All orders must be accompanied by the full payment, including postage and packing charges as stated above or advised by Customer Services staff.

Bank transfer into account no. 40209520 held by Elektor Electronics (Publishing) / Segment b.v. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics (Publishing) / Segment b.v.. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics (Publishing) / Segment b.v. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA, Access, MasterCard, JCBCard and Switch cards can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

COMPONENTS

Components for projects appearing in Elektor Electronics are usually available from certain advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. Note, however, that the source(s) given is (are) not exclusive.

TERMS OF BUSINESS

Delivery Although every effort will be made to dispatch your order within 2-3 weeks from receipt of your instructions, we can not guarantee this time scale for all orders. **Returns** Faulty goods or goods sent in error may be returned for replacement or refund, but not before obtaining our consent. All goods returned should be packed securely in a padded bag or box, enclosing a covering letter stating the dispatch note number. If the goods are returned because of a mistake on our part, we will refund the return postage. **Damaged goods** Claims for damaged goods must be received at our Brentford office within 10-days (UK); 14-days (Europe) or 21-days (all other countries). **Cancelled orders** All cancelled orders will be subject to a 10% handling charge with a minimum charge of £5.00. **Patents** Patent protection may exist in respect of circuits, devices, components, and so on, described in our books and magazines. Elektor Electronics (Publishing) does not accept responsibility or liability for failing to identify such patent or other protection. **Copyright** All drawings, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes and software carriers published in our books and magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of Elektor Electronics (Publishing) in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature. Notwithstanding the above, printed-circuit boards may be produced for private and personal use without prior permission. **Limitation of liability** Elektor Electronics (Publishing) shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connexion with, the supply of goods or services by Elektor Electronics (Publishing) other than to supply goods as described or, at the option of Elektor Electronics (Publishing), to refund the purchaser any money paid in respect of the goods.

Law Any question relating to the supply of goods and services by Elektor Electronics (Publishing) shall be determined in all respects by the laws of England.

January 2006

SUBSCRIPTION RATES FOR ANNUAL

SUBSCRIPTION

	Standard	Plus
United Kingdom	£41.90	£48.80
Surface Mail		
Rest of the World	£54.50	£61.40
USA & Canada	US\$ 95.50	US\$106.50
Airmail		
Rest of the World	£68.90	£75.80
USA & Canada	US\$120.00	US\$131.00

HOW TO PAY

Bank transfer into account no. 40209520 held by Elektor Electronics (Publishing) / Segment b.v. with ABN-AMRO Bank, London. IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L. Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics (Publishing) / Segment b.v.. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics (Publishing) / Segment b.v. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA, Access, MasterCard, JCBCard and Switch cards can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

SUBSCRIPTION CONDITIONS

The standard subscription order period is twelve months. If a permanent change of address during the subscription period means that copies have to be despatched by a more expensive service, no extra charge will be made. Conversely, no refund will be made, nor expiry date extended, if a change of address allows the use of a cheaper service.

Student applications, which qualify for a 20% (twenty per cent) reduction in current rates, must be supported by evidence of studentship signed by the head of the college, school or university faculty. A standard Student Subscription costs £33.50, a Student Subscription-Plus costs £40.40 (UK only).

Please note that new subscriptions take about four weeks from receipt of order to become effective.

Cancelled subscriptions will be subject to a charge of 25% (twenty-five per cent) of the full subscription price or £7.50, whichever is the higher, plus the cost of any issues already dispatched. Subscriptions cannot be cancelled after they have run for six months or more.

January 2006

New

CD-ROM USB TOOLBOX

This CD-ROM contains technical data about the USB interface. It also includes a large collection of data sheets for specific USB components from a wide range of manufacturers.

There are two ways to incorporate a USB interface in a microcontroller circuit: add a USB controller to an existing circuit, or use a microcontroller with an integrated USB interface. Included on this CD-ROM are USB Basic Facts, several useful design tools for hardware and software, and all Elektor Electronics articles on the subject of USB.

ISBN 90-5381-212-1
£ 18.95 / US\$ 34.95

*Embedded
USB Know How*



Order now using the Order Form in the Readers Services section in this issue.

Elektor Electronics (Publishing)
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom
Tel. +44 (0) 208 261 4509

See also www.elektor-electronics.co.uk

INDEX OF ADVERTISERS

ACG Identification Technologies	www.acg.de	25	KMK Technologies Ltd, Showcase	www.kmk.com.hk	79
Altera	www.altera.com	39	Labcenter	www.labcenter.co.uk	88
ATC Semitec Ltd, Showcase	www.atcsemitec.co.uk	78	Lichfield Electronics	www.lichfieldelectronics.co.uk	19
Audioexpress, Showcase	www.audioexpress.com	78	London Electronics College, Showcase	www.lec.org.uk	79
Avit Research, Showcase	www.avitresearch.co.uk	78	MQP Electronics, Showcase	www.mqpelectronics.co.uk	79
BAEC, Showcase	http://baec.tripod.com	78	New Wave Concepts, Showcase	www.new-wave-concepts.com	79
Beta Layout, Showcase	www.pcb-pool.com	25, 78	Newbury Electronics	www.newburyelectronics.co.uk	25
Bitscope Designs	www.bitscope.com	7	Number One Systems	www.numberone.com	12
Breadboarding Systems	www.breadboarding.co.uk	3	Nurve Networks	www.xgamestation.com	25
ByVac	www.byvac.co.uk	12	PCB World, Showcase	www.pcbworld.org.uk	79
Compulogic, Showcase	www.compulogic.co.uk	78	Peak Electronic Design	www.peakelec.co.uk	12
Conford Electronics, Showcase	www.confordelec.co.uk	78	Pico	www.picotech.com	19
Cricklewood	www.cctvcentre.co.uk	55	Quasar Electronics	www.quasarelectronics.com	45
Danbury, Showcase	www.DanburyElectronics.co.uk	78	Robot Electronics, Showcase	www.robot-electronics.co.uk	79
Design Gateway, Showcase	www.design-gateway.com	78	Scantool	www.ElmScan5.com/epe	6
Eaglepics, Showcase	www.eaglepics.co.uk	78	Showcase	78, 79
Easysync, Showcase	www.easysync.co.uk	78	SK Pang Electronics, Showcase	www.skpang.co.uk	79
Elneq, Showcase	www.elneq.com	78	Ultraleds, Showcase	www.ultraleds.co.uk	79
Eurocircuits	www.thepcbshop.com	6	University of Derby	www.vertigo.derby.ac.uk	55
First Technology Transfer Ltd, Showcase	www.ftt.co.uk	78	USB Instruments, Showcase	www.usb-instruments.com	79
Forest	www.fored.co.uk	59	Virtins Technology, Showcase	www.virtins.com	79
Future Technology Devices, Showcase	www.ftdichip.com	13, 78			
Futurlec, Showcase	www.futurlec.com	78			
Heros Technology, Showcase	www.herotechnology.co.uk	78			
Jaycar Electronics	www.jaycarelectronics.co.uk	2			
JLB Electronics, Showcase	www.jlbelectronics.com	79			

**Advertising space for the issue of 17 October 2006
may be reserved not later than 19 September 2006**

with Huson International Media – Cambridge House – Gogmore Lane – Chertsey, Surrey KT16 9AP – England – Telephone 01932 564 999 – Fax 01932 564998 – e-mail: gerryb@husonmedia.com to whom all correspondence, copy instructions and artwork should be addressed.

PROTEUS

ELECTRONIC DESIGN

FROM CONCEPT

TO COMPLETION

SCHEMATIC CAPTURE PROSPICE EMBEDDED SIMULATION PCB DESIGN

ISIS SCHEMATIC CAPTURE

A powerful capture package tailored for today's engineer and designed to allow rapid entry of complex schematics for simulation and PCB Layout.

PROSPICE MIXED MODE SIMULATOR

A customised implementation of the industry standard Berkeley SPICE 3F5 engine with extensive optimisations and enhancements for true mixed mode simulation and circuit animation.

VSM VIRTUAL SYSTEM MODELLING

The world's first and best schematic based microcontroller co-simulation software. Proteus VSM allows you to simulate the interaction between software running on a microcontroller and any analog or digital electronics connected to it. This streamlines the project lifecycle and obviates the need for expensive hardware analysis tools.

ARES PCB DESIGN

A modern and professional layout package which seamlessly integrates with the ISIS capture software. Features such as autoplacement and autorouting, interactive DRC and an intuitive interface all serve to maximise productivity and reduce time to market.

LABCENTER ELECTRONICS LTD.

A technology pioneer in the EDA industry since 1988.
Technical support direct from the program authors.
Flexible packages and pricing tailored to customer requirements.

CONTACT US NOW

to discuss requirements or
request a **FREE** evaluation copy.

labcenter  www.labcenter.co.uk
Electronics

Tel: 01756 753440
Fax: 01756 752857
Email: info@labcenter.co.uk

Labcenter Electronics Ltd., 53-55 Main Street, Grassington,
North Yorks, BD23 5AA. Registered in England 4692454